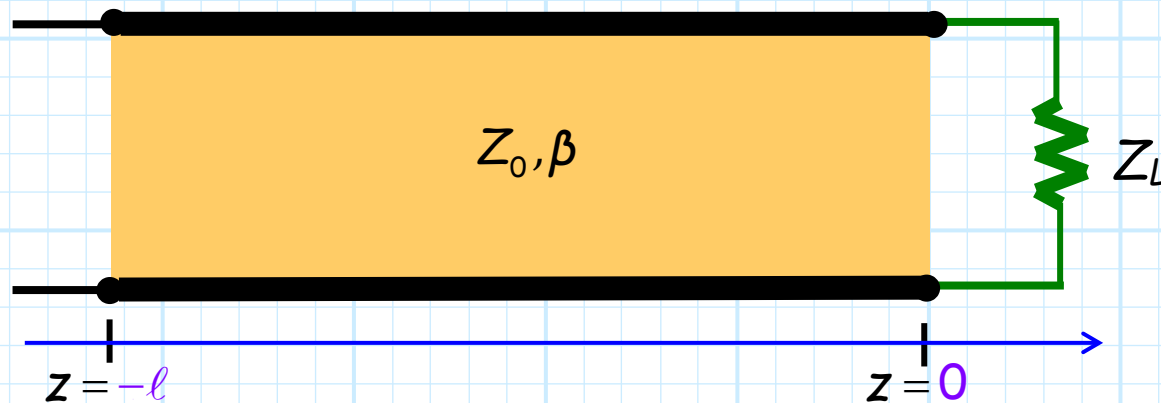


The Input Impedance of a Terminated Transmission Line

Consider a **lossless** line, length ℓ , terminated with load Z_L .





Note that this terminated transmission line is a **one-port device**!

It's not Z_{in} and it's not Z_0

The **two-port transmission line** acts as an **impedance transformer**—transforming the load impedance Z_L to an input impedance Z_{in} .

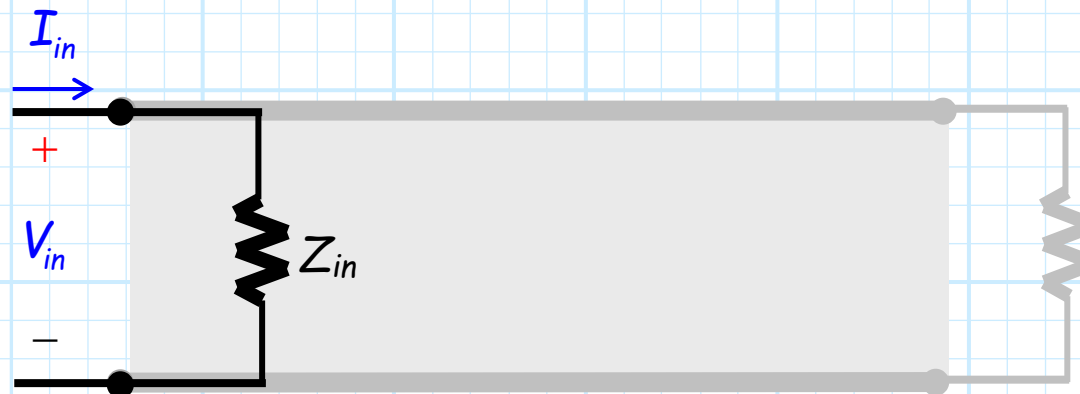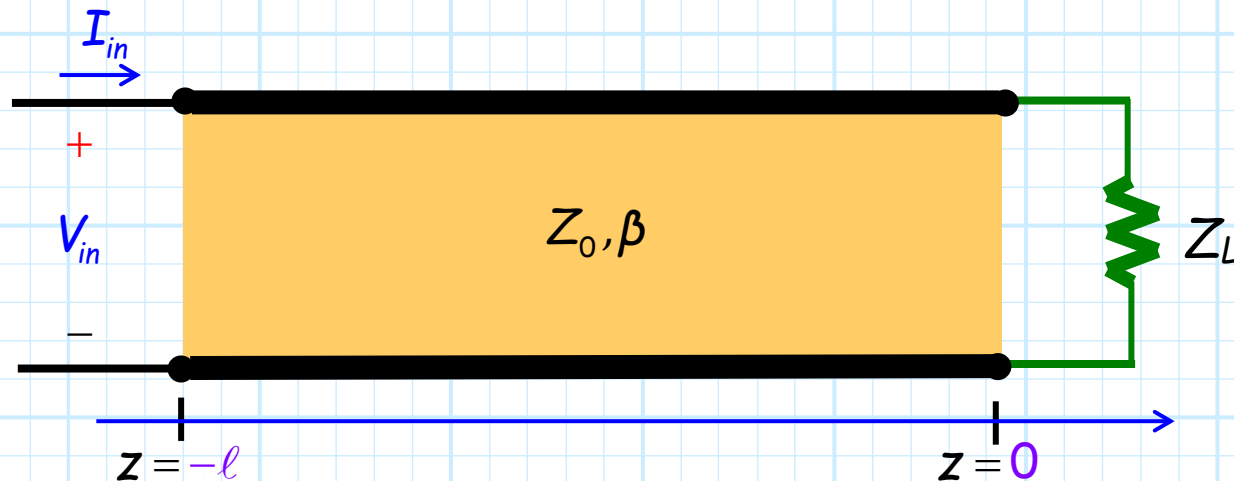Let's determine the **input impedance** of the resulting **one-port device**!



The definition of input impedance

Q: *Just how do we determine this **input** impedance?*

A: The **input impedance** of a one-port device is simply:

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

Q: *But what is V_{in} and I_{in} for this **terminated transmission line**???*

A: Sigh.


Boundary Conditions!

Using **BOUNDARY CONDITIONS**, we know that (from KVL):

$$V_{in} = V(z = -\ell)$$

And also (from KCL):

$$I_{in} = I(z = -\ell)$$

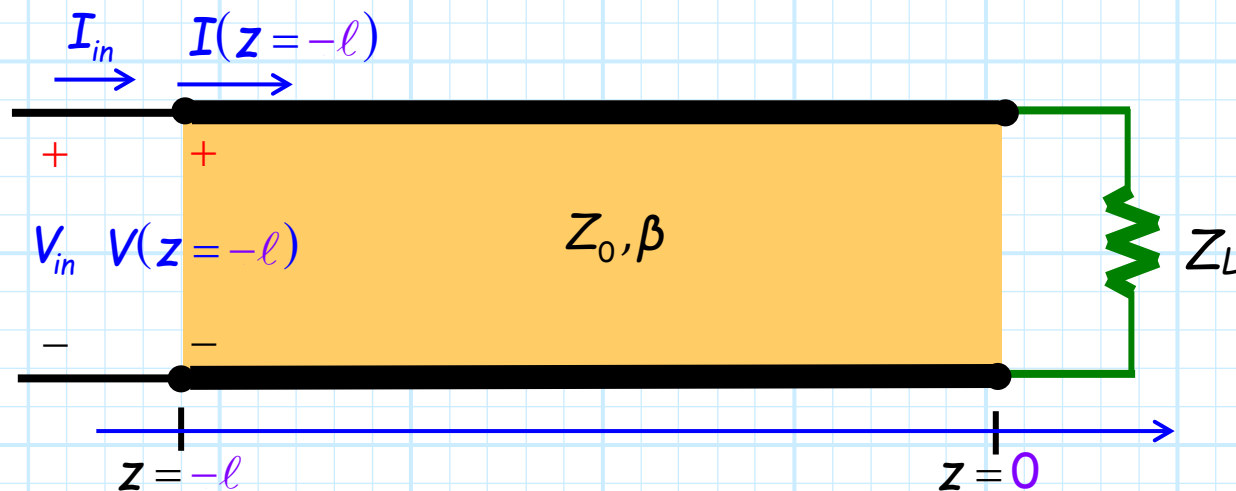

When evaluated at the beginning

Therefore, the **input impedance** of a terminated transmission line is simply the **ratio** of the total voltage and total current—**when evaluated at the beginning** of the transmission line (i.e., at index location $z = -\ell$):

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V(z = -\ell)}{I(z = -\ell)}$$

Q: Hey wait, isn't the **ratio** of total voltage $V(z)$ and total current $I(z)$ simply **line impedance**?

A: More precisely, their ratio is the line impedance **function**:

$$\frac{V(z)}{I(z)} = Z(z)$$

Say this if you wish to flunk

Q: So the *input impedance* Z_{in} of a terminated transmission line is simply equal to its *line impedance* $Z(z)$?

A: NOOOOOO!!!!!!!!!!!!!!OOOOOOOOO!!!!!!!!!!OOOOOOOOOO!!!!!!!!!!!!!!.

The input impedance of a terminated transmission line is equal to its line impedance **function**, when **evaluated** at the **beginning** of the transmission line (i.e., at index location $z = -\ell$):

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z(z = -\ell)$$

Q: You're always so *picky*.

A: But this is a **critical distinction**!

Make this make sense

The **line impedance function** $Z(z)$ describes the line impedance value at **any and all locations** z along the transmission line.

In **contrast**, **input impedance** Z_{in} is the complex **value** of the line impedance function at **one specific location**—the beginning (i.e., the **input**) of the terminated transmission line.

- * Line Impedance $Z(z)$ is a complex **function** of **position** z .
- * Input Impedance Z_{in} is a **specific complex number**—it cannot be a **function** of index z !

Remember?

Now, recalling that the line impedance function is:

$$\begin{aligned}
 Z(z) &= Z_0 \left(\frac{e^{-j\beta z} + \Gamma_L e^{+j\beta z}}{e^{-j\beta z} - \Gamma_L e^{+j\beta z}} \right) \\
 &= Z_0 \left(\frac{(\underline{Z}_L + Z_0) e^{-j\beta z} + (\underline{Z}_L - Z_0) e^{+j\beta z}}{(\underline{Z}_L + Z_0) e^{-j\beta z} - (\underline{Z}_L - Z_0) e^{+j\beta z}} \right) \\
 &= Z_0 \left(\frac{\underline{Z}_L \cos \beta z - j Z_0 \sin \beta z}{Z_0 \cos \beta z - j \underline{Z}_L \sin \beta z} \right)
 \end{aligned}$$

we can thus determine the input impedance:

$$Z_{in} = Z(z = -\ell)$$

Be careful of the signs!


$$\begin{aligned}
 Z_{in} &= Z(z = -\ell) \\
 &= Z_0 \left(\frac{e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}} \right) \\
 &= Z_0 \left(\frac{(Z_L + Z_0) e^{+j\beta\ell} + (Z_L - Z_0) e^{-j\beta\ell}}{(Z_L + Z_0) e^{+j\beta\ell} - (Z_L - Z_0) e^{-j\beta\ell}} \right) \\
 &= Z_0 \left(\frac{Z_L \cos \beta\ell + jZ_0 \sin \beta\ell}{Z_0 \cos \beta\ell + jZ_L \sin \beta\ell} \right)
 \end{aligned}$$

Note Z_{in} is equal to **neither** the load impedance Z_L , **nor** the characteristic impedance Z_0 !

$$Z_{in} \neq Z_L \quad \text{and} \quad Z_{in} \neq Z_0$$

It could be just about anything!

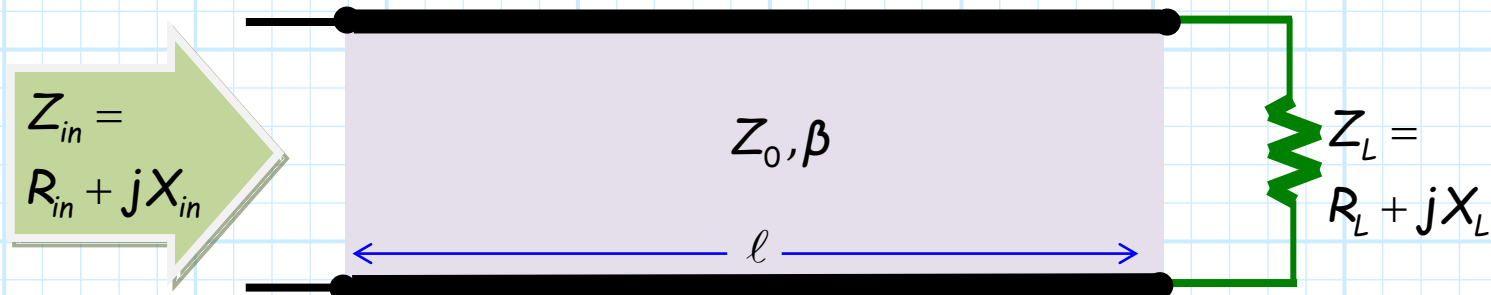Depending on the values of $\beta\ell$ and Z_0 , the **input** impedance Z_{in} can be **radically** different from the **load** impedance Z_L !



$$Z_{in} \neq Z_L \quad (\text{generally speaking})$$

Not that we're surprised

Of course, this result is **not** at all surprising.

For when a transmission line is terminated in some arbitrary **load**, the line impedance function can **change dramatically** with position z .

$$Z(z) = Z_0 \left(\frac{(Z_L + Z_0) e^{-j\beta z} + (Z_L - Z_0) e^{+j\beta z}}{(Z_L + Z_0) e^{-j\beta z} - (Z_L - Z_0) e^{+j\beta z}} \right)$$

The **input** impedance is different from the **load** impedance because the **line** impedance changes significantly between the **beginning** of the line and its **end**!

