

# PHSX 536: Homework #3

February 12, 2025

Grant Saggars

## Problem 1

(2.16) An impedance  $Z$  is built from a resistor and capacitor connected in parallel. When connected to an AC voltage source with a frequency of  $f = 60\text{Hz}$ , the impedance has a numerical value of  $Z = 1000(1 - j)\Omega$ . The impedance is connected as shown in Figure 2.19, where the voltage source has an amplitude of  $10\text{V}$  and at  $t = 0$ , the AC voltage is at a maximum.

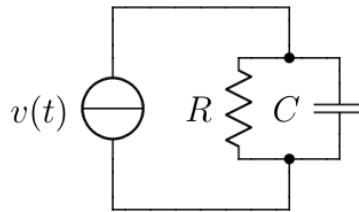


Figure 2.19: The circuit for problem 13.

(a) What are the values of  $R$  and  $C$ ?

### Solution:

We have an equivalent impedance in the branch:

$$Z = 1000(1 - j) \Omega = \left( \frac{1}{R} + \frac{1}{j\omega C} \right)^{-1}$$

Where  $\omega = 2\pi f = 120\pi$ . The real part is  $R$  and the imaginary part is  $Z_C$ , giving the convenient relation:

$$R = 1000 \Omega$$
$$1000 = \frac{1}{\omega C}, \quad \Rightarrow \quad C = \frac{1}{1000\omega} \text{ C}$$

(b) What is the power dissipated during one AC cycle in the impedance?

**Solution:**

We have a definition of power dissipation given as:

$$P = I_{\text{rms}} V_{\text{rms}} \cos \phi = I^2 R$$

$$i_R(t) = \frac{V}{R} = \frac{10\angle 0^\circ}{1000} = 0.01\angle 0^\circ \text{ A}$$

$$i_C(t) = \frac{V}{\frac{1}{j\omega C}} = j\omega CV = j(1000)\angle 90^\circ \text{ A}$$

$$i(t) = IR + IC = 0.01\angle 0^\circ + 0.01\angle 90^\circ = 0.01(1 + j) \text{ A}$$

$$\text{Re}(i(t)) = 0.01(1 + 1)^{1/2} = 0.01\sqrt{2} \text{ A}$$

We then have power dissipated:

$$P = I^2 R = (0.01)^2 \cdot 1000 = 0.1 \text{ W}$$

(c) What is the current in the resistor,  $i_R(t)$ ?

**Solution:**

Obtained in part (b)

(d) What is the current in the capacitor,  $i_C(t)$ ?

**Solution:**

Obtained in part (b)

(e) What fraction of the power from part (b) is dissipated in the resistor and the capacitor?

**Solution:**

All power is dissipated in the resistor. Capacitors don't dissipate power.

## Problem 2

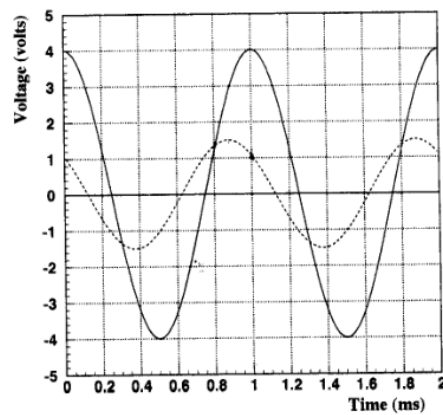


Figure 2.23: The scope trace for problem 18.

**(2.18)** Figure 2.23 is an image of your oscilloscope from lab. The solid curve is channel 1 and the dashed curve is channel 2. You may assume that the input to your circuit is displayed on channel 1 and the output from your circuit is on channel 2. Answer the following questions based on these measured scope traces.

(a) What is the frequency of the input signal?

**Solution:** There is a period of 1 second, so there is also a frequency of 1 hz.

(b) What is the "peak-to-peak" and the "RMS" voltage of the output signal?

**Solution:**

The it seems the waveform goes from -1.5 to 1.5 V, so the peak-to-peak is 3V. The RMS is, in general, given by the integral:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T V^2 \cos^2(\omega t) dt}$$

But for sinusoidal waveforms, it's simply

$$V_{\text{RMS}} = \frac{V_{\text{PK}}}{\sqrt{2}}$$

So the RMS is  $\frac{1.5}{\sqrt{2}}$ .

(c) For this particular frequency, what is the gain,  $|G|$ , of your circuit?

**Solution:**

Gain is given as output/input amplitude, so we have

$$|G| = \frac{1.5}{4} = 0.375 = 20 \log_{10}(0.375) \text{ db} = -8.52 \text{ db}$$

(d) For this particular frequency, what is the phase difference

$$\Delta\phi = \phi_{out} - \phi_{in}$$

(in degrees) between the input and output?

**Solution:**

Sinusoidal waveforms are of form:


$$V(t) = \sin(\omega t + \phi) = \sin(2\pi f + \phi)$$

Channel 1 is ahead of channel 2 by 0.2 seconds, and both have the same period of 1 second. It follows that they have a frequency of 1 Hz as well. The angular frequency is then  $2\pi$  rad / s. With the time difference,

$$\Delta\phi = 2\pi \cdot 0.2 = 0.4\pi \text{ rad} = 72^\circ$$

(e) Accurately sketch what the output signal would look like if the phase difference from part (d) were  $180^\circ$ .

**Solution:**

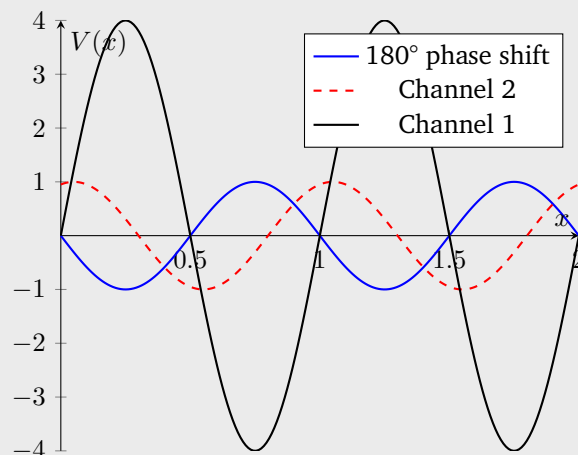

## Problem 3

(2.28) If the curve on a Bode plot is falling off at  $60\text{dB}/\text{decade}$ , what is the frequency dependence of the gain?

**Solution:**

Each pole of a bode plot indicates that it is falling off of a gain of  $-20\text{ dB} / \text{decade}$ . The frequency dependence is

$$|G| \propto \frac{1}{f^3}$$

where  $f$  is the frequency, and  $G$  is the gain.



## Problem 4

LTSpice problem: Consider the circuit shown below (this is also the circuit for Part A of Experiment #4). Use LTSpice to obtain plots of the power gain and phase shift as seen by the Ch. 2 output as a function of source frequency, with  $10 \text{ Hz} \leq f_{\text{source}} \leq 10 \text{ kHz}$ . Simulate a CR high-pass filter. Assume component values  $(C, R) = (10 \mu\text{F}, 50 \Omega)$ . (See video on "Bode plots with LTSpice.")



$Z_1$	$Z_2$	Type
L	R	low pass
C	R	high pass
R	C	low pass

### Solution:


(a) LR Circuit (low-pass):

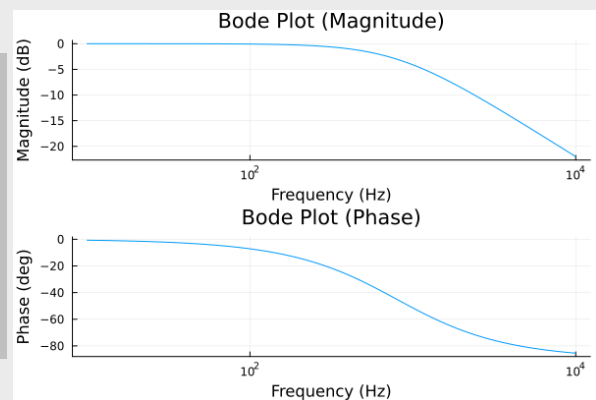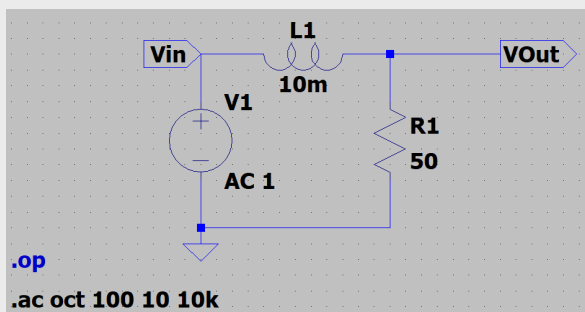

(b) CR Circuit (high-pass):

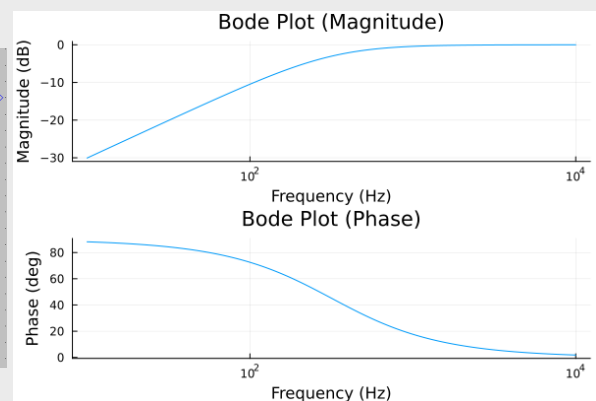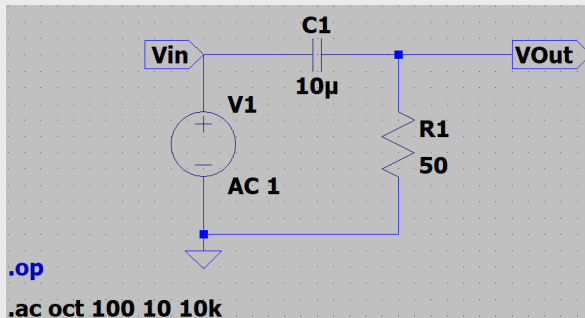

(c) RC Circuit (low-pass):

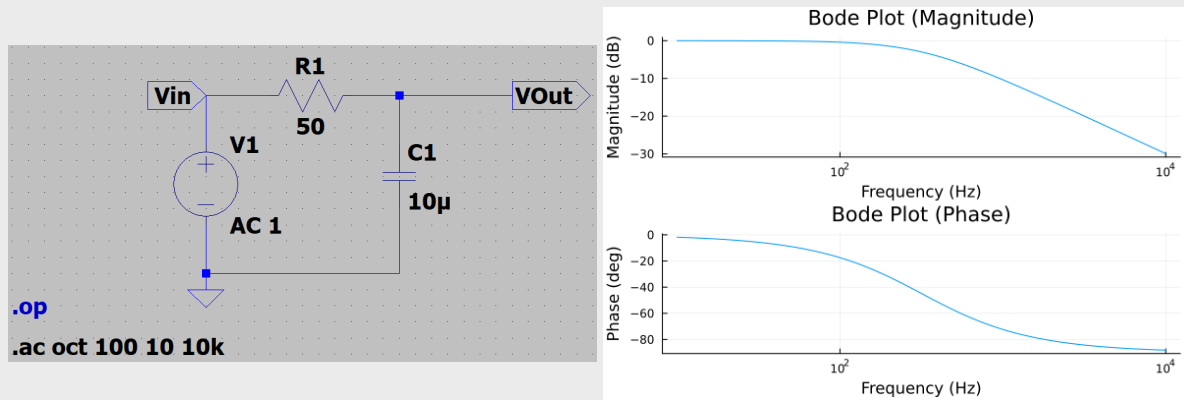

## Problem 5

LTSpice problem: Set up a series LRC circuit driven by an AC signal source. For this circuit, use  $C = 10 \mu\text{F}$ ,  $L = 10 \text{ mH}$ , and  $R = 10 \Omega$ . Generate a Bode plot of the power gain and a plot of the phase shift for  $10 \text{ Hz} \leq f_{\text{source}} \leq 10 \text{ kHz}$ . (See video on "Bode plots with LTSpice.")

**Solution:**

