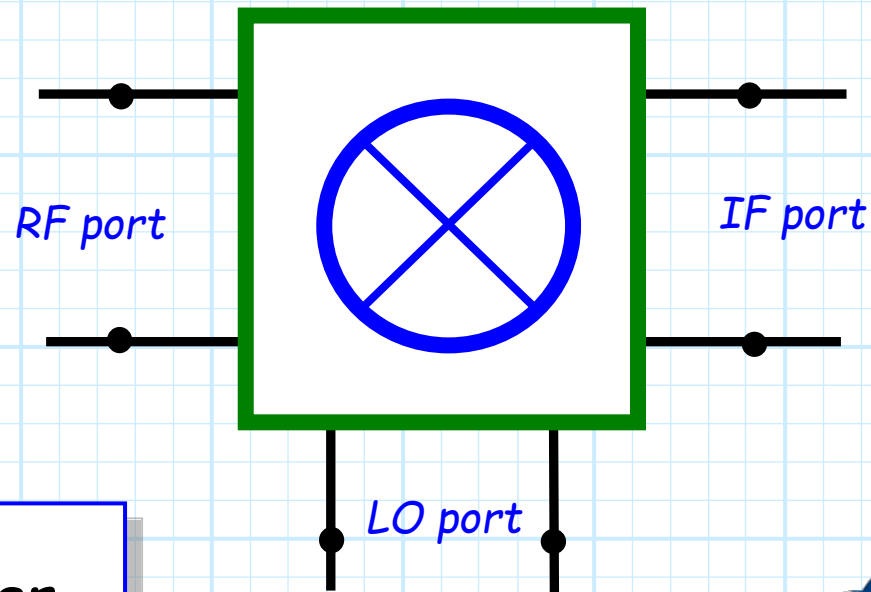


# Mixers

A **mixer** is a **three-port, non-linear** microwave device.



**The Mixer**

Usually mixers are **passive devices**, but **active** mixers also exist, and are becoming **more** and more prevalent.



## It's a multiplier

The three ports of a mixer are **distinct** and **unique**, and are typically referred to as:

- 1) The **RF** (Radio Frequency) port
- 2) The **IF** (Intermediate Frequency) port
- 3) The **LO** (Local Oscillator) port

**Q:** *So just what does a mixer **do**??*

**A:** A **clue** is in its **symbol**:  $\otimes$


**→** A mixer is a **multiplier** ( $\times$ ) !!

## An IDEAL Mixer

Say there is a real-valued signal  $v_{RF}(t)$  at the **RF mixer** port, and a signal  $v_{LO}(t)$  at the **LO mixer** port.

An **ideal** mixer would then produce at the **IF port**, a signal  $v_{IF}(t)$ , where:
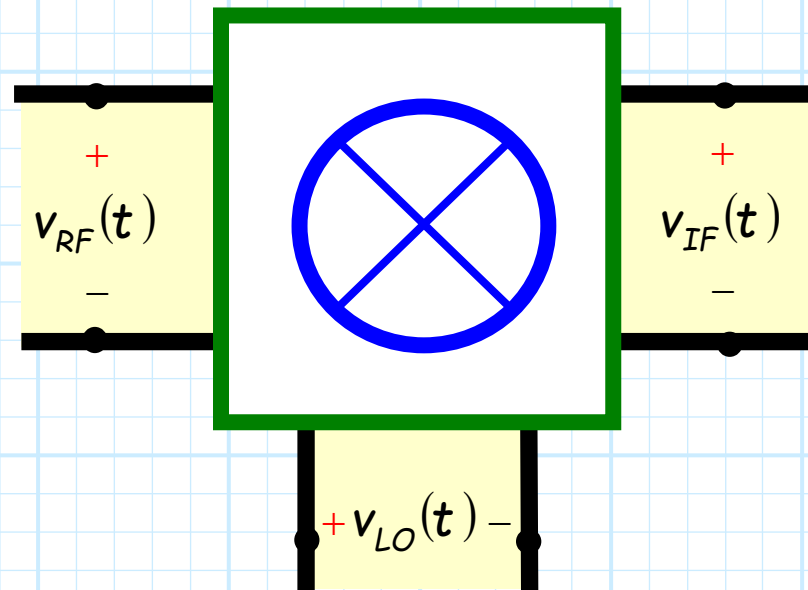
$$v_{IF}(t) = v_{RF}(t) v_{LO}(t) \quad (\text{an ideal mixer})$$



## REAL-valued multiplication

Note the **multiplied voltages** in this case (i.e.,  $v_{RF}(t)$  and  $v_{LO}(t)$ ) are:

a) **real-valued**, and

b) **some arbitrary function of time!**

In other words, a mixer does **NOT** multiply two **complex** voltages (e.g.,  $V_{RF} = j$  and  $V_{LO} = e^{j\pi/4}$ )!

Instead, it multiplies two **arbitrary real-valued function of time**.

For **example**, if:

$$v_{RF}(t) = 2t - 3t^2 \quad \text{and} \quad v_{LO}(t) = 4t^2$$

then:

$$v_{IF}(t) = v_{RF}(t) v_{LO}(t) = 8t^3 - 12t^4$$

## How and why?

**Q:** The *only* things I don't understand are:

**a)** *how this is possible, and*

**b)** *why would this would be useful?*

**A:** Let's answer the **second** part (i.e., why would this be **useful**?) first.

To see why multiplication might be **useful**, consider a case where both the RF and LO port signals are **time-harmonic**:

$$v_{RF}(t) = \cos[\omega_{RF}t] \quad \text{and} \quad v_{LO}(t) = \cos[\omega_{LO}t]$$


Note again that these are **NOT** complex values—they are instead **real-valued** functions of **time**!

## The output of an IDEAL mixer

**Multiplying** these signals, we get (remember your trig identities!):

$$\begin{aligned}v_{IF}(t) &= v_{RF}(t) v_{LO}(t) \\&= \cos[\omega_{RF}t] \cos[\omega_{LO}t] \\&= \frac{1}{2}\cos[(\omega_{RF} - \omega_{LO})t] + \frac{1}{2}\cos[(\omega_{RF} + \omega_{LO})t]\end{aligned}$$

# New signals are created!

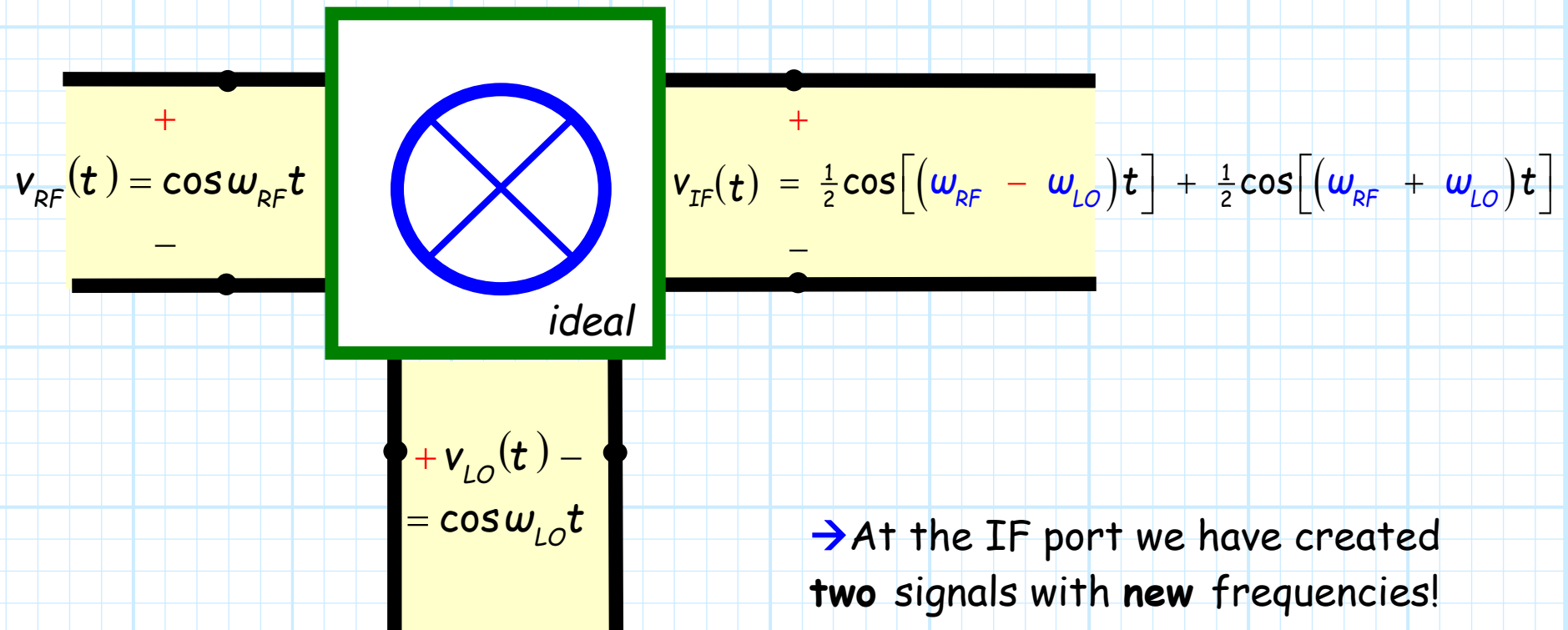

→ At the IF port we have created **two** signals with **new** frequencies!


# The IDEAL Mixer Output

**One** new signal has a frequency  $\omega_{\Delta}$ , that is the **difference** of the LO and RF signal frequencies:

$$\frac{1}{2} \cos[(\omega_{RF} - \omega_{LO})t] \doteq \frac{1}{2} \cos[\omega_{\Delta}t]$$

While the **other** new signal has a frequency  $\omega_{\Sigma}$ , that is the **sum** of the LO and RF signal frequencies:

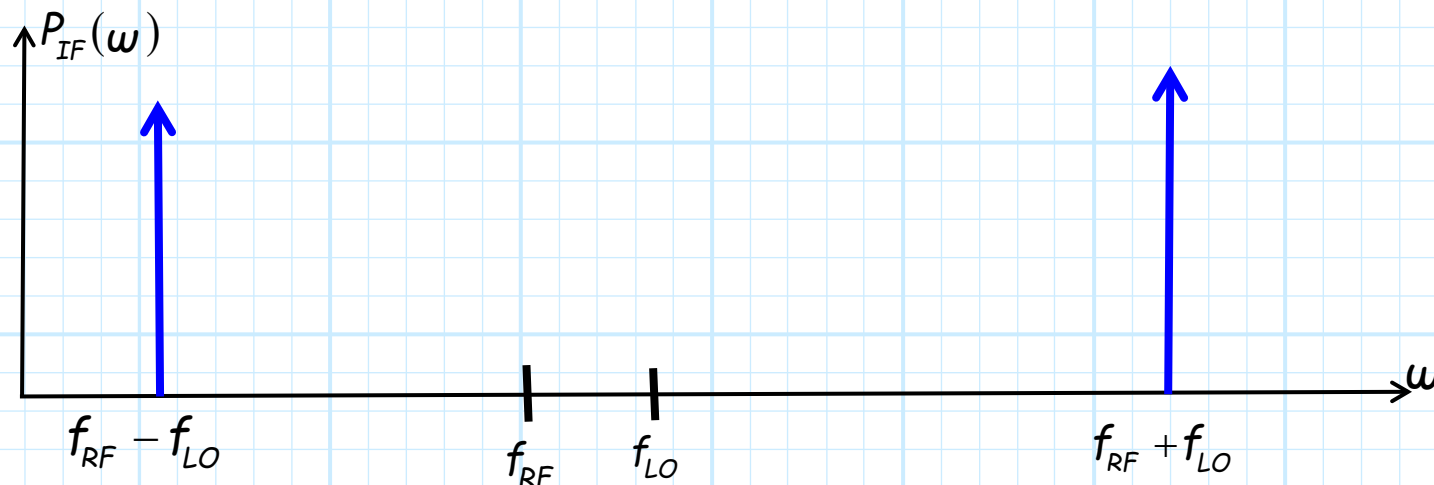
$$\frac{1}{2} \cos[(\omega_{RF} + \omega_{LO})t] \doteq \frac{1}{2} \cos[\omega_{\Sigma}t]$$





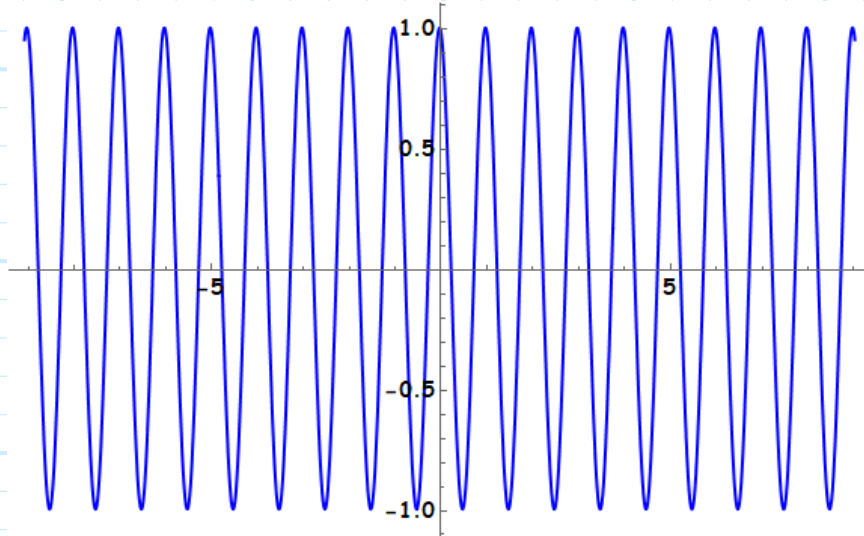
## An example...

For example, consider **this** sinusoid with frequency  $\omega_{LO} = 2.0\pi$ :



$$v_{LO}(t) = \cos(2.0\pi t)$$

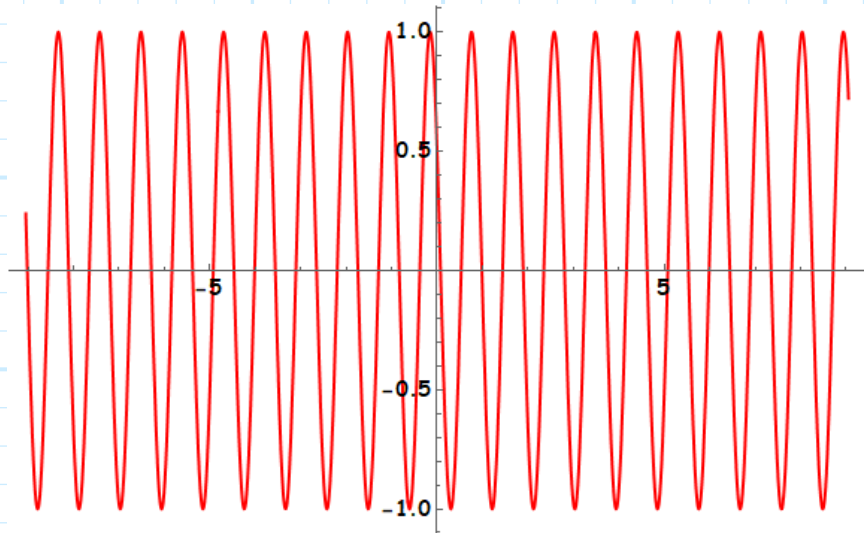Along with **this** sinusoid, with **higher** frequency  $\omega_{RF} = 2.2\pi$ :




$$v_{RF}(t) = \cos(2.2\pi t + \pi/3)$$
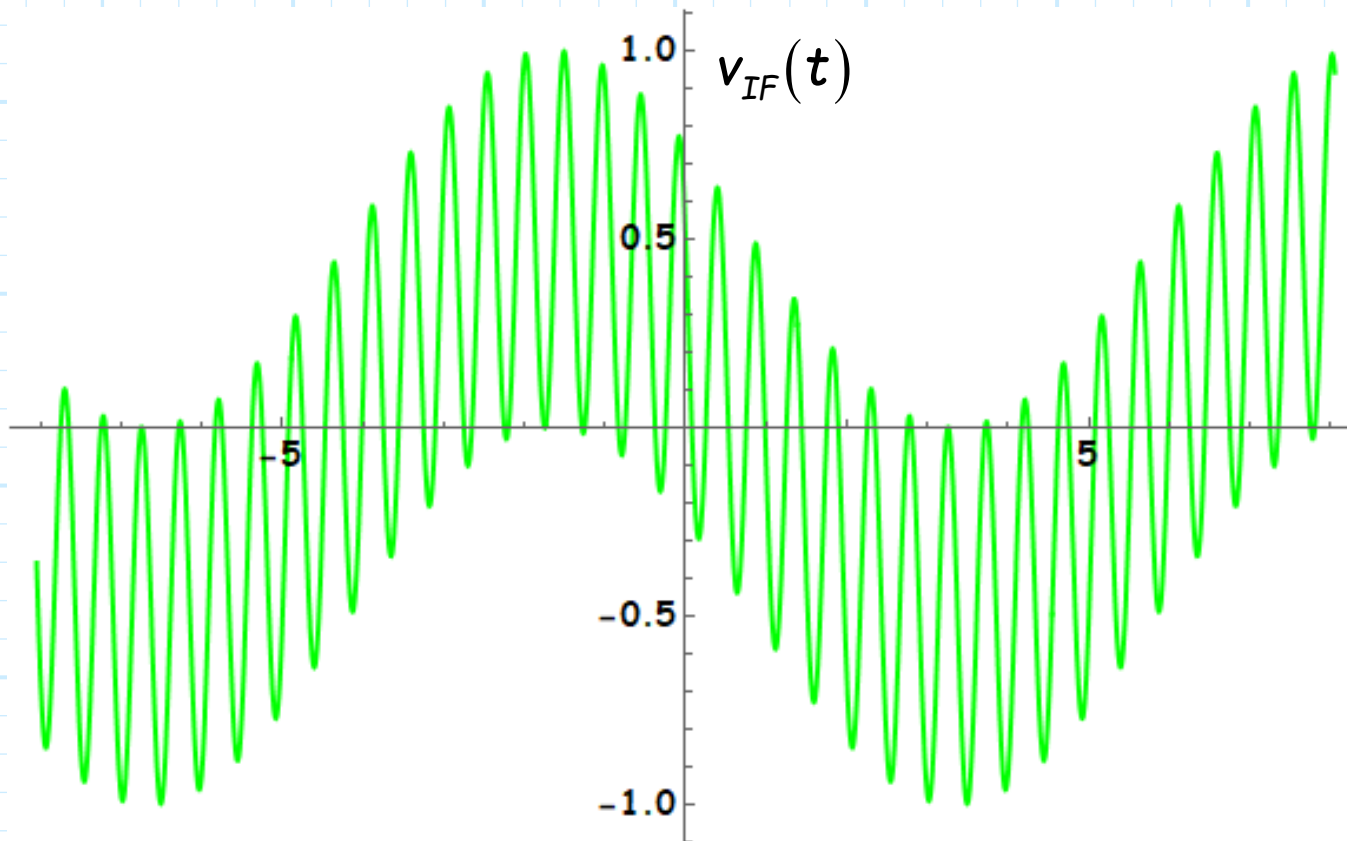
## The example output signal


**Multiplying** these two signals together, we get:

$$\begin{aligned}v_{IF}(t) &= v_{RF}(t)v_{LO}(t) \\&= \cos(2.2\pi t + \pi/3) \cos(2.0\pi t) \\&= \frac{1}{2}\cos(0.2\pi t + \pi/3) + \frac{1}{2}\cos(4.2\pi t + \pi/3)\end{aligned}$$


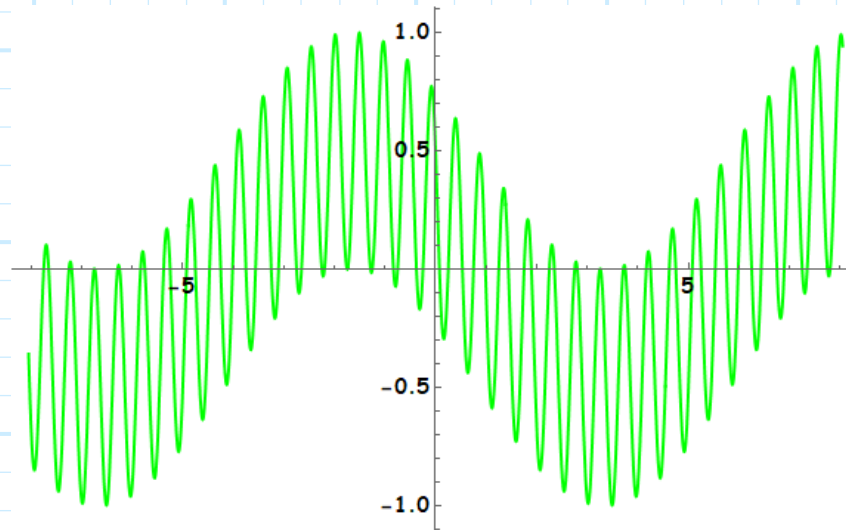
# Not the mess you think it is

**Q:** What a *mess*! I don't see *two sinusoids* in there at all!



**A:** Say we pass the above signal through a **bandpass filter**—one which **rejects the higher frequency signal**.

$$v_{IF}(t) = \frac{1}{2}\cos(0.2\pi t + \pi/3) + \frac{1}{2}\cos(4.2\pi t + \pi/3)$$

$$T(\omega = 0.2\pi) = 1.0$$


$$T(\omega = 4.2\pi) \cong 0.0$$

$$v_{IF}^{filtered}(t) \cong \frac{1}{2}\cos(0.2\pi t + \pi/3)$$
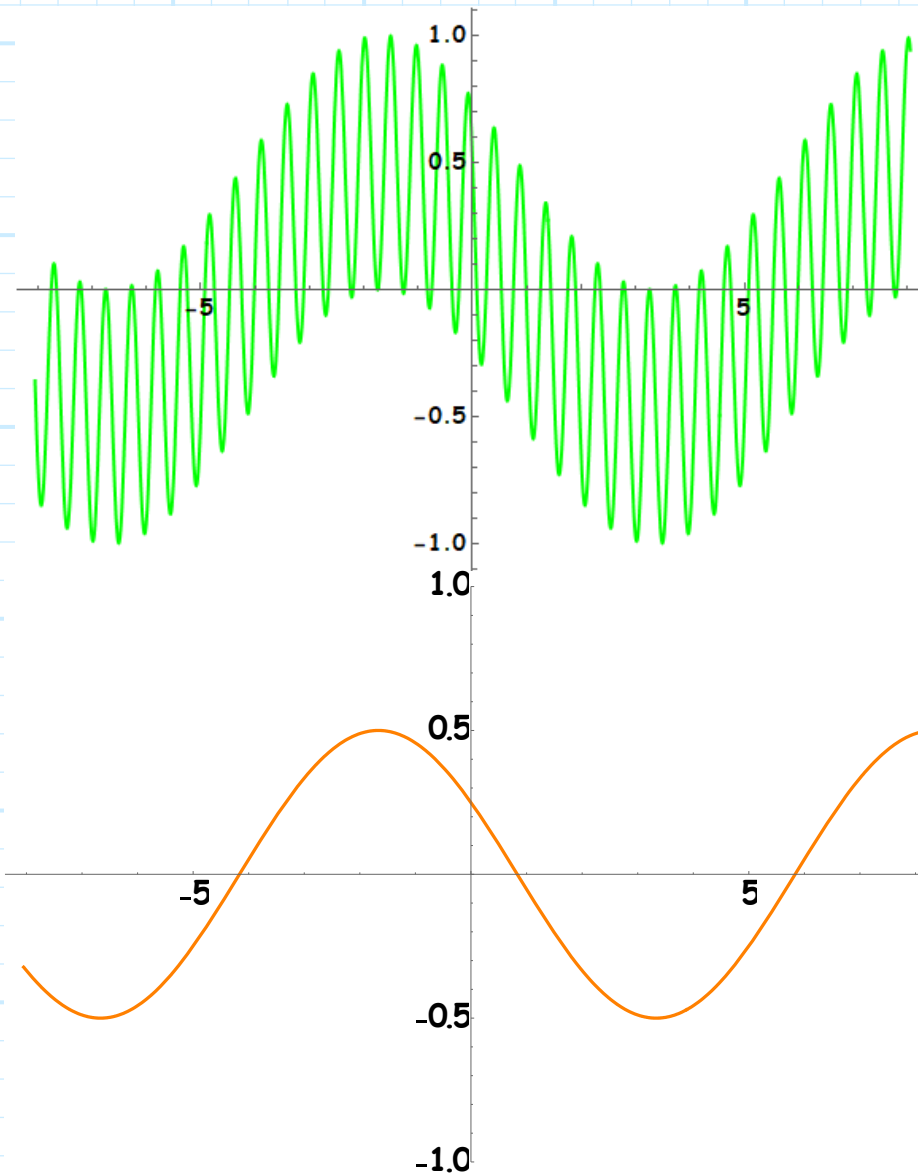
## A low-frequency component

The output of the **filter** is thus simply the **low-frequency component** of  $v_{IF}(t)$ .


$$v_{IF}(t) = \frac{1}{2}\cos(0.2\pi t + \pi/3) + \frac{1}{2}\cos(4.2\pi t + \pi/3)$$



$$v_{IF}^{filtered}(t) \cong \frac{1}{2}\cos(0.2\pi t + \pi/3)$$
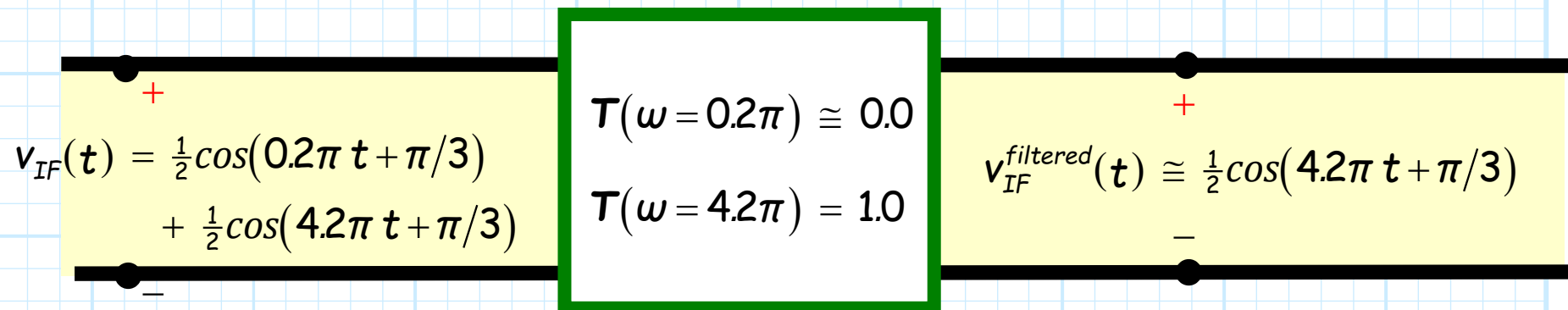
## Or, the high-frequency component


**Alternatively**, we could pass the signal  $v_{IF}(t)$  through a bandpass filter that rejects the **low-frequency** signal.




The output of the **filter** is thus simply the **high-frequency component** of  $v_{IF}(t)$ .
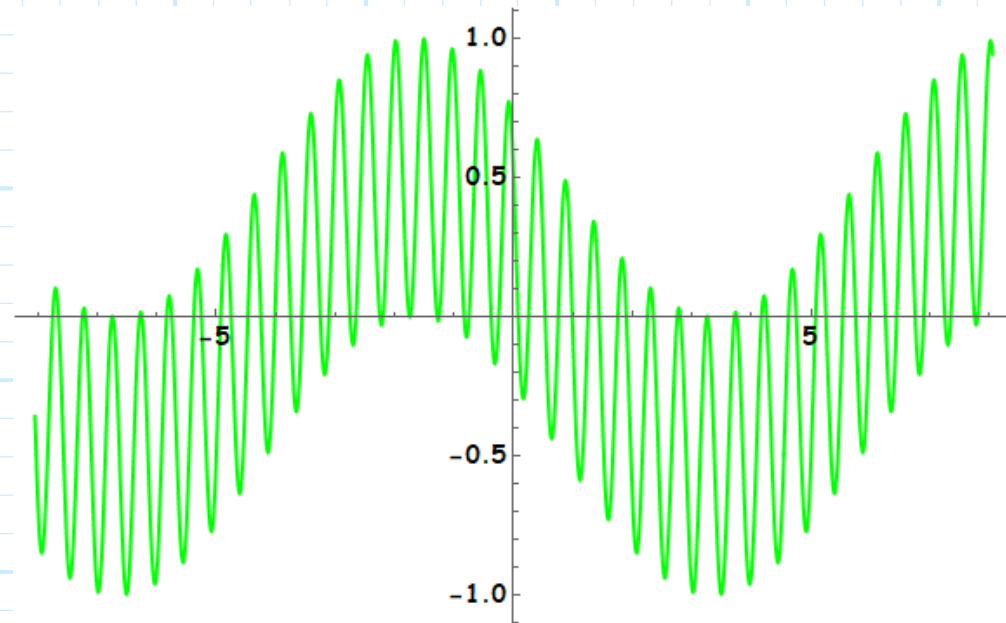
## For example...

$$v_{IF}(t) = \frac{1}{2}\cos(0.2\pi t + \pi/3) + \frac{1}{2}\cos(4.2\pi t + \pi/3)$$


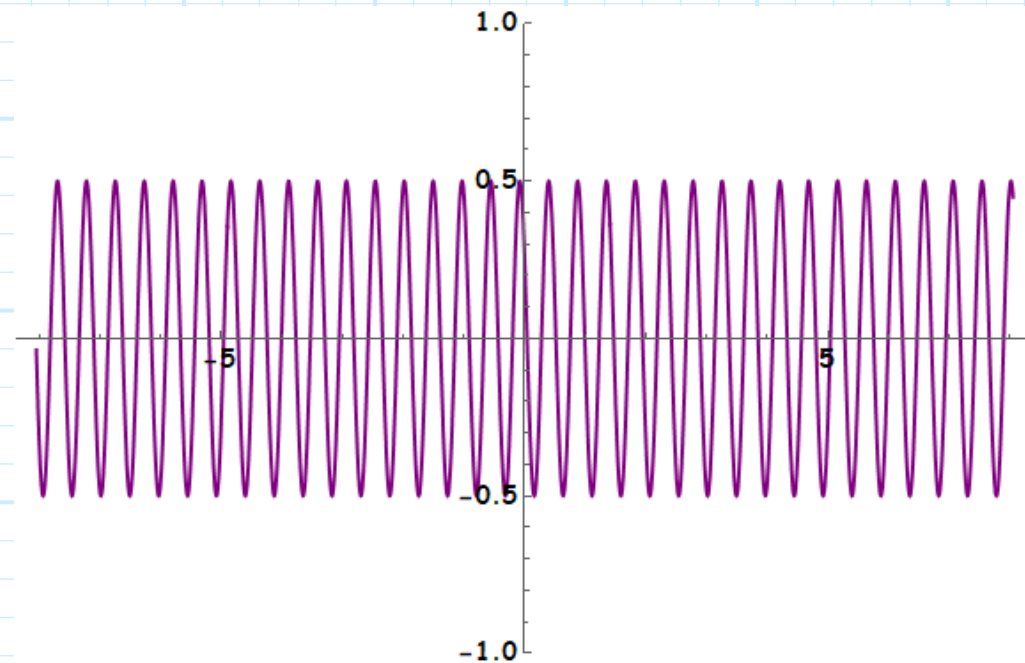
$$v_{IF}^{filtered}(t) \cong \frac{1}{2}\cos(4.2\pi t + \pi/3)$$



## These don't behave like eigen functions!

Q: Wait!

*You made a big, dramatic deal about **sinusoids** being “**eigen functions**”.*

*You said that a sinusoid with a frequency  $\omega$  at **one** place in a circuit would mean that **everywhere** in the circuit one would see the **same** sinusoid with the **exact same frequency**  $\omega$ .*

*But.*

*You now provide an **example** where the input frequencies are  $\omega = 2.0\pi$  and  $\omega = 2.2\pi$  —yet the output frequencies are a **remarkably different**  $\omega = 0.2\pi$  and  $\omega = 4.2\pi$ !*

*You must be **really confused** about this “eigen function” thing?*

# A mixer is NOT a linear device!

**A:** No confusion.


Sinusoids are the eigen functions of **ALL** linear, time-invariant circuits—but **ONLY** of linear, time-invariant circuits.

The mathematical operation:

$$V_{IF}(t) = V_{RF}(t) V_{LO}(t)$$

is decidedly **NON-linear**.

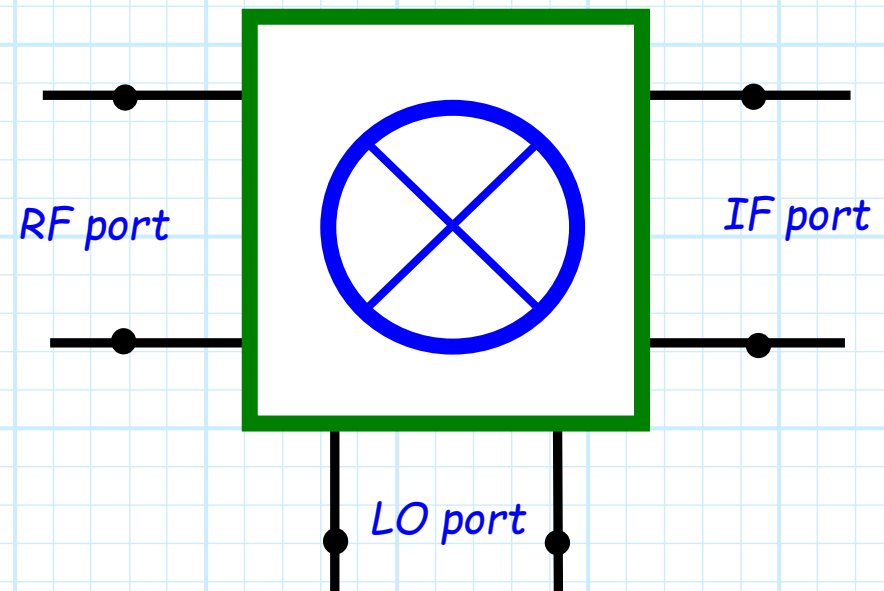This means that an **ideal mixer** is likewise a **non-linear circuit**—the **frequencies** of a sinusoid can thus be altered!





## A switch is a multiplier

**Q:** OK, so I'll return to my *first question*:

**a)** *how is this possible?*

**A:** Initially, it indeed appears the math associated with “**signal multiplication**”:

$$V_{IF}(t) = V_{RF}(t) V_{LO}(t)$$

is **inconsistent** with any electrical engineering **circuit element** (e.g., resistor, capacitors, inductors, transistors, diodes), **nor** with any **microwave** components that we have **previously studied**.


But, this **initial** appearance is **not** correct!

We in fact can achieve **signal multiplication** with the microwave device we just examined—the **microwave switch!**

**Q:** ?????

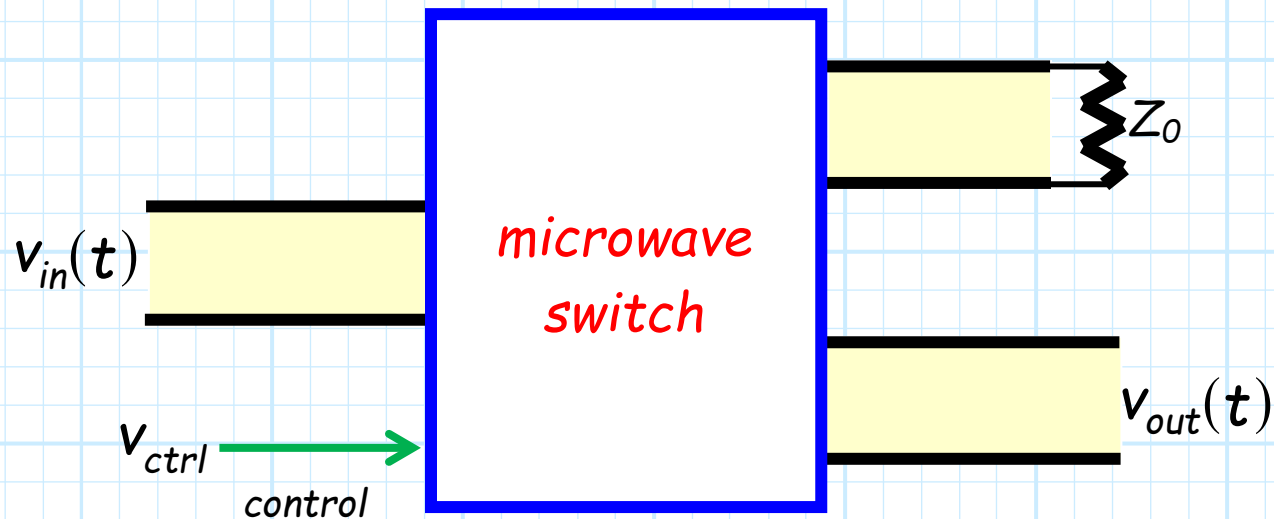
## Again, a microwave switch

**A:** Consider this **switch** with an **input** voltage  $v_{in}(t)$  and an **output** voltage  $v_{out}(t)$ :



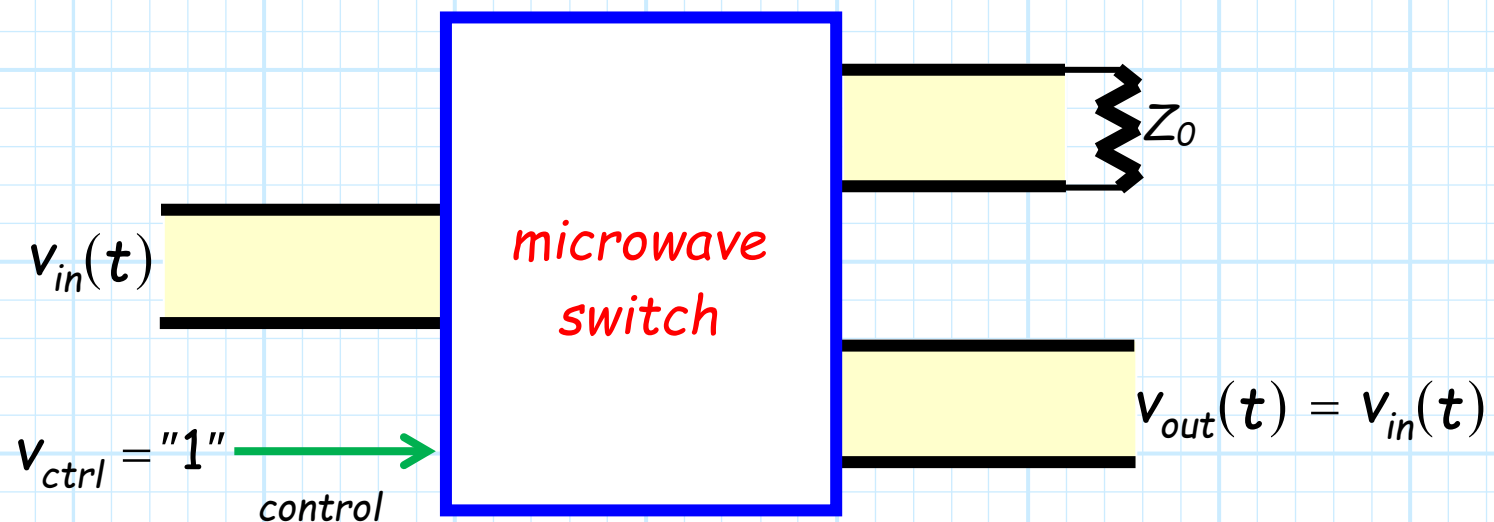
## This state: the output is equal to the input

For **one switch state**, the output voltage (at least ideally) is **equal** to the input voltage:


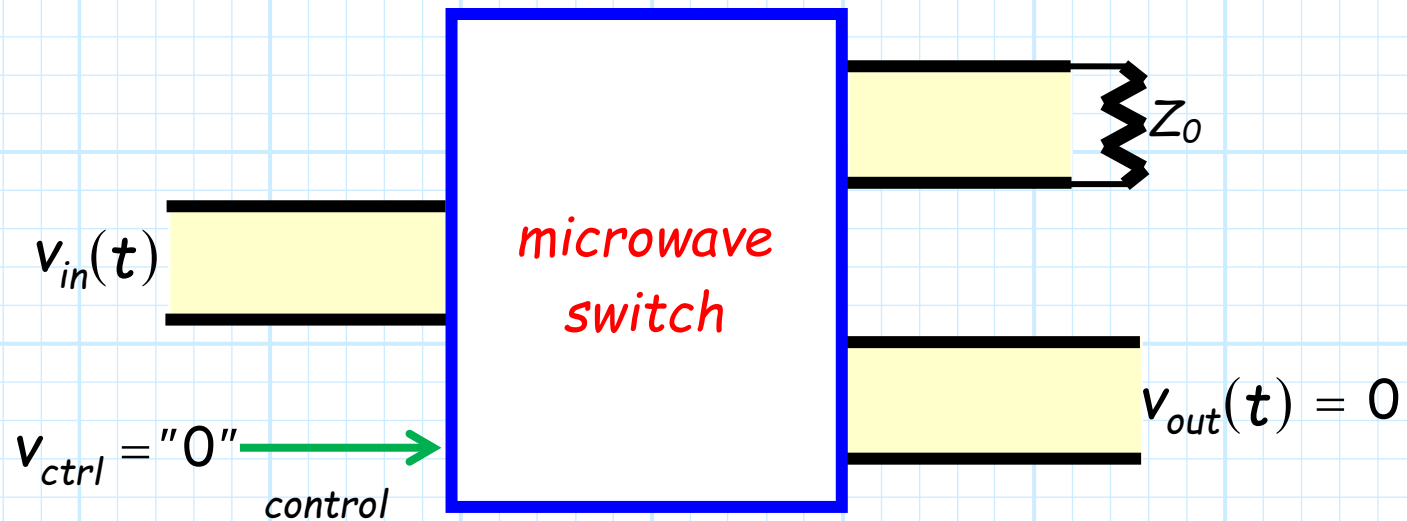
## This state: the output is equal to zero


While for the **other** state, the output voltage is **zero**:


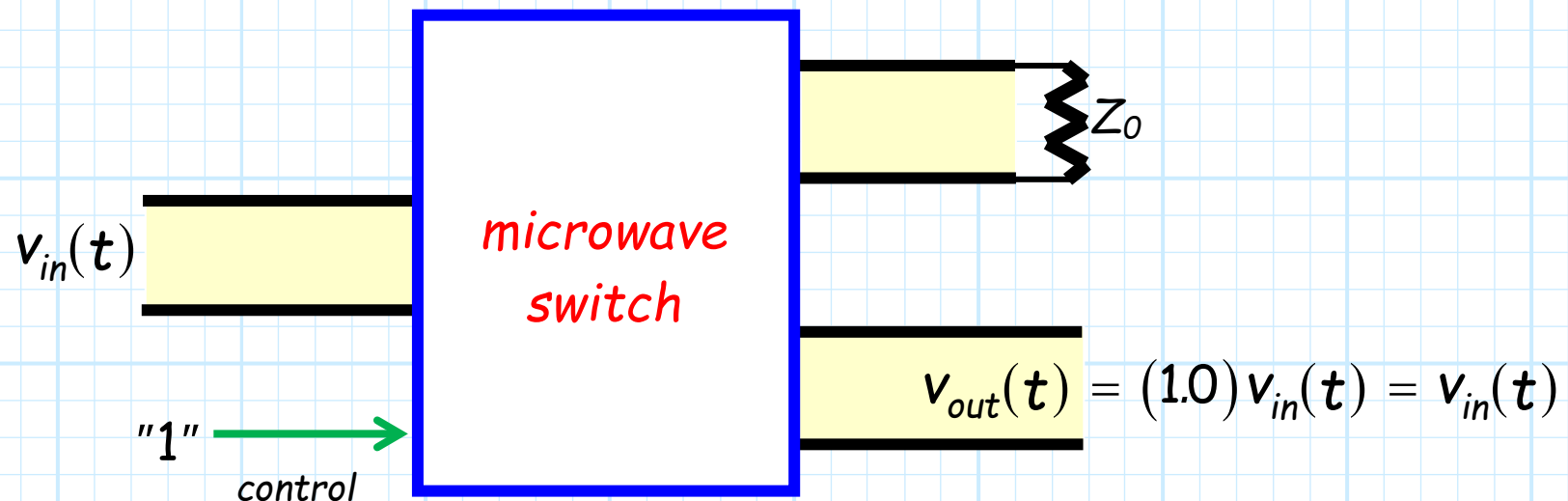
## It's like it multiplies by one...


Although we **know** these results are determined from the internal circuitry of the switch (e.g., diodes or transistors), we **could** interpret these results in **another way**.

We **could** argue that for one state, the switch **multiplies**  $v_{in}(t)$  with the value **1.0**:


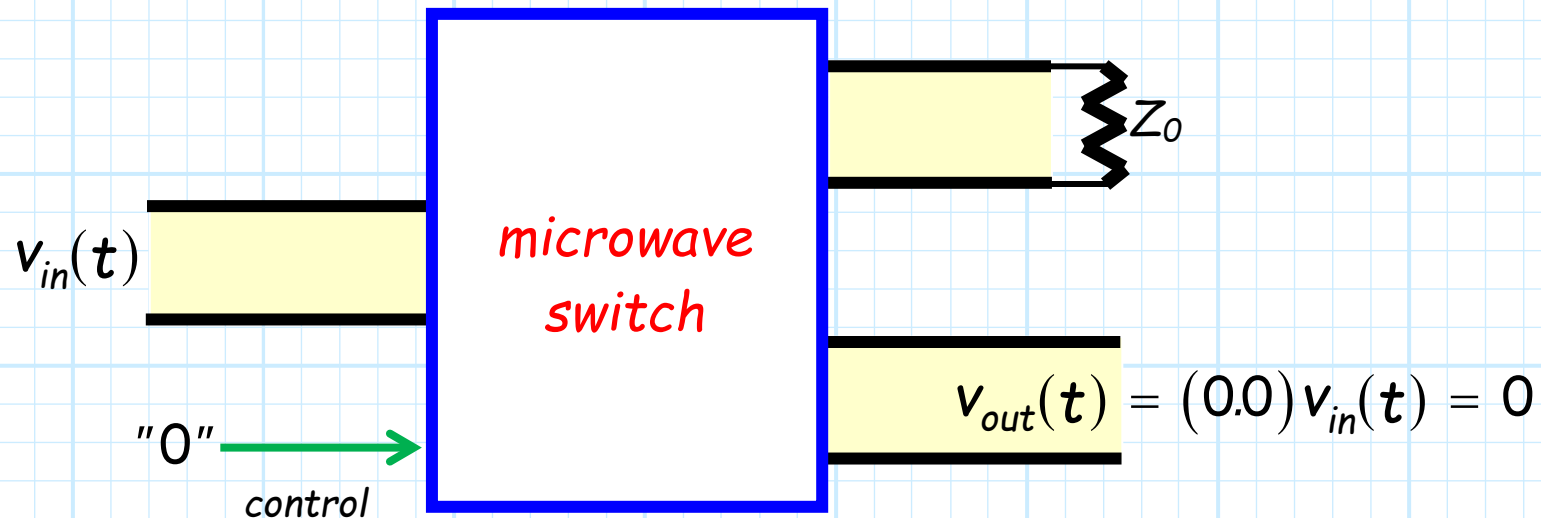
## ...or it multiplies by zero

While for the **other** state, the switch **multiplies**  $v_{in}(t)$  with the value 0.0:




## It's multiplied by a control voltage

Say now we define a **control** voltage  $v_{ctrl}$ , which can have **either one of two** states:

$$v_{ctrl} = 0.0 \quad \text{or} \quad v_{ctrl} = 1.0$$

we can write the switch output as:

$$v_{out}(t) = v_{ctrl} v_{in}(t)$$

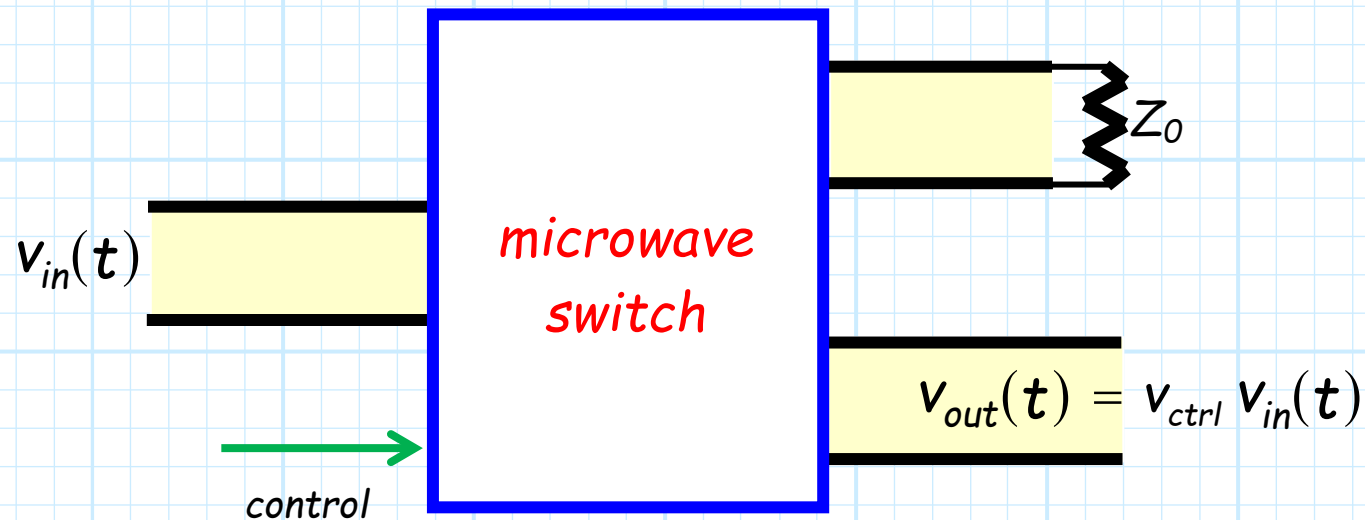


The switch appears to multiply voltages  $v_{ctrl}$  and  $v_{in}(t)$ !

## Toggle the control

**Q:** This "multiplier" seems quite *useless*; nothing at all like:

$$\begin{aligned} v_{IF}(t) &= \cos(2.2\pi t + \pi/3) \cos(2.0\pi t) \\ &= \frac{1}{2}\cos(0.2\pi t + \pi/3) + \frac{1}{2}\cos(4.2\pi t + \pi/3) \end{aligned}$$

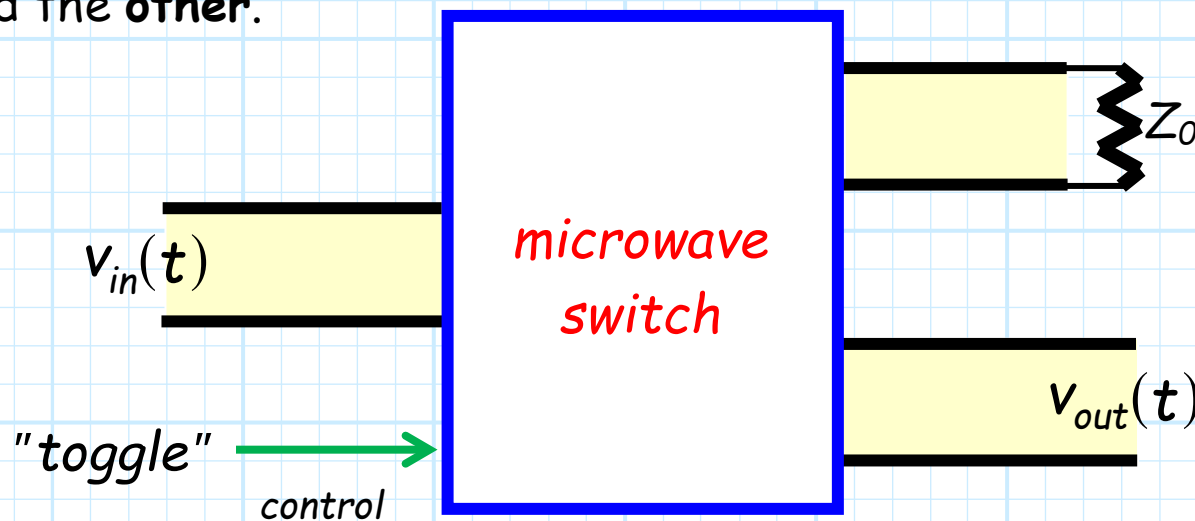**A:** But, say we continuously "toggle" the switch control, between one state and the other.




The output will thus also **toggle** between a value of  $v_{in}(t) = 0$  and  $v_{in}(t) = v_{out}(t)$ .


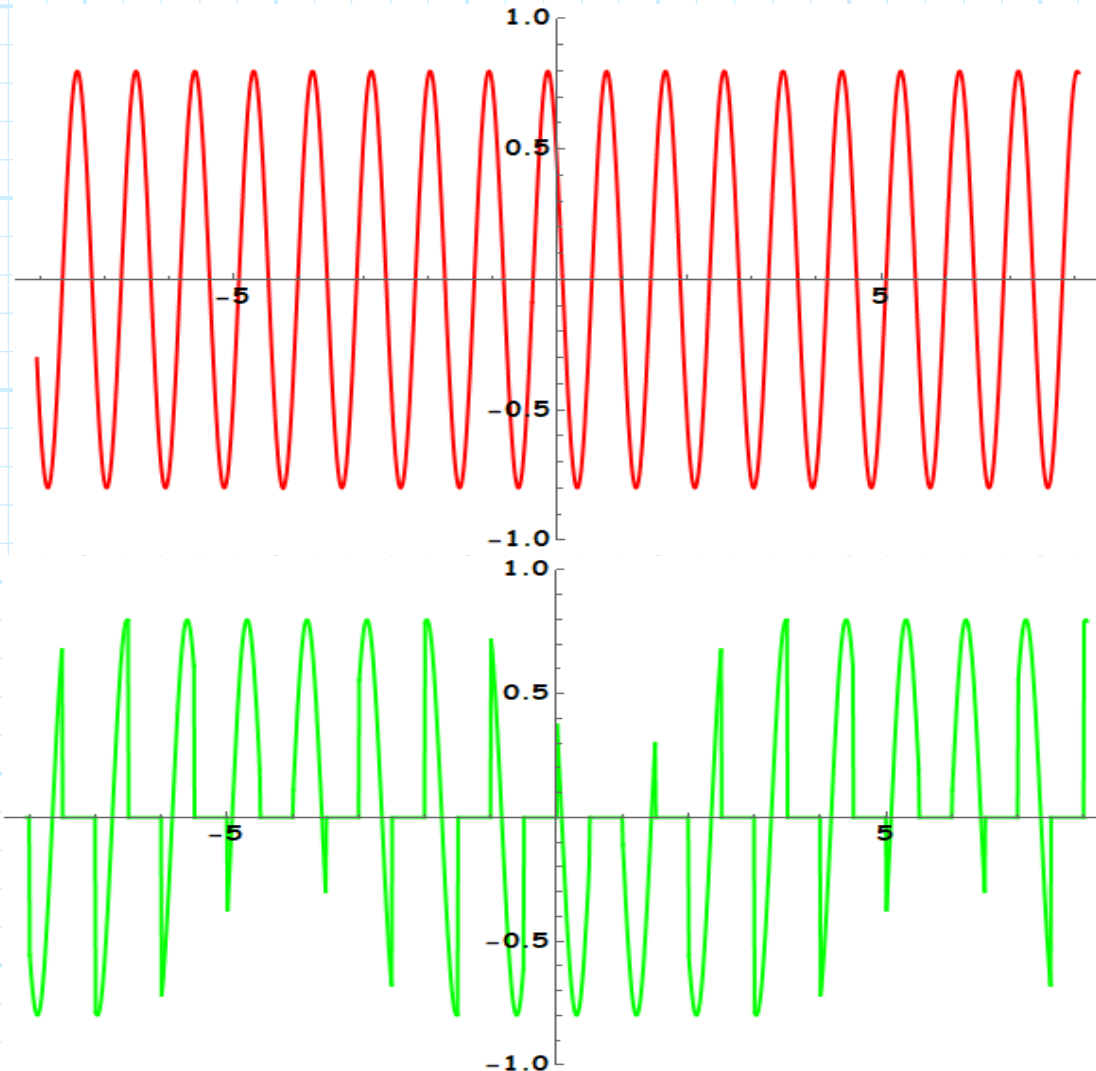
## We "chop" the input

Say also that we toggle at a **constant rate**, and with a **50% duty cycle**.  
The **output** will thus be a "**chopped**" version of the input:

$$v_{in}(t) = 0.8 \cos(2.2\pi t + \pi/3)$$




Q: ??????
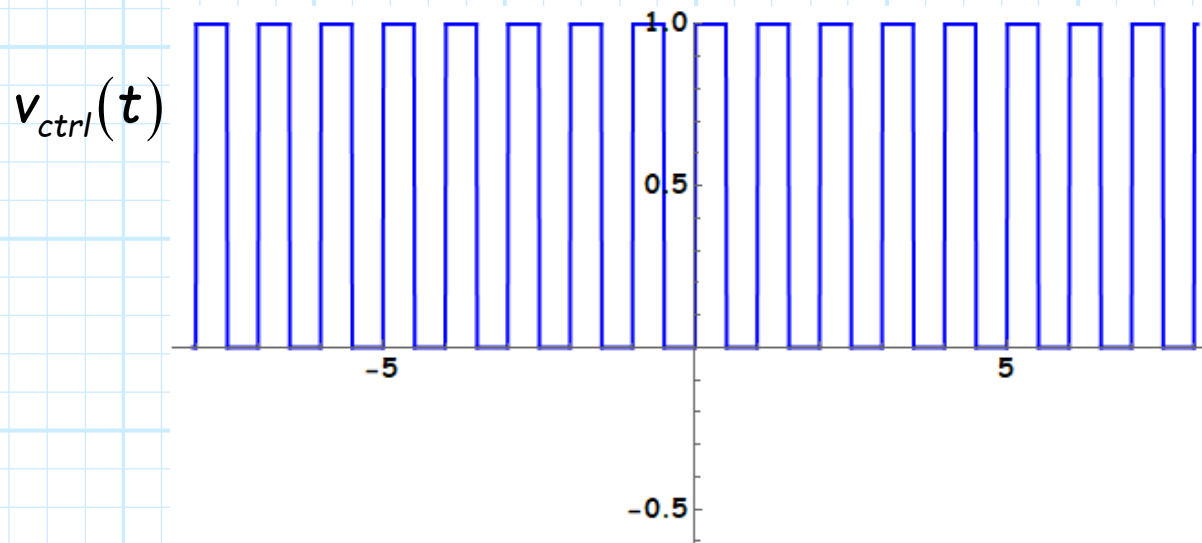
## "Chopping" is multiplying by a square wave

**A:** This "chopped" result can likewise be interpreted as multiplication!

The switch multiplies the **input** voltage  $v_{in}(t)$  with a **control voltage**  $v_{ctrl}$  —a control voltage that **toggles** between a value of  $v_{ctrl}=0.0$  and  $v_{ctrl}=1.0$ !



The control voltage is a "square wave"!


## One signal must be a square wave

Thus, a **microwave switch** can be used as a device that **multiplies** some arbitrary **input** signal  $v_{in}(t)$  with some arbitrary **square wave**  $v_{ctrl}(t)$ !

**Q:** *I don't understand.*


*You said a mixer can be used to multiply two sinusoids, giving the quite useful output:*
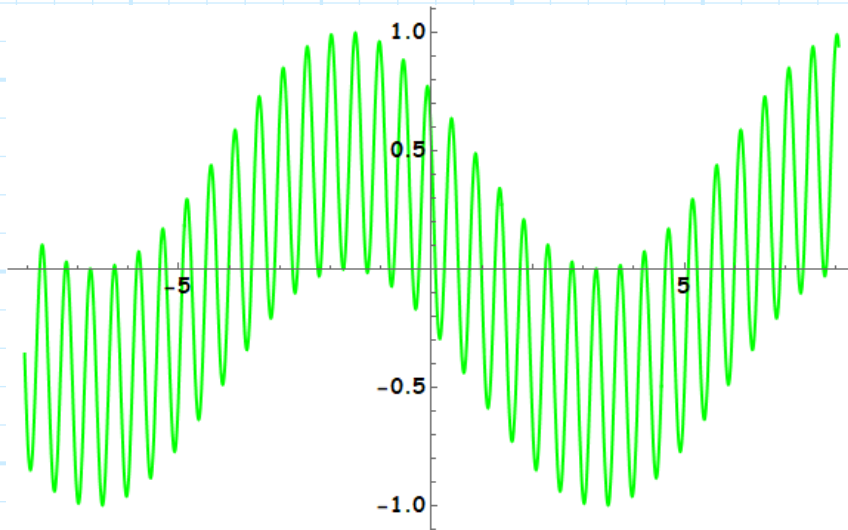
$$\begin{aligned}
 v_{IF}(t) &= v_{RF}(t) v_{LO}(t) \\
 &= \cos(2.2\pi t + \pi/3) \cos(2.0\pi t) \\
 &= \frac{1}{2} \cos(0.2\pi t + \pi/3) + \frac{1}{2} \cos(4.2\pi t + \pi/3)
 \end{aligned}$$


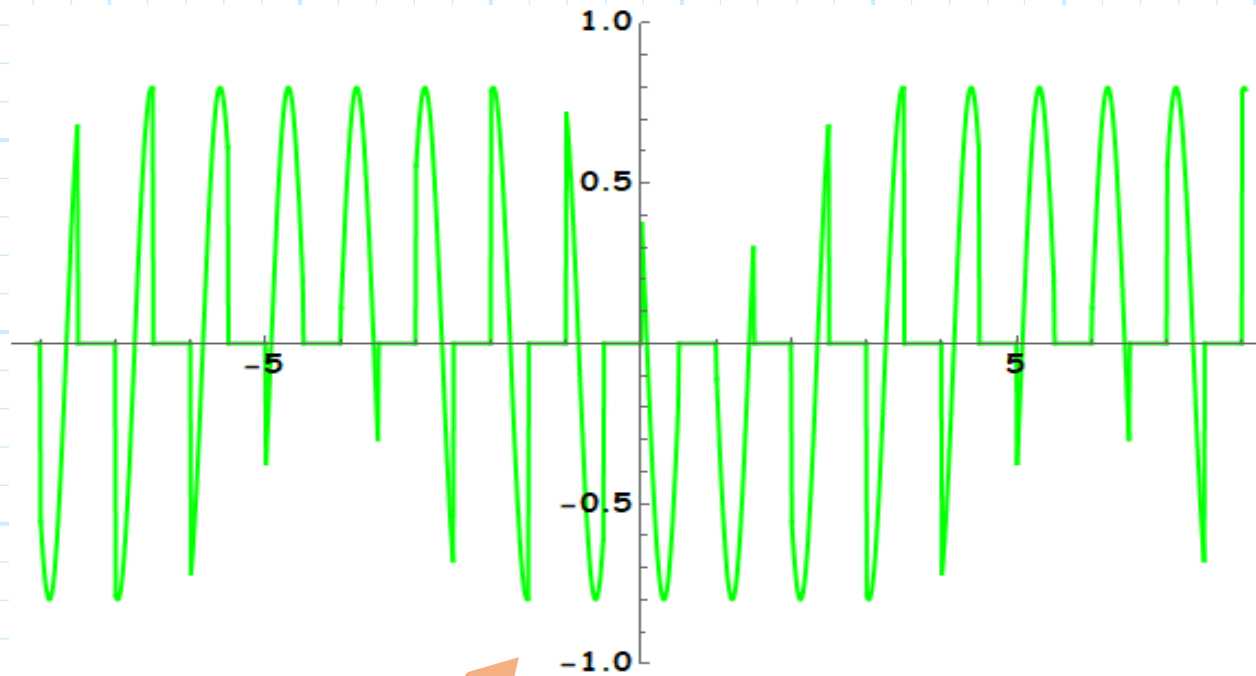
## Apparently, both ugly and useless

But, this switch “multiplier” can *only* multiply a sinusoid and a square wave, giving a result *both ugly and apparently useless*:



**A:** But **this** result is **not** useless!

## As usual, the Fourier transform reveals all

The **usefulness** of this **switch multiplier output** is **revealed** by examining it in the **frequency domain**—i.e., by evaluating its **Fourier Transform**:

$$V_{out}(\omega) = \int_{-\infty}^{\infty} v_{out}(t) e^{+j\omega t} dt = \int_{-\infty}^{\infty} v_{in}(t) v_{ctrl}(t) e^{+j\omega t} dt$$

**Q:** *I'm slightly embarrassed to admit that I'm not really sure how to evaluate this integral.*

**A:** **YOU** of course recall that:

the Fourier Transform of the **product of two functions** is simply the **convolution** of the **Fourier Transform** of each separate function!

# Trust me, it makes things WAY easier

In other "words", for our **multiplier**:

$$V_{out}(\omega) = V_{in}(\omega) * V_{ctrl}(\omega)$$

where:

$$V_{in}(\omega) = \int_{-\infty}^{\infty} v_{in}(t) e^{+j\omega t} dt \quad \text{and} \quad V_{ctrl}(\omega) = \int_{-\infty}^{\infty} v_{ctrl}(t) e^{+j\omega t} dt$$

This makes things **much easier**.

**Q:** *Umm...it appears to me to instead to make things much more difficult.*

**A:** Not for **this** problem! (You can skip ahead to page 50 if you **want**).

## Consider arbitrary sinusoid at the input

Consider an **arbitrary sinusoidal** input function of the form:

$$v_{in}(t) = A_{in} \cos(\omega_{in} t + \varphi_{in})$$

From **Euler's identity**, this input can be expressed as:



$$\begin{aligned} v_{in}(t) &= A_{in} \cos(\omega_{in} t + \varphi_{in}) \\ &= \frac{1}{2} A_{in} \left( e^{+j(\omega_{in} t + \varphi_{in})} + e^{-j(\omega_{in} t + \varphi_{in})} \right) \\ &= \frac{1}{2} A_{in} e^{+j\varphi_{in}} e^{+j\omega_{in} t} + \frac{1}{2} A_{in} e^{-j\varphi_{in}} e^{-j\omega_{in} t} \end{aligned}$$

# Impulse functions—make sure you understand them!


The **Fourier Transform** of this arbitrary sinusoid is thus:

$$\begin{aligned}
 V_{in}(\omega) &= \int_{-\infty}^{\infty} v_{in}(t) e^{+j\omega t} dt \\
 &= \int_{-\infty}^{\infty} \left( \frac{1}{2} A_{in} e^{+j\varphi_{in}} e^{+j\omega_{in}t} + \frac{1}{2} A_{in} e^{-j\varphi_{in}} e^{-j\omega_{in}t} \right) e^{+j\omega t} dt \\
 &= \frac{1}{2} A_{in} e^{+j\varphi_{in}} \int_{-\infty}^{\infty} e^{+j(\omega + \omega_{in})t} dt + \frac{1}{2} A_{in} e^{-j\varphi_{in}} \int_{-\infty}^{\infty} e^{+j(\omega - \omega_{in})t} dt \\
 &= \frac{1}{2} A_{in} e^{-j\varphi_{in}} 2\pi \delta(\omega + \omega_{in}) + \frac{1}{2} A_{in} e^{+j\varphi_{in}} 2\pi \delta(\omega - \omega_{in}) \\
 &= \pi A_{in} e^{-j\varphi_{in}} \delta(\omega + \omega_{in}) + \pi A_{in} e^{+j\varphi_{in}} \delta(\omega - \omega_{in})
 \end{aligned}$$


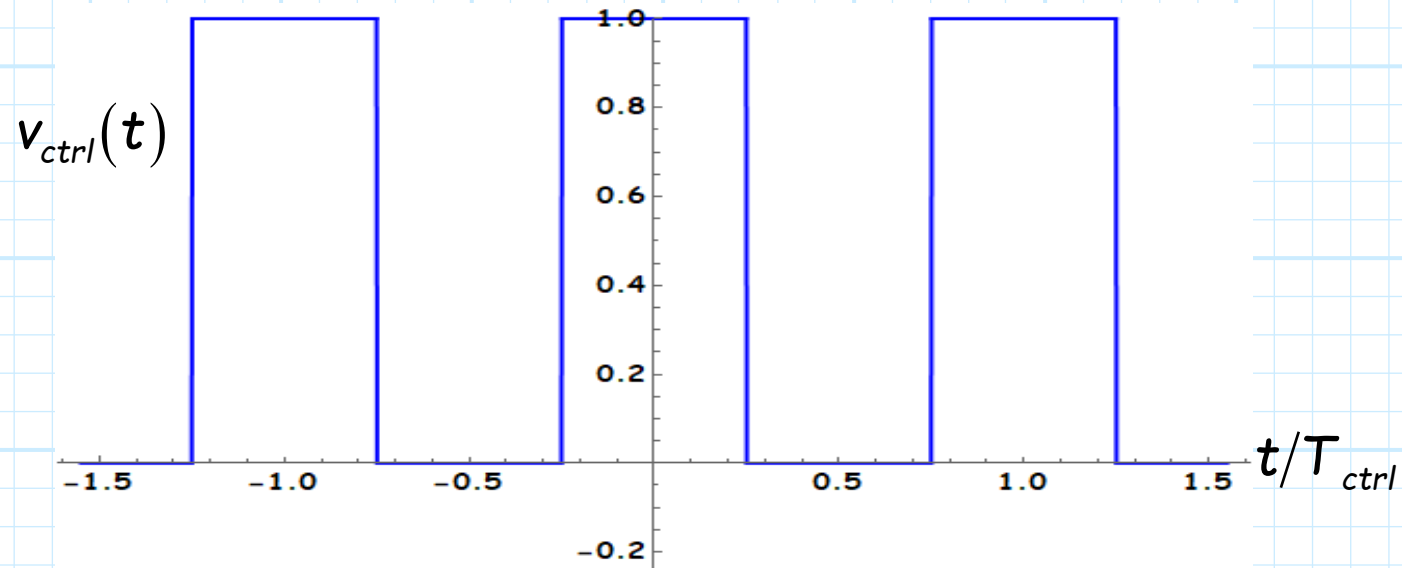
## A periodic square wave

Now the **square-wave** control voltage, which is **periodic** with time  $T_{ctrl}$ :



**Mathematically**, this is described as:

$$v_{LO}(t) = \begin{cases} 0 & (n - \frac{1}{2})T_{ctrl} < t < (n - \frac{1}{4})T_{ctrl} \\ 1 & (n - \frac{1}{4})T_{ctrl} < t < (n + \frac{1}{4})T_{ctrl} \\ 0 & (n + \frac{1}{4})T_{ctrl} < t < (n + \frac{1}{2})T_{ctrl} \end{cases}$$

where  $n$  is any arbitrary **integer**.

## Its Fourier transform

The Fourier transform of this square-wave is therefore:

$$\begin{aligned}
 V_{ctrl}(\omega) &= \int_{-\infty}^{\infty} v_{ctrl}(t) e^{+j\omega t} dt \\
 &= \sum_n \left( \int_{(n-\frac{1}{2})T_{ctrl}}^{(n-\frac{1}{4})T_{ctrl}} 0 e^{+j\omega t} dt + \int_{(n-\frac{1}{4})T_{ctrl}}^{(n+\frac{1}{4})T_{ctrl}} 1 e^{+j\omega t} dt + \int_{(n+\frac{1}{4})T_{ctrl}}^{(n+\frac{1}{2})T_{ctrl}} 0 e^{+j\omega t} dt \right) \\
 &= \sum_n \int_{(n-\frac{1}{4})T_{ctrl}}^{(n+\frac{1}{4})T_{ctrl}} e^{+j\omega t} dt
 \end{aligned}$$

## Evaluating that integral

Evaluating the **integral** of this last result:

$$\begin{aligned}
 \int_{(n-\frac{1}{4})T_{ctrl}}^{(n+\frac{1}{4})T_{ctrl}} e^{+j\omega t} dt &= \frac{1}{j\omega} e^{+j\omega t} \Big|_{(n-\frac{1}{4})T_{ctrl}}^{(n+\frac{1}{4})T_{ctrl}} \\
 &= \frac{1}{j\omega} \left( e^{+j\omega(n+\frac{1}{4})T_{ctrl}} - e^{+j\omega(n-\frac{1}{4})T_{ctrl}} \right) \\
 &= \frac{e^{+jn\omega T_{ctrl}}}{j\omega} \left( e^{+j\omega T_{ctrl}/4} - e^{-j\omega T_{ctrl}/4} \right) \\
 &= \frac{e^{+jn\omega T_{ctrl}}}{j\omega} \left( j2 \sin[\omega T_{ctrl}/4] \right) \\
 &= \frac{T_{ctrl}}{2} \left( \frac{\sin[\omega T_{ctrl}/4]}{\omega T_{ctrl}/4} \right) e^{+jn\omega T_{ctrl}}
 \end{aligned}$$

# I'm kinda embarrassed

And so the **Fourier transform** of the **square wave** is:

$$\begin{aligned}
 V_{ctrl}(\omega) &= \int_{-\infty}^{\infty} v_{ctrl}(t) e^{+j\omega t} dt \\
 &= \sum_n \int_{(n-1/4)T_{ctrl}}^{(n+1/4)T_{ctrl}} e^{+j\omega t} dt \\
 &= \sum_n \frac{T_{ctrl}}{2} \left( \frac{\sin[\omega T_{ctrl}/4]}{\omega T_{ctrl}/4} \right) e^{+jn\omega T_{ctrl}} \\
 &= \frac{T_{ctrl}}{2} \left( \frac{\sin[\omega T_{ctrl}/4]}{\omega T_{ctrl}/4} \right) \sum_n e^{+jn\omega T_{ctrl}}
 \end{aligned}$$

The **summation** can be shown (hand-waving time!) to be:



$$\sum_{n=-\infty}^{\infty} e^{+jn\omega T_{ctrl}} = \frac{1}{T_{ctrl}} \sum_{n=-\infty}^{\infty} \delta\left(\omega - n\left(\frac{2\pi}{T_{ctrl}}\right)\right)$$

## The result

Defining:

$$f_{ctrl} \doteq \frac{1}{T_{ctrl}} \quad \text{and} \quad \omega_{ctrl} \doteq 2\pi f_{ctrl} = \frac{2\pi}{T_{ctrl}}$$

this summation is then:

$$\sum_n e^{+jn\omega T_{ctrl}} = \frac{1}{T_{ctrl}} \sum_n \delta\left(\omega - n\left(\frac{2\pi}{T_{ctrl}}\right)\right) = \frac{1}{T_{ctrl}} \sum_n \delta(\omega - n\omega_{ctrl})$$

And so finally:

$$\begin{aligned} V_{ctrl}(\omega) &= \int_{-\infty}^{\infty} v_{ctrl}(t) e^{+j\omega t} dt \\ &= \frac{T_{ctrl}}{2} \left( \frac{\sin[\omega T_{ctrl}/4]}{\omega T_{ctrl}/4} \right) \sum_n e^{+jn\omega T_{ctrl}} \\ &= \frac{1}{2} \left( \frac{\sin[\omega T_{ctrl}/4]}{\omega T_{ctrl}/4} \right) \sum_n \delta(\omega - n\omega_{ctrl}) \end{aligned}$$

## In summary

So, we have determined the Fourier transform of the **input sinusoid**:

$$V_{in}(\omega) = \pi A_{in} e^{-j\varphi_{in}} \delta(\omega + \omega_{in}) + \pi A_{in} e^{+j\varphi_{in}} \delta(\omega - \omega_{in})$$

And also for the **control square wave**:

$$V_{ctrl}(\omega) = \frac{1}{2} \left( \frac{\sin[\omega T_{ctrl}/4]}{\omega T_{ctrl}/4} \right) \sum_n \delta(\omega - n\omega_{ctrl})$$

## Not as difficult as it looks

The Fourier transform of the **output** signal  $v_{out}(t) = v_{in}(t)v_{ctrl}(t)$  is therefore the **convolution** of these two spectra:

$$\begin{aligned} V_{out}(\omega) &= \int_{-\infty}^{\infty} v_{out}(t) e^{+j\omega t} dt \\ &= V_{in}(\omega) * V_{ctrl}(\omega) \\ &= \int_{-\infty}^{\infty} V_{in}(\omega - \omega') V_{ctrl}(\omega') d\omega' \end{aligned}$$

**Q:** *I thought you said this would be **easy**?*

**A:** It is easy!

# The Dirac delta function!

$$\begin{aligned}
 V_{out}(\omega) &= \int_{-\infty}^{\infty} V_{in}(\omega - \omega') V_{ctrl}(\omega') d\omega' \\
 &= \int_{-\infty}^{\infty} \pi V_{in} e^{-j\varphi} \delta(\omega - \omega' - \omega_{in}) \sum_n \frac{1}{2} \left( \frac{\sin[\omega' T_{ctrl}/4]}{\omega' T_{ctrl}/4} \right) \delta(\omega' - n\omega_{ctrl}) d\omega' \\
 &\quad + \int_{-\infty}^{\infty} \pi V_{in} e^{+j\varphi} \delta(\omega - \omega' + \omega_{in}) \sum_n \frac{1}{2} \left( \frac{\sin[\omega' T_{ctrl}/4]}{\omega' T_{ctrl}/4} \right) \delta(\omega' - n\omega_{ctrl}) d\omega' \\
 &= V_{in} e^{-j\varphi} \frac{\pi}{2} \sum_n \int_{-\infty}^{\infty} \delta(\omega - \omega' - \omega_{in}) \left( \frac{\sin[\omega' T_{ctrl}/4]}{\omega' T_{ctrl}/4} \right) \delta(\omega' - n\omega_{ctrl}) d\omega' \\
 &\quad + V_{in} e^{+j\varphi} \frac{\pi}{2} \sum_n \int_{-\infty}^{\infty} \delta(\omega - \omega' + \omega_{in}) \left( \frac{\sin[\omega' T_{ctrl}/4]}{\omega' T_{ctrl}/4} \right) \delta(\omega' - n\omega_{ctrl}) d\omega'
 \end{aligned}$$

**Q:** *I'm still not seeing easy anywhere.*

**A:** Look closely at the **integrals**—they involve **Dirac delta function**  $\delta(x)$ !




## As a professor once said to me

And, integrating with the Dirac delta function is “joy itself”!

Recall that:
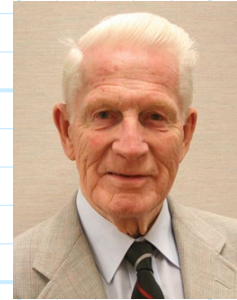
$$\int_{-\infty}^{\infty} f(x) \delta(x) dx = f(x=0)$$



In other words, we evaluate the **integral** simply by evaluating the **function**  $f(x)$  at  $x=0$  (the result  $f(x=0)$  is thus a **number**).

A corollary to this result is the “**sampling integral**”:

$$\int_{-\infty}^{\infty} f(x) \delta(x-c) dx = f(x=c)$$

The integral returns the value of function  $f(x)$ , evaluated at some **arbitrary** value  $x=c$  (e.g.,  $x=2.7$ ).

# Cake simple

Happily, our integrals involve the Dirac delta function:

$$\delta(\omega' - n\omega_{ctrl})$$

Thus, we **simply** evaluate the remainder of the integrand at  $\omega' = n\omega_{ctrl}$ :

$$\begin{aligned} & \int_{-\infty}^{\infty} \delta(\omega - \omega' - \omega_{in}) \left( \frac{\sin[\omega' T_{ctrl}/4]}{\omega' T_{ctrl}/4} \right) \delta(\omega' - n\omega_{ctrl}) d\omega' \\ &= \delta(\omega - n\omega_{ctrl} - \omega_{in}) \left( \frac{\sin[n\omega_{ctrl} T_{ctrl}/4]}{n\omega_{ctrl} T_{ctrl}/4} \right) \end{aligned}$$



## Wait! It gets even better!

And so:

$$V_{out}(\omega) = V_{in} e^{-j\phi} \frac{\pi}{2} \sum_n \delta(\omega - n\omega_{ctrl} - \omega_{in}) \left( \frac{\sin[n\omega_{ctrl} T_{ctrl}/4]}{n\omega_{ctrl} T_{ctrl}/4} \right) \\ + V_{in} e^{+j\phi} \frac{\pi}{2} \sum_n \delta(\omega - n\omega_{ctrl} + \omega_{in}) \left( \frac{\sin[n\omega_{ctrl} T_{ctrl}/4]}{n\omega_{ctrl} T_{ctrl}/4} \right)$$

Now, recalling that:

$$\omega_{ctrl} \doteq 2\pi f_{ctrl} = \frac{2\pi}{T_{ctrl}}$$

So that:

$$n\omega_{ctrl} T_{ctrl} = n2\pi$$

# Simple

We can express:

$$\frac{\sin[n\omega_{ctrl} T_{ctrl}/4]}{n\omega_{ctrl} T_{ctrl}/4} = \frac{\sin[n2\pi/4]}{n2\pi/4 n\omega_{ctrl}} = \frac{\sin[n(\pi/2)]}{n(\pi/2)}$$

So that finally:

$$\begin{aligned} V_{out}(\omega) = & V_{in} e^{-j\varphi} \frac{\pi}{2} \sum_n \delta(\omega - n\omega_{ctrl} - \omega_{in}) \frac{\sin[n(\pi/2)]}{n(\pi/2)} \\ & + V_{in} e^{+j\varphi} \frac{\pi}{2} \sum_n \delta(\omega - n\omega_{ctrl} + \omega_{in}) \frac{\sin[n(\pi/2)]}{n(\pi/2)} \end{aligned}$$

## Even values result in zero

Evaluating over different integers  $n$ :

$n$	$\frac{\sin[n(\pi/2)]}{n(\pi/2)}$
-4	0
-3	$2/(3\pi)$
-2	0
-1	$2/\pi$
0	1.0
+1	$2/\pi$
+2	0
+3	$2/(3\pi)$
+4	0

## Even simpler

It is apparent that all (non-zero) **even** values of integer  $n$  result in a **zero** value, and that odd values of  $n$  result in  $(2/|n|\pi)$ .

Therefore:

$$V_{out}(\omega) = V_{in}e^{-j\varphi} \frac{\pi}{2} \left( \delta(\omega - \omega_{in}) + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} \delta(\omega - n\omega_{ctrl} - \omega_{in}) \right) \\ + V_{in}e^{+j\varphi} \frac{\pi}{2} \left( \delta(\omega + \omega_{in}) + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} \delta(\omega - n\omega_{ctrl} + \omega_{in}) \right)$$

## Rearrange the delta functions

**Q:** *I'm not sure I understand what those Dirac delta functions mean.*

**A:** Remember, the value of  $\delta(x)$  is zero at all  $x \neq 0$ .

Thus, the Dirac delta functions in the above Fourier transform indicate **zero** energy for all frequencies—**except** those **specific few** which make the argument of the delta function **zero**!

**Q:** *Just what "specific few" frequencies are those?*

**A:** Let's **rewrite** the Dirac delta function to see them **clearly**.

$$\delta(\omega - n\omega_{ctrl} - \omega_{in}) = \delta(\omega - (n\omega_{ctrl} + \omega_{in}))$$

$$\delta(\omega - n\omega_{ctrl} + \omega_{in}) = \delta(\omega - (n\omega_{ctrl} - \omega_{in}))$$

## Zero almost everywhere

$$V_{out}(\omega) = V_{in} e^{-j\phi} \frac{\pi}{2} \left( \delta(\omega - \omega_{in}) + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} \delta(\omega - (n\omega_{ctrl} + \omega_{in})) \right) \\ + V_{in} e^{+j\phi} \frac{\pi}{2} \left( \delta(\omega + \omega_{in}) + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} \delta(\omega - (n\omega_{ctrl} - \omega_{in})) \right)$$

The Fourier transform of  $v_{out}(t)$  is therefore **non-zero only** at frequencies:

$$\omega = n\omega_{ctrl} + \omega_{in}$$

and also:

$$\omega = n\omega_{ctrl} - \omega_{in}$$

Or equivalently, they are non-zero at **these** "specific few" frequencies:


$$\omega = n\omega_{ctrl} \pm \omega_{in}$$



## Back to the time domain!

To see this more explicitly, let's take the **Inverse Fourier transform** of this result, returning again to a **real-valued time domain function**:

$$\begin{aligned}
 v_{out}(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} V_{out}(\omega) e^{-j\omega t} d\omega \\
 &= \frac{1}{2\pi} \int_{-\infty}^{\infty} V_{in} e^{-j\phi} \frac{\pi}{2} \left( \delta(\omega - \omega_{in}) + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} \delta(\omega - (n\omega_{ctrl} + \omega_{in})) \right) e^{-j\omega t} d\omega \\
 &\quad + \frac{1}{2\pi} \int_{-\infty}^{\infty} V_{in} e^{+j\phi} \frac{\pi}{2} \left( \delta(\omega + \omega_{in}) + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} \delta(\omega - (n\omega_{ctrl} - \omega_{in})) \right) e^{-j\omega t} d\omega \\
 &= \frac{V_{in}}{4} e^{+j\phi} \left( e^{-j\omega_{in}t} + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} e^{-j(n\omega_{ctrl} + \omega_{in})t} \right) \\
 &\quad + \frac{V_{in}}{4} e^{-j\phi} \left( e^{+j\omega_{in}t} + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} e^{+j(n\omega_{ctrl} + \omega_{in})t} \right) \\
 &= \frac{V_{in}}{4} \left( e^{-j[\omega_{in}t - \phi]} + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} e^{-j[(n\omega_{ctrl} + \omega_{in})t - \phi]} \right) \\
 &\quad + \frac{V_{in}}{4} \left( e^{+j[\omega_{in}t - \phi]} + \sum_{n \in \text{odd}} \frac{2}{\pi|n|} e^{+j[(n\omega_{ctrl} + \omega_{in})t - \phi]} \right)
 \end{aligned}$$

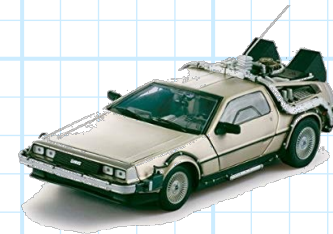

# Sinusoids!

Now applying **Euler's equation** to this output signal:

$$\begin{aligned}
 v_{out}(t) &= \frac{V_{in}}{4} \left( e^{-j[\omega_{in}t - \varphi]} + \sum_{n \in \text{odd}} \frac{2}{\pi |n|} e^{-j[(n\omega_{ctrl} + \omega_{in})t - \varphi]} \right) \\
 &+ \frac{V_{in}}{4} \left( e^{+j[\omega_{in}t - \varphi]} + \sum_{n \in \text{odd}} \frac{2}{\pi |n|} e^{+j[(n\omega_{ctrl} + \omega_{in})t - \varphi]} \right) \\
 &= \frac{V_{in}}{4} \left( e^{-j[\omega_{in}t - \varphi]} + e^{+j[\omega_{in}t - \varphi]} \right) \\
 &+ \frac{V_{in}}{4} \left( \sum_{n \in \text{odd}} \frac{2}{\pi |n|} e^{-j[(n\omega_{ctrl} + \omega_{in})t - \varphi]} + \sum_{n \in \text{odd}} \frac{2}{\pi |n|} e^{+j[(n\omega_{ctrl} + \omega_{in})t - \varphi]} \right) \\
 &= \frac{V_{in}}{2} \cos[\omega_{in}t - \varphi] + V_{in} \sum_{n \in \text{odd}} \frac{1}{\pi |n|} \cos[(n\omega_{ctrl} + \omega_{in})t - \varphi]
 \end{aligned}$$



## We've seen these before!

Among the most “energetic” of these sinusoidal output terms are for  $n \in \{-1, 0, 1\}$ , such that the output can be approximated as:

$$v_{out}(t) \cong \frac{V_{in}}{2} \cos[\omega_{in} t - \varphi] + \frac{V_{in}}{\pi} \cos[(\omega_{in} - \omega_{ctrl})t - \varphi] + \frac{V_{in}}{\pi} \cos[(\omega_{in} + \omega_{ctrl})t - \varphi]$$

**Compare** these last two terms with the output of an **ideal mixer**:

$$v_{IF}(t) = \frac{1}{2} \cos[(\omega_{RF} - \omega_{LO})t] + \frac{1}{2} \cos[(\omega_{RF} + \omega_{LO})t] !$$

# Input is RF, output is IF, control is LO

If we equate the **input** signal with the RF signal:

$$v_{in}(t) = v_{RF}(t)$$

and the **control** signal with the **LO** signal:


$$v_{ctrl}(t) = v_{LO}(t)$$

and the **output** signal with the **IF** signal:


$$v_{out}(t) = v_{IF}(t)$$

# A microwave mixer is a toggled switch

Such that:

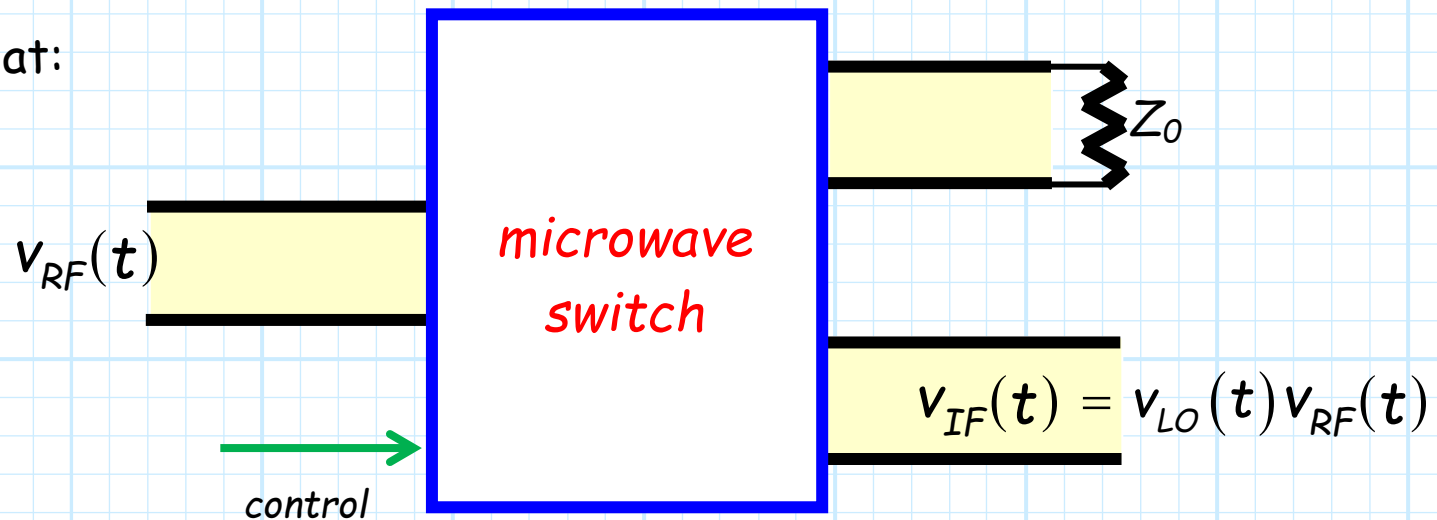

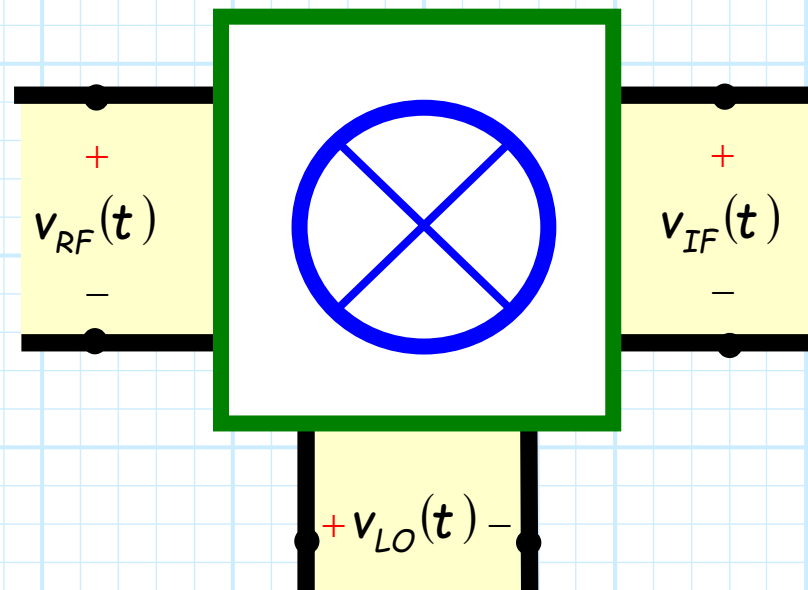We see the output of our "toggled" switch is **similar** to an ideal mixer:



## The two signals we need

Each device produces a sinusoid that is the **sum** ( $\omega_{\Sigma}$ ) of the two frequencies:

$$\cos\left[(\omega_{RF} + \omega_{LO})t\right] = \cos\left[(\omega_{in} + \omega_{ctrl})t\right]$$

and a sinusoid that is the **difference** ( $\omega_{\Delta}$ ) of the two frequencies:

$$\cos\left[(\omega_{RF} - \omega_{LO})t\right] = \cos\left[(\omega_{in} - \omega_{ctrl})t\right]$$

A “toggled” switch can be used to create similar signals as an **ideal mixer!**

## NOT an ideal mixer term

**Q:** Yes, but this toggled switch mixer seems also to generate some **other** signals as well. Most notably a one at **input frequency**  $\omega_{in}(\omega_{RF})$ :

$$\frac{V_{in}}{2} \cos[\omega_{in}t - \varphi] = \frac{V_{RF}}{2} \cos[\omega_{RF}t - \varphi]$$

**A:** Yes it does.

**Q:** Is that a **bad** thing?


**A:** Yes it is.

Among other things, this "extra" signal **reduces the power** of the two desired signals (i.e., **conservation of energy** at work):

$$\frac{V_{RF}}{\pi} \cos[(\omega_{RF} - \omega_{LO})t - \varphi] \quad \text{and} \quad \frac{V_{in}}{\pi} \cos[(\omega_{RF} + \omega_{LO})t - \varphi]$$
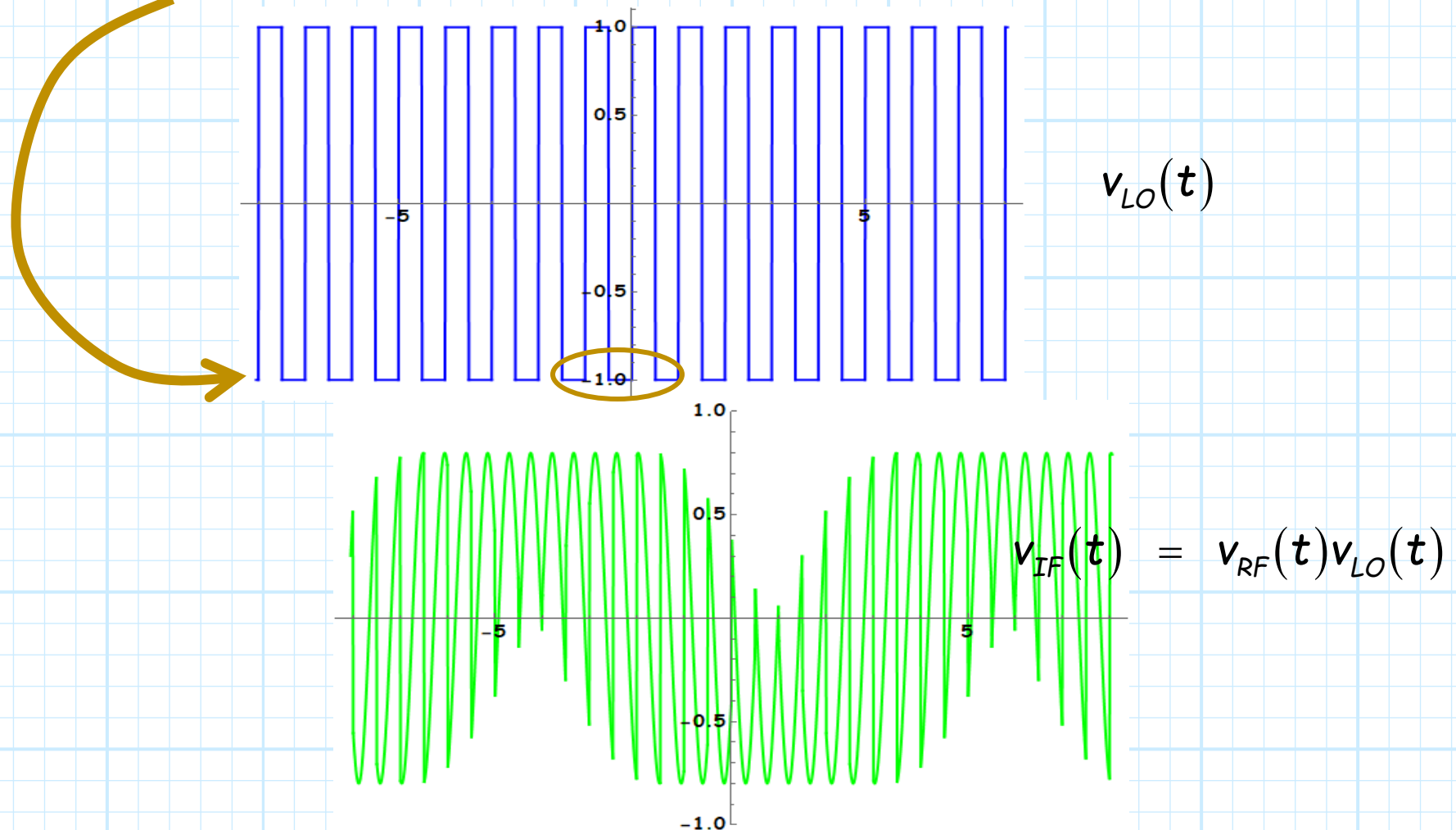
## A different square wave

To “fix” this problem, we can **instead** “multiply” the input with a **different** square wave—one instead that toggles between a value of 1.0 and -1.0.





## I'll let you verify this

Reworking all the math, **you** will find that the IF (i.e., the output) is now:

$$v_{IF}(t) = V_{RF} \sum_{n \in \text{odd}} \frac{2}{\pi |n|} \cos[(n\omega_{LO} + \omega_{RF})t - \varphi]$$

So that the IF (i.e., the output) is **approximately**:

$$v_{IF}(t) \cong V_{RF} \frac{2}{\pi} \cos[(\omega_{RF} - \omega_{LO})t - \varphi] + V_{RF} \frac{2}{\pi} \cos[(\omega_{RF} + \omega_{LO})t - \varphi]$$

Note the  $\omega_{RF}$  sinusoid is **missing**, and the remaining two terms are **twice as large**!

## Balanced and unbalanced

The first result (where the LO toggles between 1.0 and 0.0), is known as an **unbalanced mixer**:

$$v_{IF}^{unbal}(t) \cong \frac{V_{RF}}{2} \cos[\omega_{RF}t - \varphi_{RF}] + \frac{V_{RF}}{\pi} \cos[(\omega_{RF} - \omega_{LO})t - \varphi_{RF}] + \frac{V_{RF}}{\pi} \cos[(\omega_{in} + \omega_{ctrl})t - \varphi_{RF}]$$

This last result (where the LO toggles between 1.0 and -1.0), is known as a **balanced mixer**:

$$v_{IF}^{bal}(t) \cong V_{RF} \frac{2}{\pi} \cos[(\omega_{RF} - \omega_{LO})t - \varphi_{RF}] + V_{RF} \frac{2}{\pi} \cos[(\omega_{in} + \omega_{ctrl})t - \varphi_{RF}]$$

The vast majority of microwave mixers are “**balanced**”!

## A balanced mixer!

**Q:** But how can we *make* these balanced mixers? How can we multiply by  $-1.0$ ?

**A:** Remember, multiplying a sinusoid by  $-1$  is the same thing as **phase shifting** it by  $\pi$  radians (i.e.,  $-1 = e^{j\pi}$ ).

Thus, we can **equivalently** say that a **balanced mixer** toggles between a  $0^\circ$  phase shift and a  $180^\circ$  phase shift!

