


PHSX 886: Homework #9

October 3, 2025

Grant Saggars

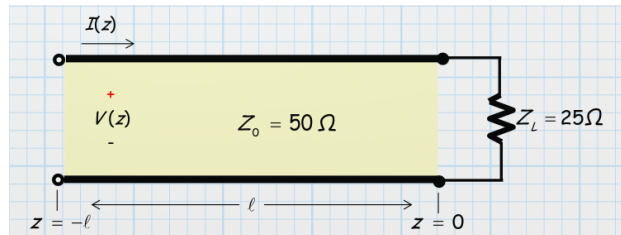Problem 1

Consider a terminated, lossless **transmission line**:



$$Z_0 = 50 \Omega, \quad Z_L = 25 \Omega$$

The wave **reflected** from load Z_L has the form:

$$V^-(z) = j e^{+j\beta z}$$

Determine the current flowing through load Z_L .

Solution:

By ohm's law, we have a constraint

$$V_L = I_L Z_L$$

By exploiting the reflection constraint, we may extract V_L :

$$\begin{aligned} V(z, \omega) &= V^+(z, \omega) + V^-(z, \omega) \\ &= V^-(z, \omega) \left(1 + \frac{1}{\Gamma_0} \right) \end{aligned} \quad \left(\Gamma_0(\omega) = \frac{V_0^-}{V_0^+} \right)$$

Γ_0 we derived from ohm's law,


$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = -\frac{1}{3}$$

The current flowing through load Z_L is then,

$$I_L = \frac{V^-(z, \omega) \left(1 + \frac{1}{\Gamma_0} \right)}{Z_L} \bigg|_{z=0} = -\frac{2j}{25} \text{ A}$$

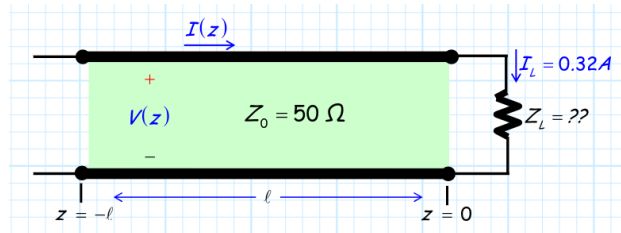Problem 2

Consider this **lossless**, terminated transmission line:



$$Z_0 = 50 \Omega, \quad I_L = 0.32 A$$

The **plus-wave voltage** along this line is:

$$V^+(z) = 12e^{-j\beta z} V$$

and the load current is:

$$I_L = 0.32 A$$

Determine the value of unknown load impedance Z_L .

Solution:

By ohm's law, we have a constraint

$$V_L = I_L Z_L$$

The definition of current, taken from the derivative of the voltage can be used to express Γ_0 in terms of known values

$$I(z, \omega) = \frac{V^+(z, \omega)}{Z_0} - \frac{V^-(z, \omega)}{Z_0}$$

$$I(z, \omega) = \frac{V^+(z, \omega)}{Z_0} (1 - \Gamma_0)$$

$$1 - \Gamma_0 = \frac{I(z, \omega) Z_0}{V^+(z, \omega)}$$

$$\Gamma_0 = 1 - \frac{I(z, \omega) Z_0}{V^+(z, \omega)}$$

Z_L we derived from ohm's law,

$$Z_L = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0}$$

$$Z_L = Z_0 \frac{1 + \left(1 - \frac{I(z, \omega) Z_0}{V^+(z, \omega)}\right)}{1 - \left(1 - \frac{I(z, \omega) Z_0}{V^+(z, \omega)}\right)}$$

$$Z_L = Z_0 \frac{2 - \frac{I(z, \omega) Z_0}{V^+(z, \omega)}}{\frac{I(z, \omega) Z_0}{V^+(z, \omega)}}$$

$$Z_L = \frac{2V^+(z, \omega)}{I(z, \omega)} - Z_0.$$

Substitution of numeric values nets:

$$Z_L = 25 \, \Omega$$