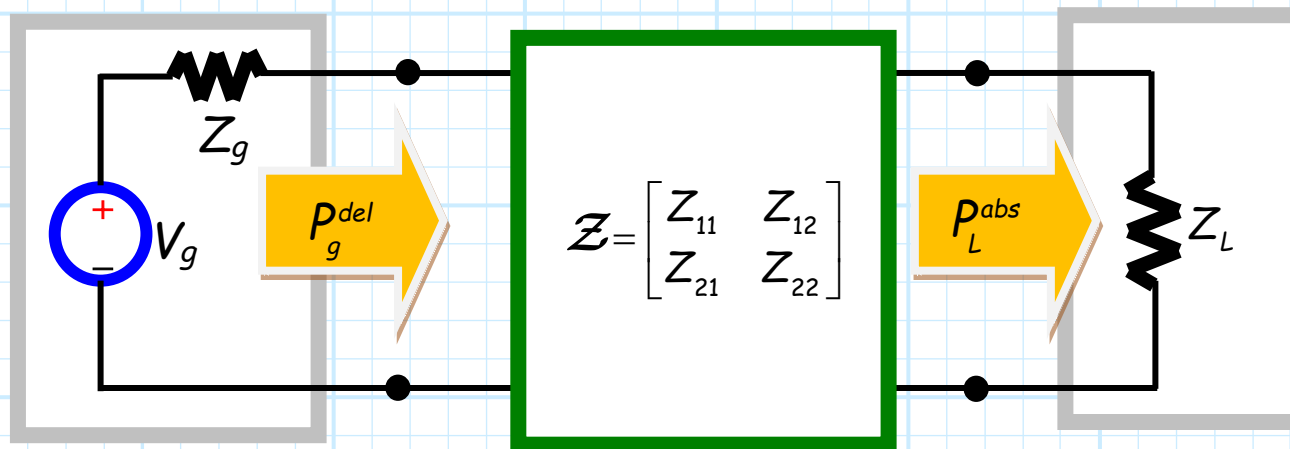


The Powers That Be

So.

We've determined the port **voltages** and port **current**—now let's determine the **rate** at which **energy** flows!



Remember this?


Recall we previously determined the voltages and currents at each of these **two** ports:

$$I_1 = V_g \frac{Z_{22} + Z_L}{(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12}Z_{21}}$$

$$V_1 = V_g \frac{Z_{11}(Z_{22} + Z_L) - Z_{12}Z_{21}}{(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12}Z_{21}}$$

$$I_2 = -V_g \frac{Z_{21}}{(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12}Z_{21}}$$
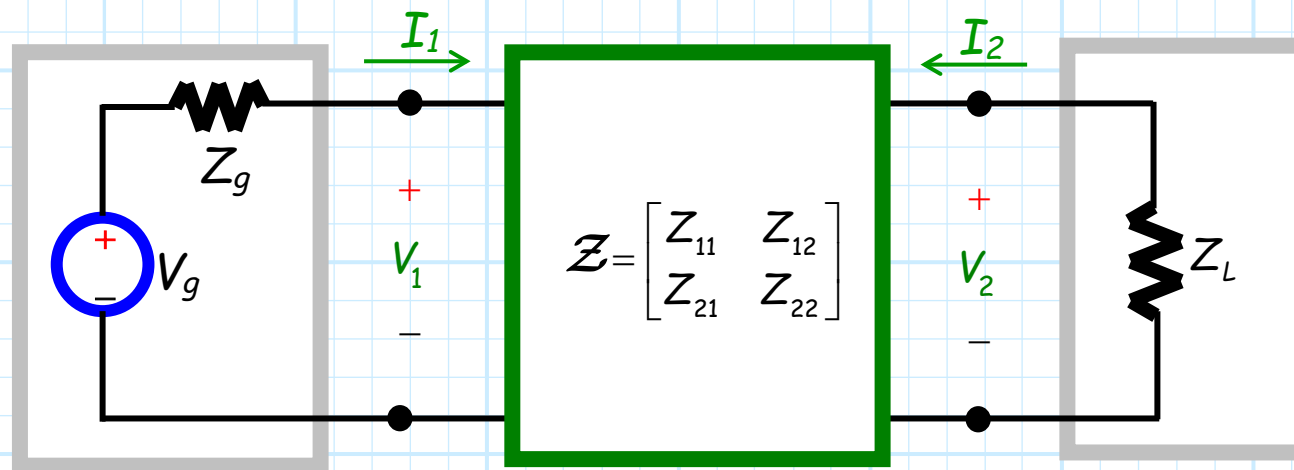
$$V_2 = V_g \frac{Z_L Z_{21}}{(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12}Z_{21}}$$



Nutin' more enjoyable than complex arithmetic

Using these results, we can determine precisely the rate (J/s) at which energy is **delivered** by the **source** to the input port:


$$\begin{aligned}
 P_g^{del} &= \frac{1}{2} \operatorname{Re}\{V_1 I_1^*\} \\
 &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re}\{Z_{11}\} |(Z_{22} + Z_L)|^2 - \operatorname{Re}\{Z_{12} Z_{21} Z_{22}^*\} - \operatorname{Re}\{Z_{12} Z_{21} Z_L^*\}}{|(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12} Z_{21}|^2}
 \end{aligned}$$

Likewise, the rate at which energy from the output port (J/s) is **absorbed** by the **load** (note the **sign!**):

$$\begin{aligned}
 P_L^{abs} &= \frac{1}{2} \operatorname{Re}\{-V_2 I_2^*\} \\
 &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re}\{Z_L\} |Z_{21}|^2}{|(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12} Z_{21}|^2}
 \end{aligned}$$

Looking at it a different way

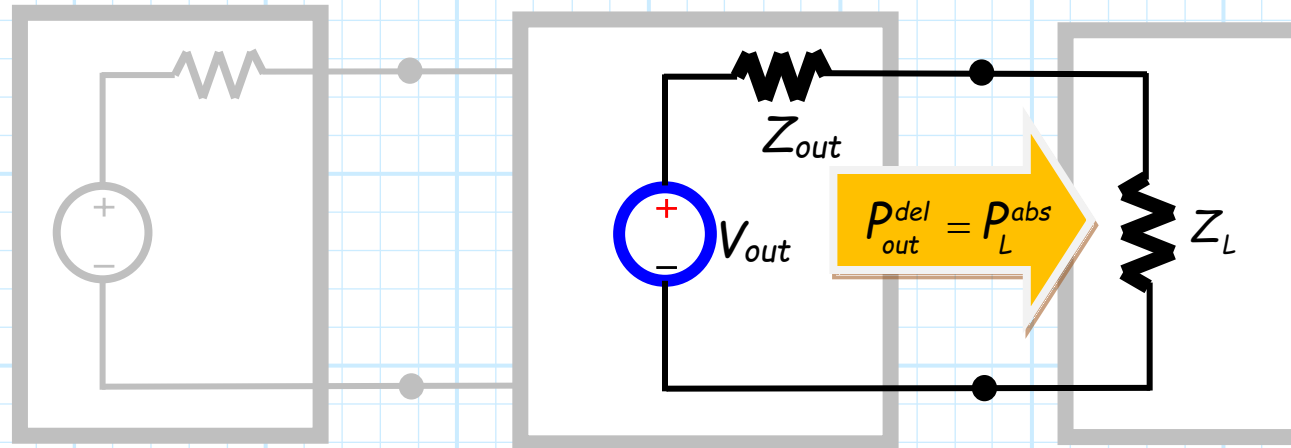Alternatively, we can now replace the **left** side of the circuit with its equivalent circuit:




By conservation of energy, the power absorbed by the load is equal to the power delivered by the equivalent source V_{out} and Z_{out} :

$$p_{out}^{del} = \frac{1}{2} |V_{out}|^2 \frac{\text{Re}\{Z_L\}}{|Z_{out} + Z_L|^2} = p_L^{abs}$$



Or, if the right side is replaced Z_{in}

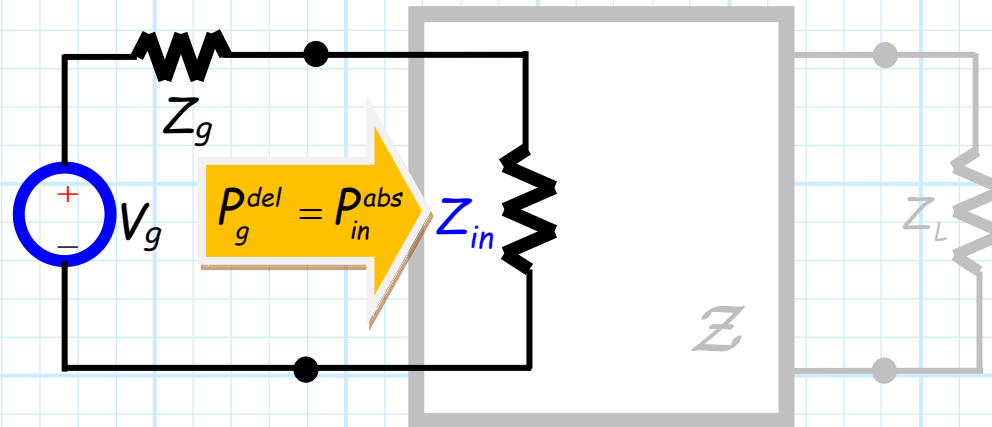Or, replacing the **right** side of the circuit with its **equivalent**:



we see that the power delivered by the source is **equal** to the power absorbed by the input impedance Z_{in} !!



$$p_g^{del} = \frac{1}{2} |V_g|^2 \frac{\operatorname{Re}\{Z_{in}\}}{|Z_g + Z_{in}|^2} = p_{in}^{abs}$$

Absorbed by Z_{in} —what that means

Q: Absorbed by the *input* impedance? What the heck does *that* mean?

*Is this the power absorbed by the **two-port device**?*

A: Note the input impedance Z_{in} characterizes the :

two-port device, when terminated in a load Z_L

thus, the power absorbed by Z_{in} is in fact the rate at which energy is absorbed by the:

two-port device terminated in a load Z_L

In other words, the power absorbed by Z_{in} is the power absorbed by the

two-port device, AND the load Z_L !!!!

Either way, the results are exactly the same!

It is **essential** that **you** understand that either of these two viewpoints provide precisely the same numerical results!

$$\begin{aligned}
 P_g^{del} &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re}\{Z_{in}\}}{|Z_g + Z_{in}|^2} \\
 &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re}\{Z_{11}\} |(Z_{22} + Z_L)|^2 - \operatorname{Re}\{Z_{12} Z_{21} Z_{22}^*\} - \operatorname{Re}\{Z_{12} Z_{21} Z_L^*\}}{|(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12} Z_{21}|^2}
 \end{aligned}$$

and:

$$\begin{aligned}
 P_L^{abs} &= \frac{1}{2} |V_{out}|^2 \frac{\operatorname{Re}\{Z_L\}}{|Z_{out} + Z_L|^2} \\
 &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re}\{Z_L\} |Z_{21}|^2}{|(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12} Z_{21}|^2}
 \end{aligned}$$

Dad gummit

Q: Now wait just *one dog-gone second!*

*I thought you said that conservation of energy required that the **delivered** power and the **absorbed** power be **equal**.*

*But it does **not** appear to **me** that **these** results for P_g^{del} and P_L^{abs} **are** equal—shouldn't they be the **same**?*

A: Nope—for this case, the values of P_g^{del} and P_L^{abs} are often very different!

Three types of devices

- * Devices or networks that **decrease** the rate of energy flow are known as **lossy**.
- * Devices or networks that **increase** the rate of energy flow are known as **active**.
- * Devices or networks that leave the rate of energy flow **unchanged** are known as **lossless**.