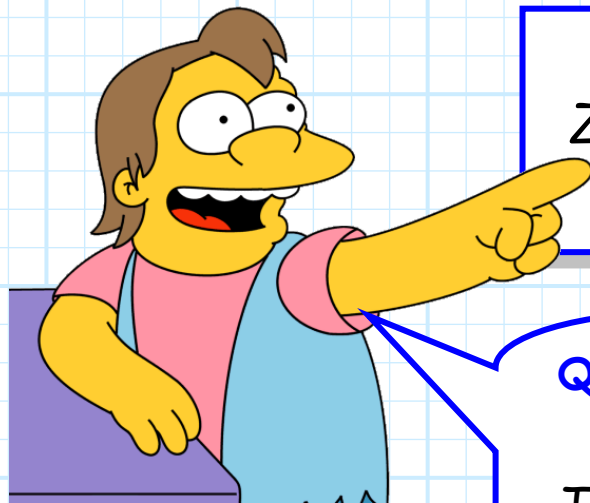


Line Impedance

Now let's define **line impedance** $Z(z, \omega)$, a **complex** function which is simply the ratio of the complex **total voltage** and complex total **current**:



$$Z(z, \omega) = \frac{V(z, \omega)}{I(z, \omega)}$$

Q: Hey! I know what **this** is!

The ratio of the voltage to current is simply the **characteristic impedance** Z_0 , right ???

A: **NO!** The line impedance $Z(z, \omega)$ is (generally speaking) **NOT** the transmission line **characteristic impedance** Z_0 !!!



→ It is unfathomably important that you understand this!!!!



Why line impedance is not Z_0

To see why **line** impedance $Z(z, \omega)$ is different than **characteristic** impedance Z_0 , recall that:

$$V(z, \omega) = V^+(z, \omega) + V^-(z, \omega) \quad \text{and} \quad I(z, \omega) = \frac{V^+(z, \omega) - V^-(z, \omega)}{Z_0}$$

Therefore, **line** impedance $Z(z, \omega)$ is:

$$Z(z, \omega) = \frac{V(z, \omega)}{I(z, \omega)} = Z_0 \left[\frac{V^+(z, \omega) + V^-(z, \omega)}{V^+(z, \omega) - V^-(z, \omega)} \right] \neq Z_0$$

Or, more specifically, we can write:

$$Z(z, \omega) = Z_0 \left[\frac{V_0^+(\omega) e^{-j\beta z} + V_0^-(\omega) e^{+j\beta z}}{V_0^+(\omega) e^{-j\beta z} - V_0^-(\omega) e^{+j\beta z}} \right]$$

What then is Z_0 ?

Q: *I'm confused! Isn't:*

$$V^+(z, \omega) / I^+(z, \omega) = Z_0 ???$$



A: Yes! That is true!

The ratio of the voltage to current for **each** of the two propagating waves is $\pm Z_0$.

$$\frac{V^+(z, \omega)}{I^+(z, \omega)} = Z_0$$

$$\frac{V^-(z, \omega)}{I^-(z, \omega)} = -Z_0$$

However, the ratio of the **sum** of the two voltages (i.e., **total voltage**) to the **sum** of the two currents (i.e., **total current**) is **not** equal to Z_0 (generally speaking)!

There is no inconsistency here

Note the expression for **line** impedance:

$$Z(z, \omega) = \frac{V(z, \omega)}{I(z, \omega)} = Z_0 \left[\frac{V^+(z, \omega) + V^-(z, \omega)}{V^+(z, \omega) - V^-(z, \omega)} \right]$$

is **consistent** with this definition of **characteristic** impedance (i.e., $Z_0 = V^+(z, \omega)/I^+(z, \omega)$)!

Say that $V^-(z) = 0$, so that only **one** wave (i.e., $V^+(z, \omega)$) is propagating on the line.

In this case, the ratio of the **total** voltage to the total current is simply the ratio of the voltage and current of the **one** remaining wave—the **characteristic impedance** Z_0 !

$$\frac{V^+(z, \omega)}{I^+(z, \omega)} = Z(z, \omega)|_{V^-(z)=0} = Z_0 \left[\frac{V^+(z, \omega) + 0}{V^+(z, \omega) - 0} \right] = Z_0$$

Let's Summarize!!

Q: So, it appears to me that characteristic impedance Z_0 is a **transmission line parameter**, depending **only** on the transmission line values L and C .

Whereas **line impedance** is $Z(z, \omega)$ depends the magnitude and phase of the two propagating waves $V^+(z, \omega)$ and $V^-(z, \omega)$ —values that depend **not only** on the transmission line, but also on the two things **attached** to either **end** of the transmission line!

Right !?



A: Exactly! Moreover, note that characteristic impedance Z_0 is simply a **real-valued number**.

Whereas, line impedance $Z(z, \omega)$ is a **complex function** of position z .