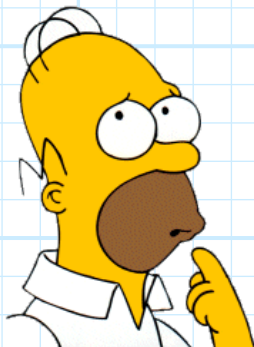


# The Transmission Line Wave Equations

$$\frac{\partial V(z, \omega)}{\partial z} = -(R + j\omega L) I(z, \omega)$$

$$\frac{\partial I(z, \omega)}{\partial z} = -(G + j\omega C) V(z, \omega)$$

So **remember**, not just **any** function  $I(z)$  and  $V(z)$  can exist on a transmission line, but rather **only** those functions that satisfy the **telegrapher's equations**.



Our task, therefore, is to **solve** the telegrapher equations and find **all** solutions  $I(z, \omega)$  and  $V(z, \omega)$ !

## The lossless approximation

**Q:** So, what functions  $I(z, \omega)$  and  $V(z, \omega)$  do satisfy both telegrapher's equations??

**A:** To make things easier, we recognize that at high frequencies:

$$R \ll j\omega L \quad \text{and} \quad G \ll j\omega C$$

So the telegrapher equations can be approximated as:

$$\frac{\partial V(z, \omega)}{\partial z} = -j\omega L I(z, \omega) \quad \frac{\partial I(z, \omega)}{\partial z} = -j\omega C V(z, \omega)$$

→ This is called the **lossless approximation** (i.e.,  $R \cong 0$  and  $G \cong 0$ ).

# The Transmission Line Wave Equations

The complex telegrapher's equations are a pair of **coupled** differential equations:

$$\frac{\partial V(z, \omega)}{\partial z} = -j\omega L I(z, \omega) \qquad \frac{\partial I(z, \omega)}{\partial z} = -j\omega C V(z, \omega)$$

With a little mathematical elbow grease, we can **decouple** the telegrapher's equations, such that we now have **two** equations involving **one** function only:

$$\frac{\partial^2 V(z, \omega)}{\partial z^2} = -\beta^2 V(z, \omega)$$

$$\frac{\partial^2 I(z, \omega)}{\partial z^2} = -\beta^2 I(z, \omega)$$

where

$$\beta^2 \doteq \omega^2 LC$$

These equations are known as the transmission line **wave equations**.

## The (one and only) solution to the wave equations

Since these wave equations each involve only **one** unknown function, they are **easily** solved!

The **solutions** are:

$$V(z, \omega) = V_0^+(\omega) e^{-j\beta z} + V_0^-(\omega) e^{+j\beta z}$$


$$I(z, \omega) = I_0^+(\omega) e^{-j\beta z} + I_0^-(\omega) e^{+j\beta z}$$

where  $V_0^+(\omega)$ ,  $V_0^-(\omega)$ ,  $I_0^+(\omega)$ , and  $I_0^-(\omega)$  are **complex constants**.

→ It is **unfathomably** important that **you** understand what this result means!



## 4 complex constants—and that's it!

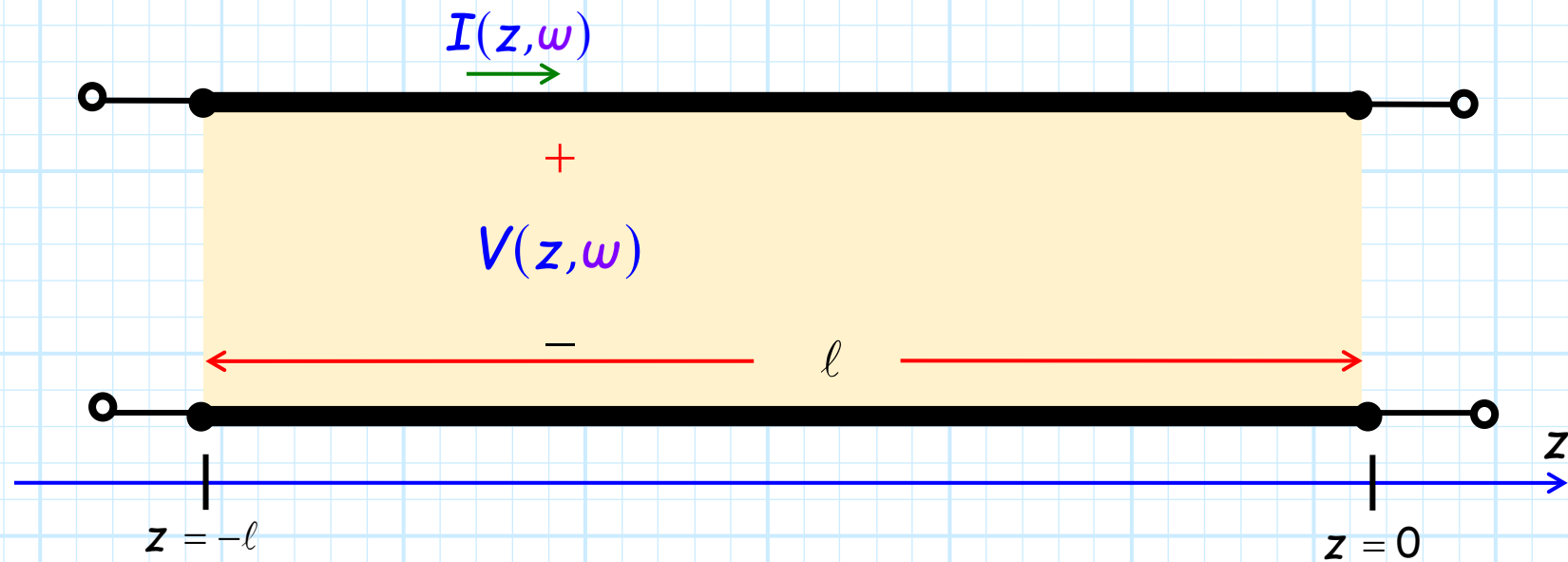

These results mean that the functions  $I(z)$  and  $V(z)$ —the functions describing the current and voltage at **all** points along a transmission line—can **always** be **completely** specified with just **four complex constants!!!!**

1.  $V_0^+(\omega)$


2.  $V_0^-(\omega)$

3.  $I_0^+(\omega)$

4.  $I_0^-(\omega)$


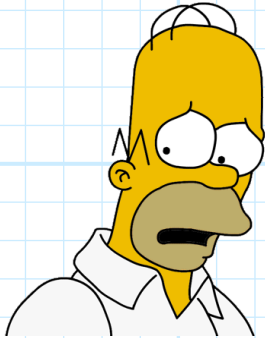
# Determining the Complex Wave Amplitudes



**Q:** But what **determines** these wave functions? How do we **find** the values of constants  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$ ?

**A:** As you might expect, the voltage and current on a transmission line is determined by the devices **attached** to it on either end (e.g., active **sources** and/or passive **loads**)!

The precise values of  $V_0^+(\omega)$ ,  $V_0^-(\omega)$ ,  $I_0^+(\omega)$ ,  $I_0^-(\omega)$  are therefore determined by satisfying the **boundary conditions** applied at **each end** of the transmission line—**more on this later!**