

EECS 622: Homework #15

October 30, 2025

Grant Saggars

Problem 1

Say you require a filter with a center frequency $f_0 = 1.0\text{GHz}$, and bandwidth $\Delta f = 100\text{MHz}$.

You need this filter to attenuate a signal with frequency $f = 1.1\text{GHz}$ by at least 40dB.

1. Determine the lowest filter order value that will achieve this requirement (i.e., 40 dB attenuation at $f = 1.1\text{GHz}$) for:


a) a Butterworth Filter

Solution:

Before anything, we will want a normalized frequency domain.

$$\begin{aligned}\alpha(f) &= \left| \frac{f_0}{f_H - f_L} \left(\frac{f}{f_0} - \frac{f_0}{f} \right) \right| - 1 \\ &= \left| \frac{1.0 \text{ GHz}}{100 \text{ MHz}} \left(\frac{f}{1.0 \text{ GHz}} - \frac{1.0 \text{ GHz}}{f} \right) \right| - 1 \\ \alpha(1.1 \text{ GHz}) &= 0.9090 \dots\end{aligned}$$

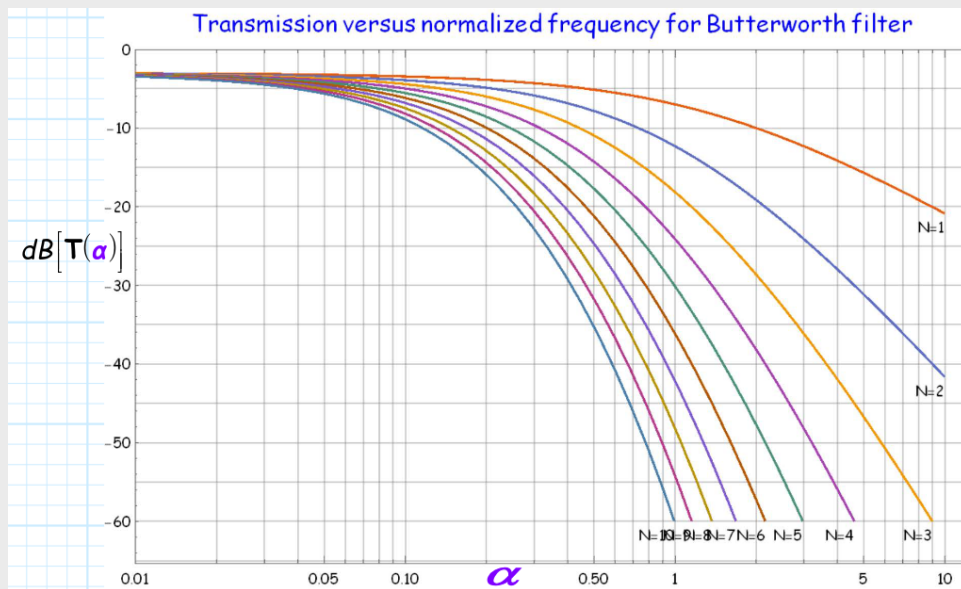
Using the normalized transmission chart from the lecture, it seems as though we could potentially get away with $N = 6$, but $N = 7$ will probably be better.



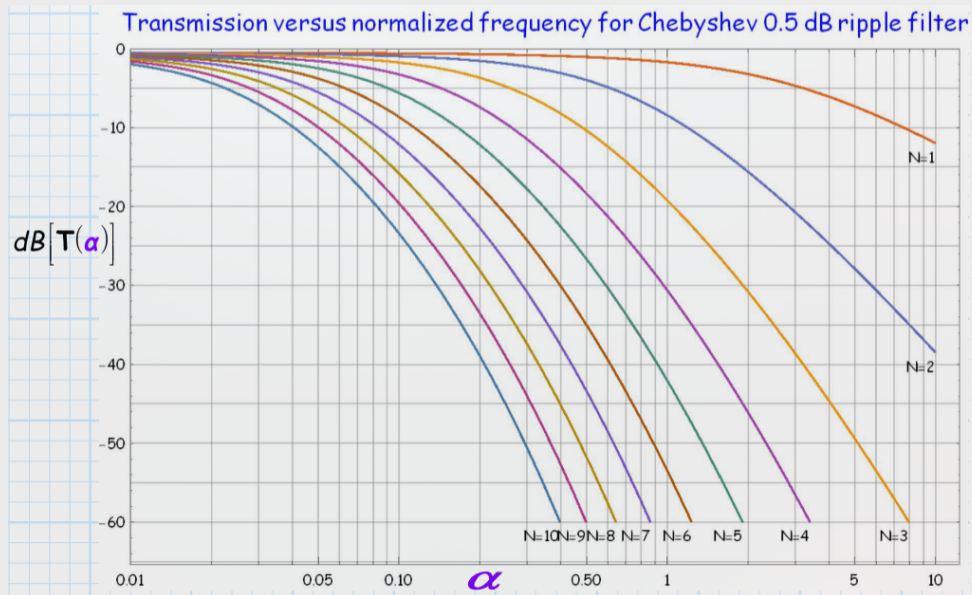b) a Chebyshev with 0.5 dB passband ripple.

Solution:


We will use the same α as in (a). We can potentially use $N = 5$, however $N = 6$ is guaranteed to achieve the desired attenuation.



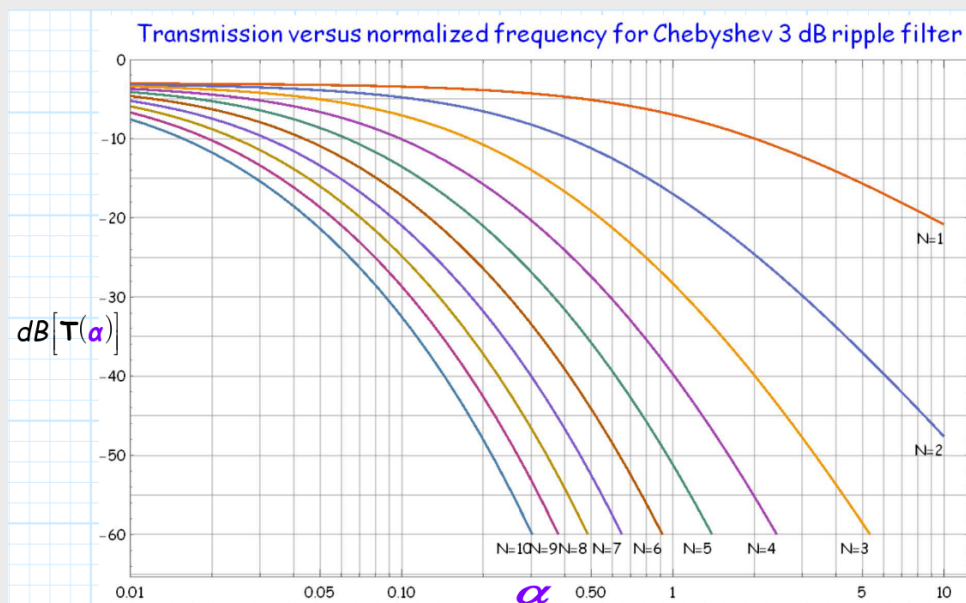c) a Chebyshev with 3.0 dB passband ripple.

Solution:

We will use the same α as in (a). $N = 5$ will safely work well to achieve the desired attenuation.



2. Using the filter orders found in part 1, determine the filter attenuation of a signal at $f = 930\text{MHz}$, for each of the three filter designs.

Solution:

We will have $\alpha(930\text{ MHz}) = 0.45$.

- (a) **Butterworth:** $N = 6$ will attenuate by -20 dB; $N = 7$ will attenuate by about -22.5 dB.
 (b) **Chebyshev 0.5 dB Passband Ripple:** $N = 5$ will attenuate by -25 dB; $n = 6$ will attenuate by about -26.5 dB
 (c) **Chebyshev 3.0 dB Passband Ripple:** $N = 5$ will attenuate by -34 dB.

Problem 2

The output of a low-pass microwave filter is terminated in a matched load.

The reflection coefficient resulting from this filter's input impedance is:

$$\Gamma_{\text{in}}(\omega) = \frac{25 \times 10^3}{25 \times 10^3 + j\left(\frac{\omega}{400}\right)}$$

Determine the 3dB cutoff frequency of this low-pass filter

Solution:

The 3 dB cutoff frequency is the point at which $P_L^{\text{abs}} \approx 0.5 \cdot P_g^{\text{avl}}$, or $V_L^{\text{abs}} \approx \frac{V_g^{\text{avl}}}{\sqrt{2}}$. We can rewrite this statement in terms of power *transmission*:

$$[T] \Big|_{3\text{dB}} = \left[\frac{P_L^{\text{abs}}}{P_g^{\text{avl}}} \right] \Big|_{3\text{dB}} \approx 0.5$$

Moreover, from our lesson on microwave filter design, we have derived:

$$|\Gamma_{\text{in}}(\omega)|^2 = 1 - T(\omega) \implies \Gamma_{\text{in}}(\omega) = \frac{\sqrt{2}}{2}$$

at the 3 dB point for any microwave filter. It's very straightforward to solve for ω_c to satisfy this:

$$\begin{aligned} \left| \frac{25 \times 10^3}{25 \times 10^3 + j\left(\frac{\omega_c}{400}\right)} \right| \left| \frac{25 \times 10^3}{25 \times 10^3 - j\left(\frac{\omega_c}{400}\right)} \right| &= \frac{\sqrt{2}}{2} \\ \frac{(25 \times 10^3)^2}{(25 \times 10^3)^2 + \left(\frac{\omega_c}{400}\right)^2} &= \frac{1}{2} \\ 2 \times 625 \times 10^6 &= 625 \times 10^6 + \frac{\omega_c^2}{160000} \\ 625 \times 10^6 &= \frac{\omega_c^2}{160000} \\ \omega_c^2 &= 625 \times 10^6 \times 160000 = 10^{14} \\ \omega_c &= 10^7 \text{ rad/s} \approx 1.6 \text{ MHz} \end{aligned}$$