

Impedance


Q: How are **complex** voltages V_n and **complex** currents I_n related?

A: We can relate a complex voltage and a complex current **if (and only if!)** they represent:

a) the current I_n **through** and,

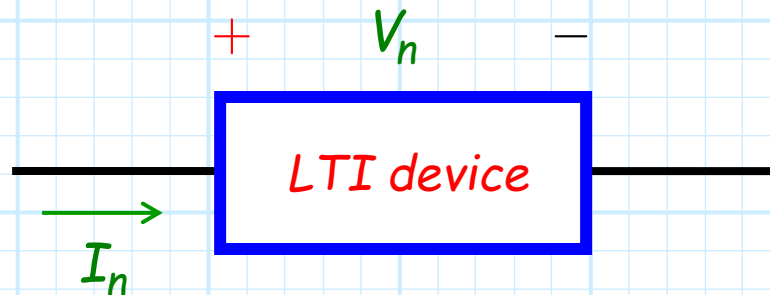b) voltage V_n **across**,

a **linear, two-terminal** (i.e., one port) **device**:



Pay particular attention to this

The ratio of the **complex** voltage and **complex** current is a **complex** value that depends on:

1. The **physical characteristics** of the two-terminal device (i.e., resistance and reactance).
2. The **frequency** ω of the time-harmonic (i.e., sinusoidal) excitation source.

→ More importantly, the ratio V_n/I_n depends **only** on these two things!

Complex impedance

This ratio is of course known as the **complex impedance** of the two-terminal, LTI (Linear Time-Invariant) device:

$$Z_n \doteq \frac{V_n}{I_n}$$

Q: *Impedance is a **complex value**—what does this complex number actually tell us?*

A: Quite a number of things!

Real and imaginary...

First, we find that:

1. the **real part** of the impedance is due to **resistive** elements in the two-terminal device—no **reactive** elements mean the impedance is **purely real** (i.e., the **imaginary part** is **zero**).

$$Z_R = R + j0 = R e^{j0}$$



2. the **imaginary part** of Z_n is due to the **reactive** elements within the two-terminal device—no **resistive** elements mean the impedance is **purely imaginary** (i.e., the **real part** is **zero**).

$$Z_L(\omega) = 0 + j\omega L = \omega L e^{j(\pi/2)}$$



$$Z_C(\omega) = 0 - j\frac{1}{\omega C} = \frac{1}{\omega C} e^{j(3\pi/2)}$$



...is resistance and reactance

Thus, we can write a complex **impedance** as:

$$Z_n = R_n + jX_n$$

where:

$R_n = \operatorname{Re}\{Z_n\}$ is the element **resistance** and,

$X_n = \operatorname{Im}\{Z_n\}$ is element **reactance**.

Q: *I guess the magnitude and phase of impedance tells us nothing important?*

A: Actually, the magnitude and phase of Z_n tells us **much!**

Magnitude is important...

Since:

$$Z_n = \frac{V_n}{I_n} = \frac{V_{0n} e^{-j\varphi_n^v}}{i_{0n} e^{-j\varphi_n^i}} = \frac{V_{0n}}{i_{0n}} e^{-j(\varphi_n^v - \varphi_n^i)}$$

the **magnitude** of Z_n is therefore:

$$|Z_n| = \left| \frac{V_{0n}}{i_{0n}} \right| \left| e^{-j(\varphi_n^v - \varphi_n^i)} \right| = \frac{V_{0n}}{i_{0n}}$$

→ The **impedance magnitude** tells us the ratio of the **magnitudes** of the **voltage** sinusoid and the **current** sinusoid!

...as is phase!

Now, the **phase** of Z_n is:

$$\arg\{Z_n\} = \arg\left\{\frac{V_{0n}}{i_{0n}} e^{-j(\varphi_n^v - \varphi_n^i)}\right\} = \varphi_n^v - \varphi_n^i$$

→ The phase of the **complex** value Z_n tells us the relative **phase difference** between the voltage sinusoid and the current sinusoid!

If $Z(\omega)$ is known, then everything is known

Remember, complex impedance depends of the **frequency ω** of the time-harmonic oscillation (i.e., the frequency of the **sinusoid**)!

As a result, we find that for most **LTI elements**, the **impedance is a function of frequency**:

$$Z_n(\omega) = R(\omega) + jX(\omega)$$

This impedance function depends on the element—and the element **only**.

→ As a matter of fact, the impedance function $Z_n(\omega)$ **completely characterizes** the LTI element!!!!!!

Can the real part depend on frequency?

Q: Wait just a *dog-gone* second! On the *previous* page you wrote:

$$Z_n(\omega) = R(\omega) + jX(\omega)$$

Obviously, the imaginary (i.e., **reactive**) component $X(\omega)$ is a function of **frequency**, but I **don't** see why the real (i.e., **resistive**) component $R(\omega)$ should depend on ω !

Perhaps you made a **mistake**?


A: Nope, no mistake!

Generally speaking, **both the imaginary and real components of impedance indeed vary with frequency ω .**

→ Maybe an **example** would help...

...and here it is

Consider **this** simple LTI device:

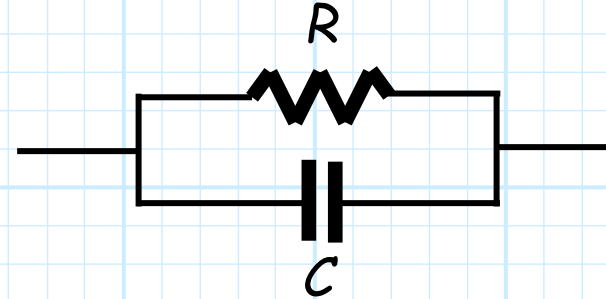

The two **parallel** circuit-elements result in **this** impedance:

$$Z(\omega) = R \parallel \frac{-j}{\omega C} = -j \left(\frac{R}{\omega C} \right) \left(\frac{1}{R - \frac{j}{\omega C}} \right) = \left(\frac{R}{1 + j\omega RC} \right)$$

Q: Yikes! Just how do we determine the real and imaginary component of *that*?

A: Multiply **both** the numerator **and** denominator by the **complex conjugate of the denominator**, i.e., by:

$$(1 + j\omega RC)^* = 1 - j\omega RC$$

The resistive component is frequency dependent!

This impedance is therefore:

$$\begin{aligned}
 Z(\omega) &= \left(\frac{R}{1 + j\omega RC} \right) \left(\frac{1 - j\omega RC}{1 - j\omega RC} \right) \\
 &= \frac{R - j\omega R^2 C}{1 + \omega^2 (RC)^2} \\
 &= \left(\frac{R}{1 + \omega^2 (RC)^2} \right) - j \left(\frac{\omega R^2 C}{1 + \omega^2 (RC)^2} \right)
 \end{aligned}$$

And so the real (**resistive**) component is **indeed** a function of frequency ω :

$$R(\omega) = \frac{R}{1 + \omega^2 (RC)^2} \quad !!!$$