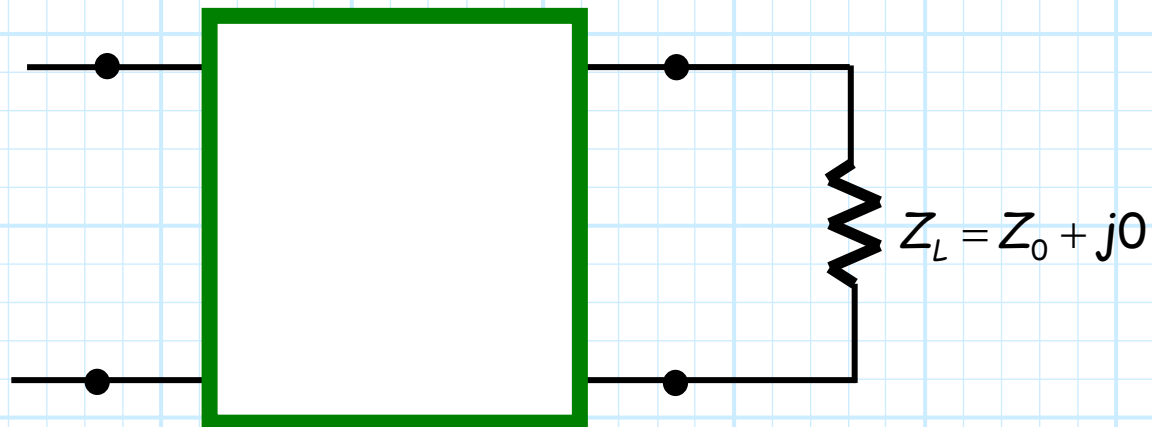



# Matched Components

Consider a **two-port device** that is terminated with a **real-valued impedance** of  $Z_L = Z_0 + j0$ .



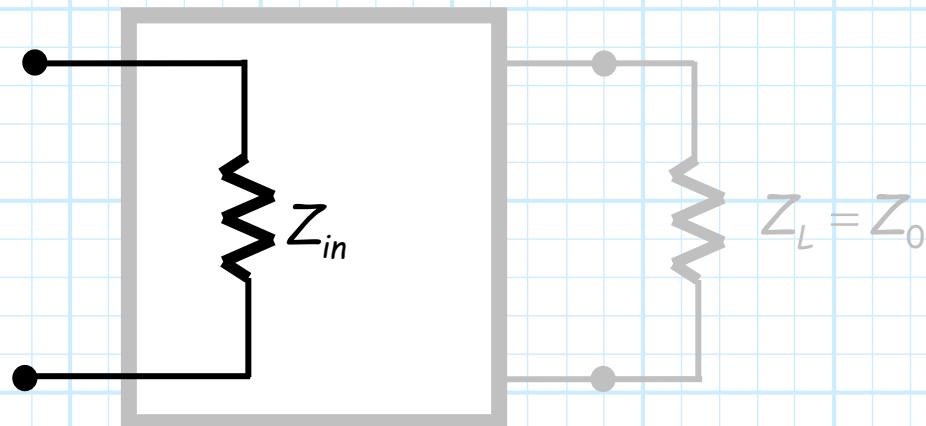
## An impedance transformer

This two-port device can (of course!) be viewed as an **impedance transformer**, as it transforms this specific **load** impedance into an **input impedance**  $Z_{in}$ :


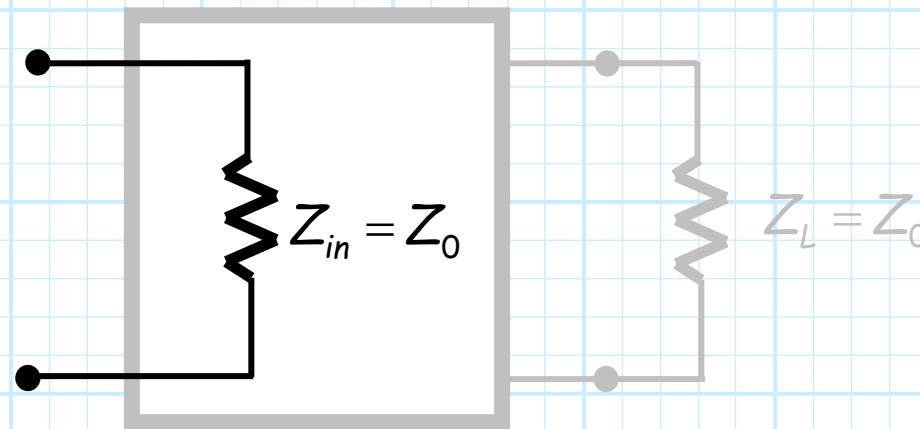
## A “matched” device (that word again!)

Say though, that this two-port network transforms the **load** impedance  $Z_0 + j0$  into an **input** impedance that is (wait for it)—**also** equal to  $Z_0 + j0$ !!!!




It “transforms” load  $Z_L = Z_0$  into  $Z_{in} = Z_0$ !!!!

A two-port device with **this** property (i.e., it “transforms” a load  $Z_0 + j0$  into input impedance  $Z_0 + j0$ ) is referred to a **“matched” device**.
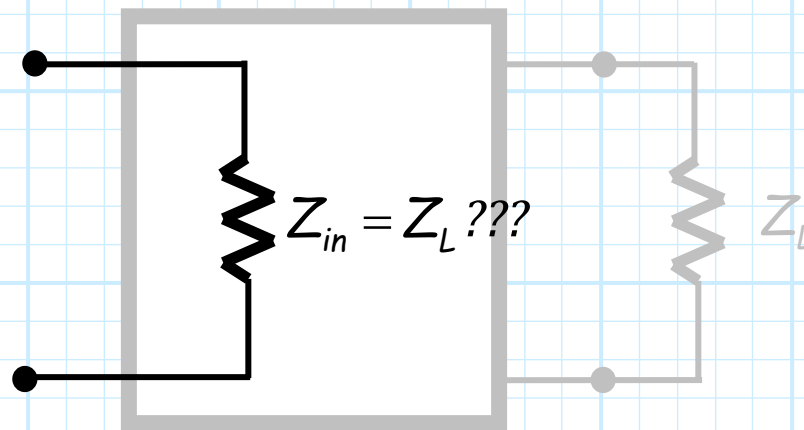
## "Matched" to a specific value

**Q:** So, does a "matched" device "transform" a load impedance of **any arbitrary value** into an **input** impedance of that **same** arbitrary value?




**A:** NO! This is **not** (in general) true.

The "transformation" of a load impedance into a **same-valued** input impedance occurs **ONLY** if the load impedance is a specific value  $Z_0 + j0$ .

More specifically then, a "matched" device is matched to **one numerical value**  $Z_0 + j0$  (e.g., "matched" to  $50\Omega$ ).
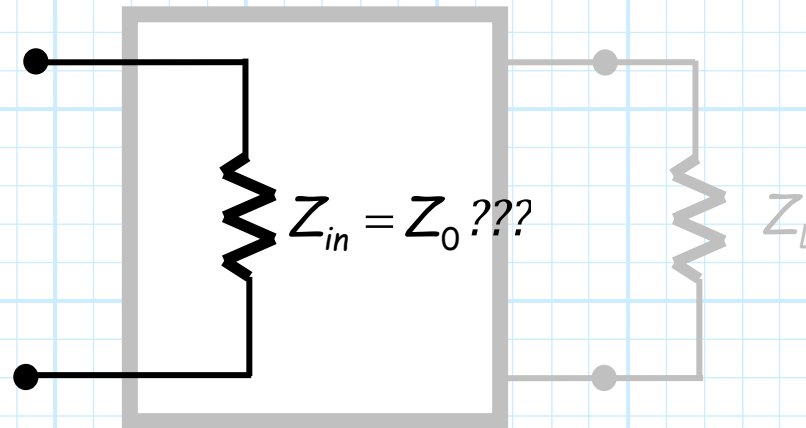
## This is NOT what it does

**Q:** So, does a “matched” device “transform” a load impedance of *any arbitrary value* into a specific input impedance  $Z_0 + j0$ ?



**A:** NO! This is **not** (in general) true either.

The “transformation” of a load impedance into an input impedance of  $Z_0$  occurs **ONLY** if the load impedance also has value  $Z_0$ .

I.E., a “matched” device **cannot** “fix” a **mismatched** (i.e.,  $Z_L \neq Z_0$ ) load!


## Now you are really annoying me

**Q:** So are "matched" devices and matching networks the same thing?

**A:** ACK. NO. STOP.


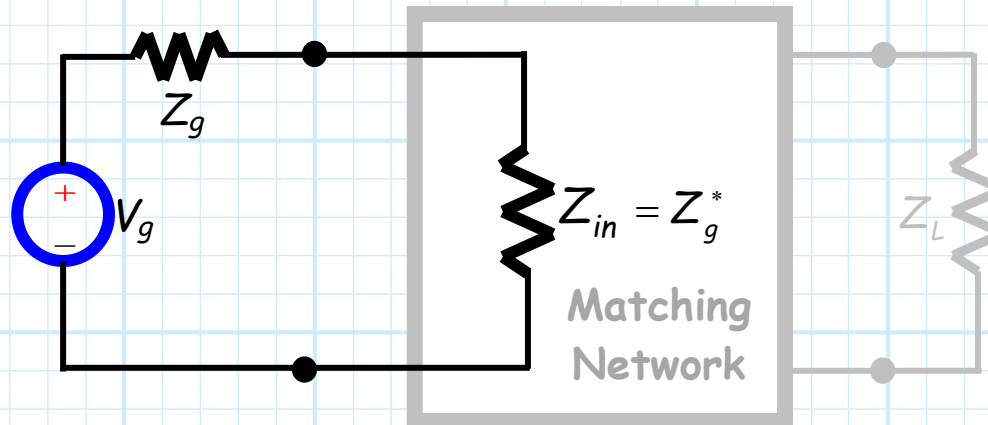
**Matching networks and a "matched" components are two very different things!!!!!!**

Recall a **matching network** is **lossless** two-port device **specifically designed** to provide a **conjugate match** between a source and load where **no conjugate match** would **otherwise** exist (i.e.,  $Z_L \neq Z_g^*$ ).



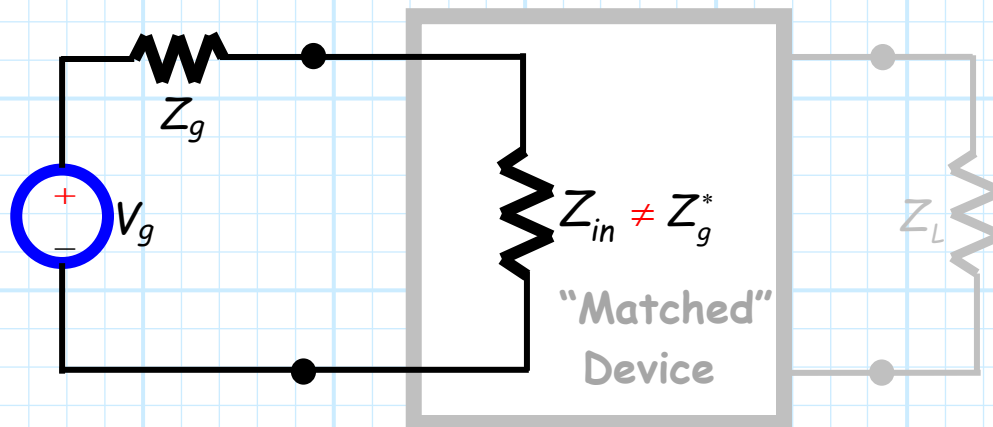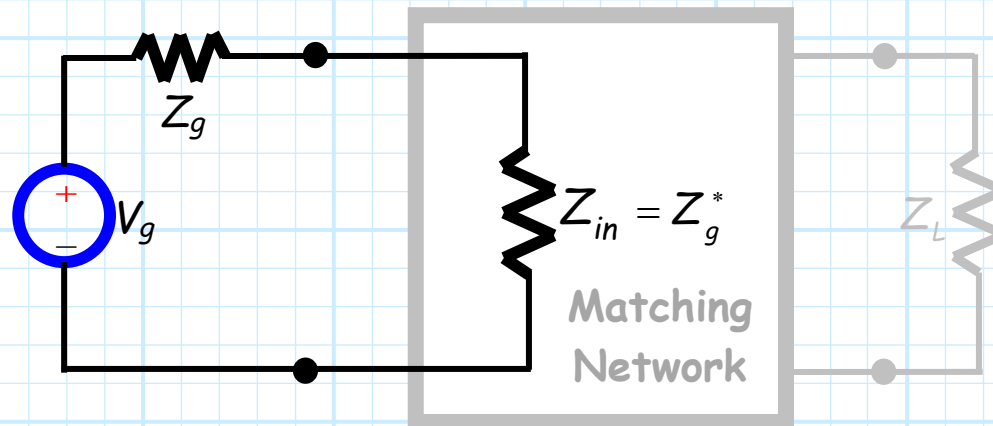
## Matching networks are not “matched” networks

In contrast, a “matched” device would almost **certainly not** result in a **conjugate match** for this case!


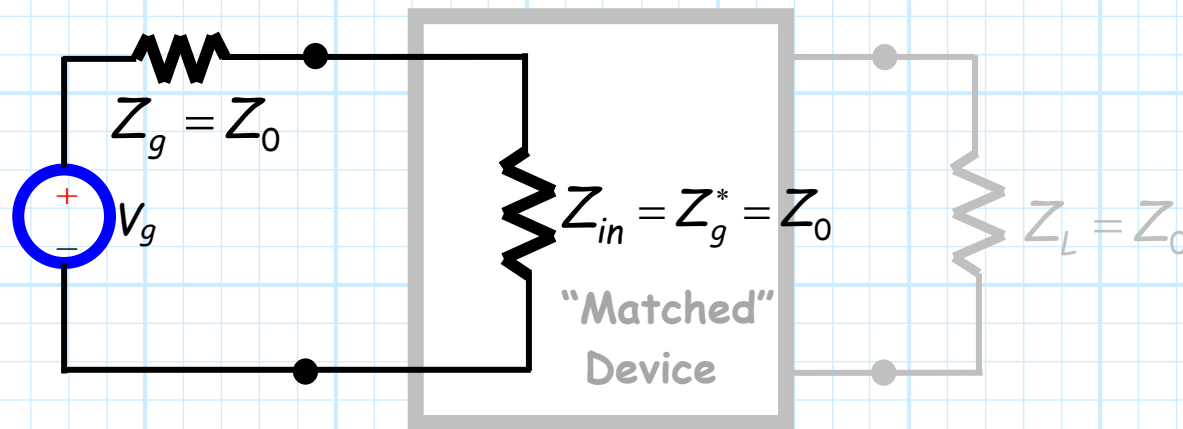
## But for this one special case...

The **exception** to this would be the case where **both** the source **and** load impedances are equal to  $Z_0$ .



For this special case, a matched device **would** result in a conjugate match!

But of course, if  $Z_g = Z_0$  and  $Z_L = Z_0$  then a **conjugate match** between the source and load would **already** exist, and there would be **no need** for a matching network!



## A matched device is useful, and not disruptive

**Q:** *So then, what's the point?*

*Why would we want, or ever use, a "matched" component?*

**A:** A "matched" component is a **useful** microwave device (e.g., amplifier, attenuator, coupler, filter, etc.).

These devices have many **attractive purposes**—but **none** of these purposes are to create a **conjugate match** (that's what **matching networks** are for!).

**Instead**, a "matched" component is designed to **both**:


- A.** Provide some **helpful purpose** (e.g., power gain).
- B.** **Preserve** (as opposed to create) the **conjugate match** between a source with  $Z_g = Z_0$  and a load with  $Z_L = Z_0$ .

## A specific example (so get off my case)

**Q:** Can you provide a *specific example* of a matched component?

**A:** Sure.

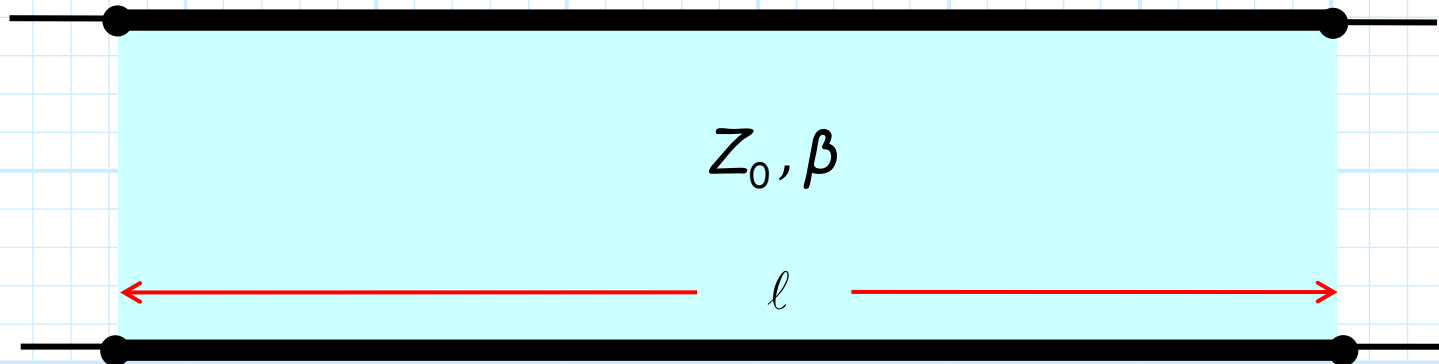
Consider an **arbitrary length** of transmission line.



This of course is a lossless **two-port device**, and we can consider it an **impedance transformer**.
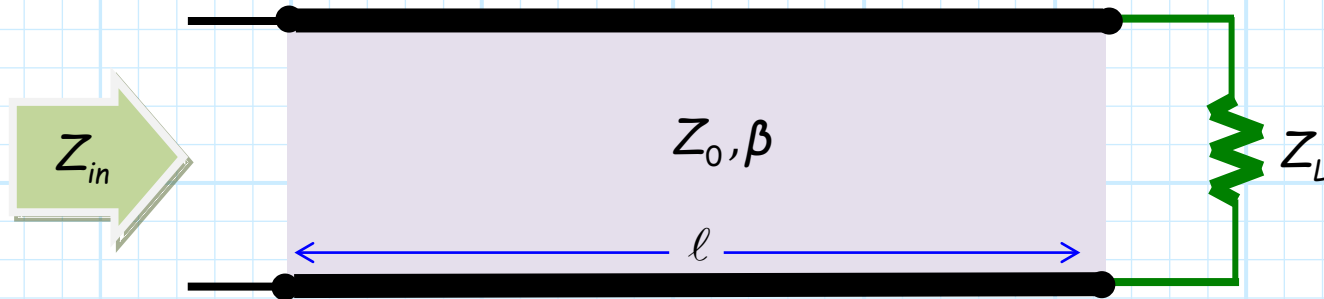
## $Z_{in}$ is neither $Z_L$ nor $Z_0$

We know that **terminating** the transmission line with some **load impedance** will result in an **input impedance** that is **neither** equal to the **load impedance** **nor** the **characteristic impedance** of the transmission line:




$$Z_{in} = Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right)$$

$$Z_{in} \neq Z_L \quad \text{and} \quad Z_{in} \neq Z_0$$
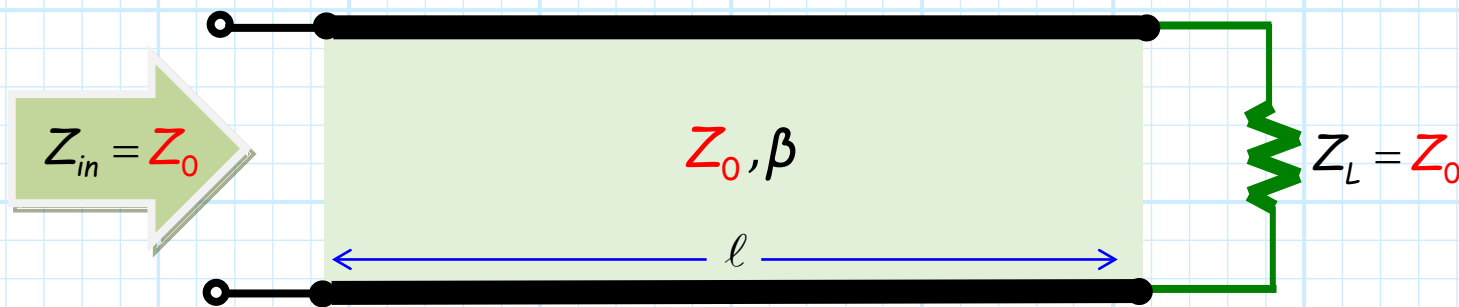
## Unless, of course, $Z_L$ equals $Z_0$

However, if the load impedance **happens** to have value  $Z_L = Z_0 + j0$ , then we **know** that the input impedance will likewise have this **same value**  $Z_0$  (regardless of length  $\ell$  !):




**This property (transforming  $Z_L = Z_0$  to  $Z_{in} = Z_0$ ) is precisely the definition of a “matched” device.**

**Thus, an arbitrary length of transmission line is a (very important) example of a two-port “matched” device (“matched” to the value  $Z_0$  of the transmission line).**

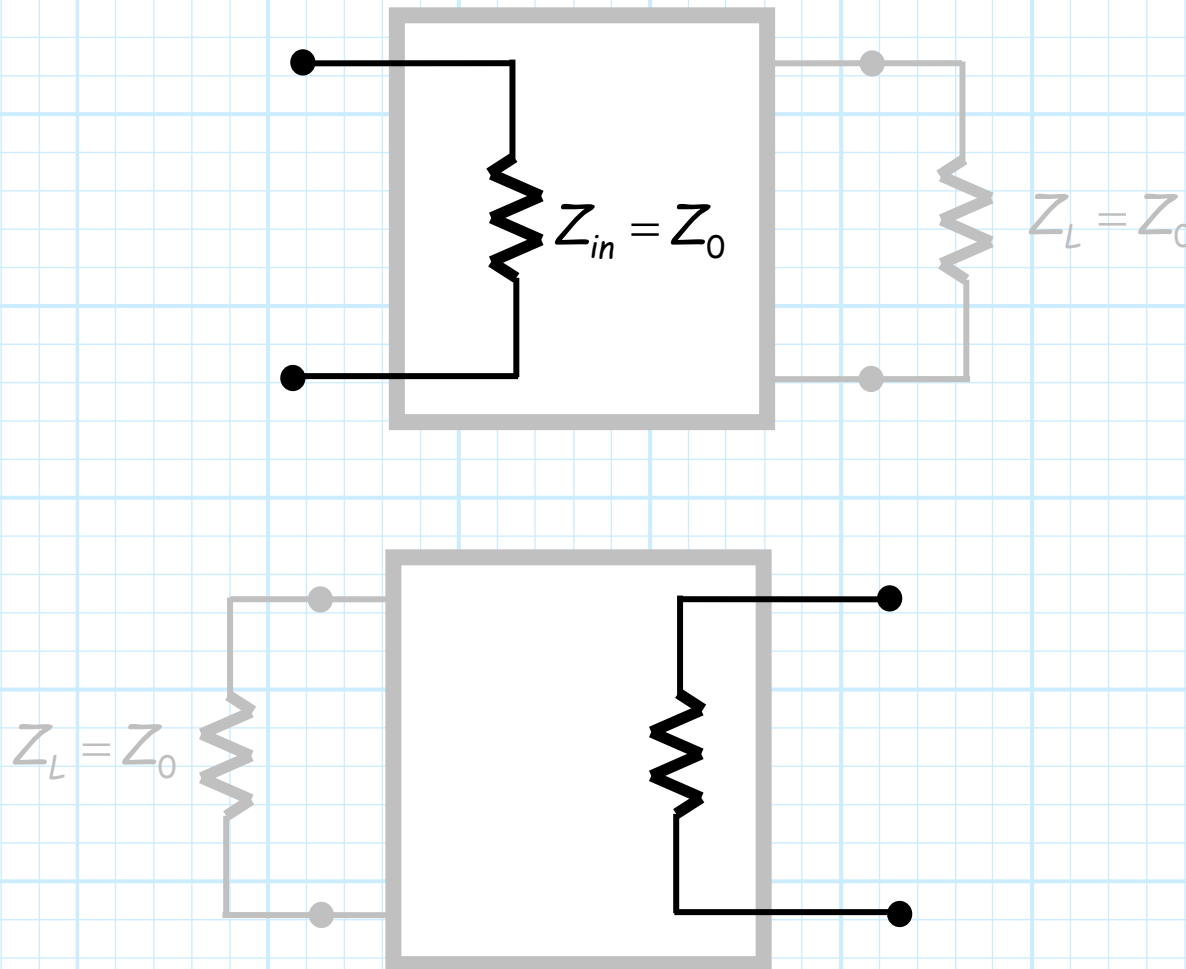
## It must work in either direction

For a two-port component to be considered “**matched**”, it must transform  $Z_L = Z_0$  to  $Z_{in} = Z_0$  in **both** directions:



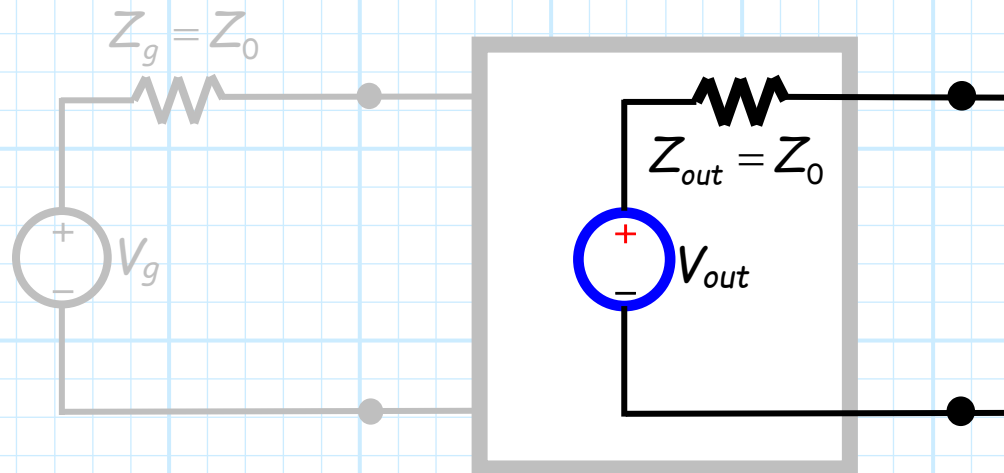
## A “matched” device transforms a source as well

Note that a “**matched**” device will likewise transform a **source** with  $Z_g = Z_0$  to one where  $Z_{out} = Z_0$  (i.e., it transforms a “matched” source into another “matched” source!).



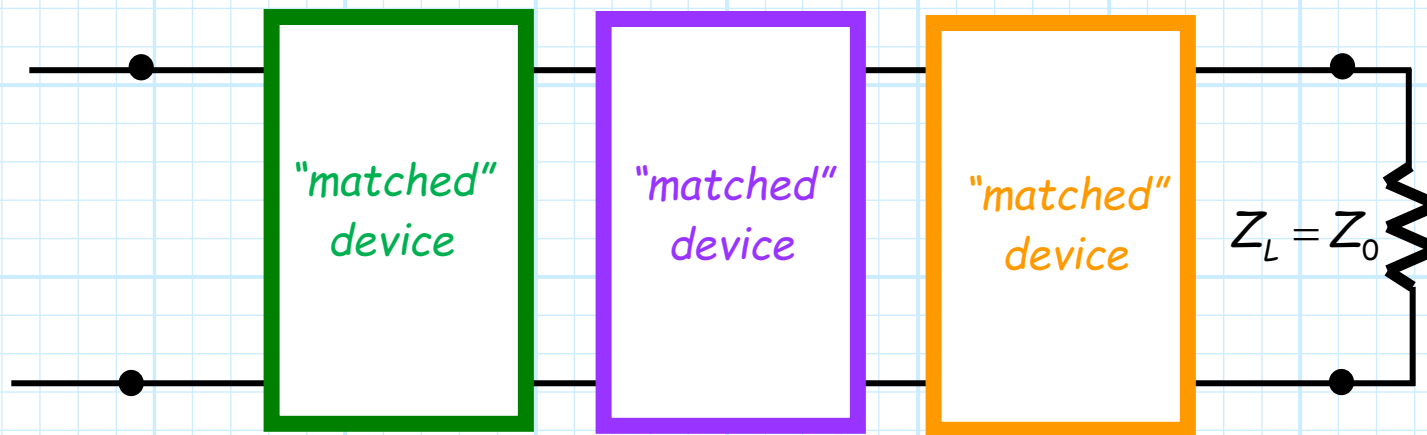
## A network of "matched" devices is also "matched"

Consider now the case where we connect multiple "matched" devices together.



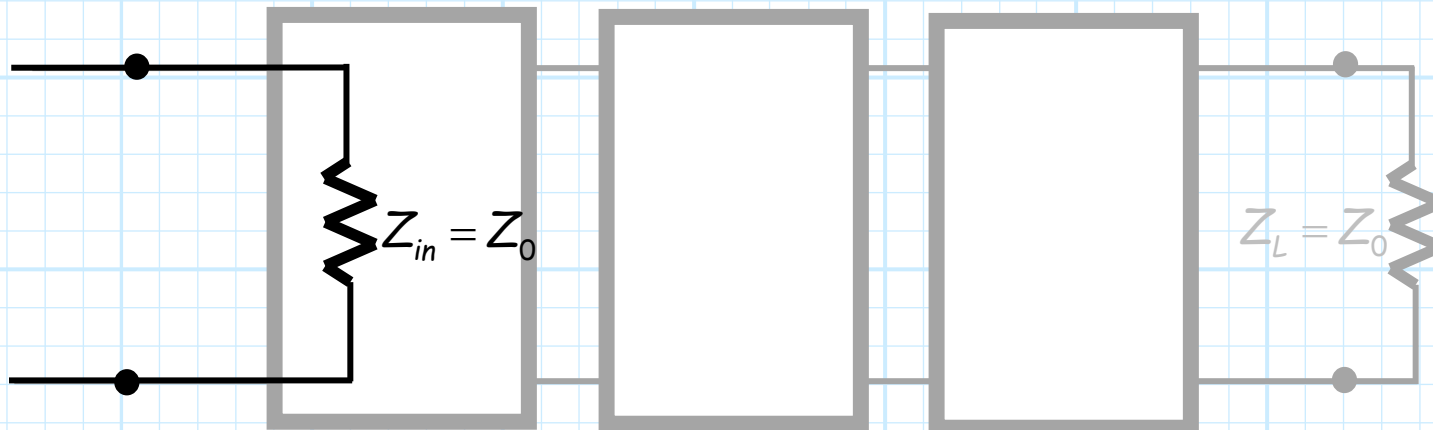Note the transformation of  $Z_L = Z_0$  to  $Z_{in} = Z_0$  is likewise **preserved**!



In a “matched” system  
—but only in a “matched” system—  
line lengths do not matter!!!!

Thus, a system constructed **completely** (i.e., no exceptions) of “matched” devices is itself a “matched” device as well.

Of course, **many** of the “matched” devices in this “matched” system could be **lengths of transmission lines**.

Most importantly, the **lengths** of these transmission lines are completely **arbitrary**.

In other words, **change** the transmission line **lengths**, and you have effectively **changed nothing**.

The system is still “matched” (i.e., a **conjugate match is preserved!**)—**regardless of the lengths of these transmission lines!!!!!!!!!!!!**



## Multi-port devices

**Q:** Are all "matched" components **two-port** devices?

**A:** Gosh no.


There are **many** useful microwave components that have 3 ports and 4 ports (or more!).

To be useful (i.e., to **not mess-up** the conjugate match  $Z_{in} = Z_0 = Z_{out}$ ), these **multi-port** devices must also be "matched".


This means that the **input impedance** of each and **every** port must be equal to  $Z_{in} = Z_0$ , provided that **all other ports** are terminated in "matched" loads  $Z_L = Z_0$ .

Note then that "matched" loads and "matched" sources are just **one-port** manifestations of "matched" devices.

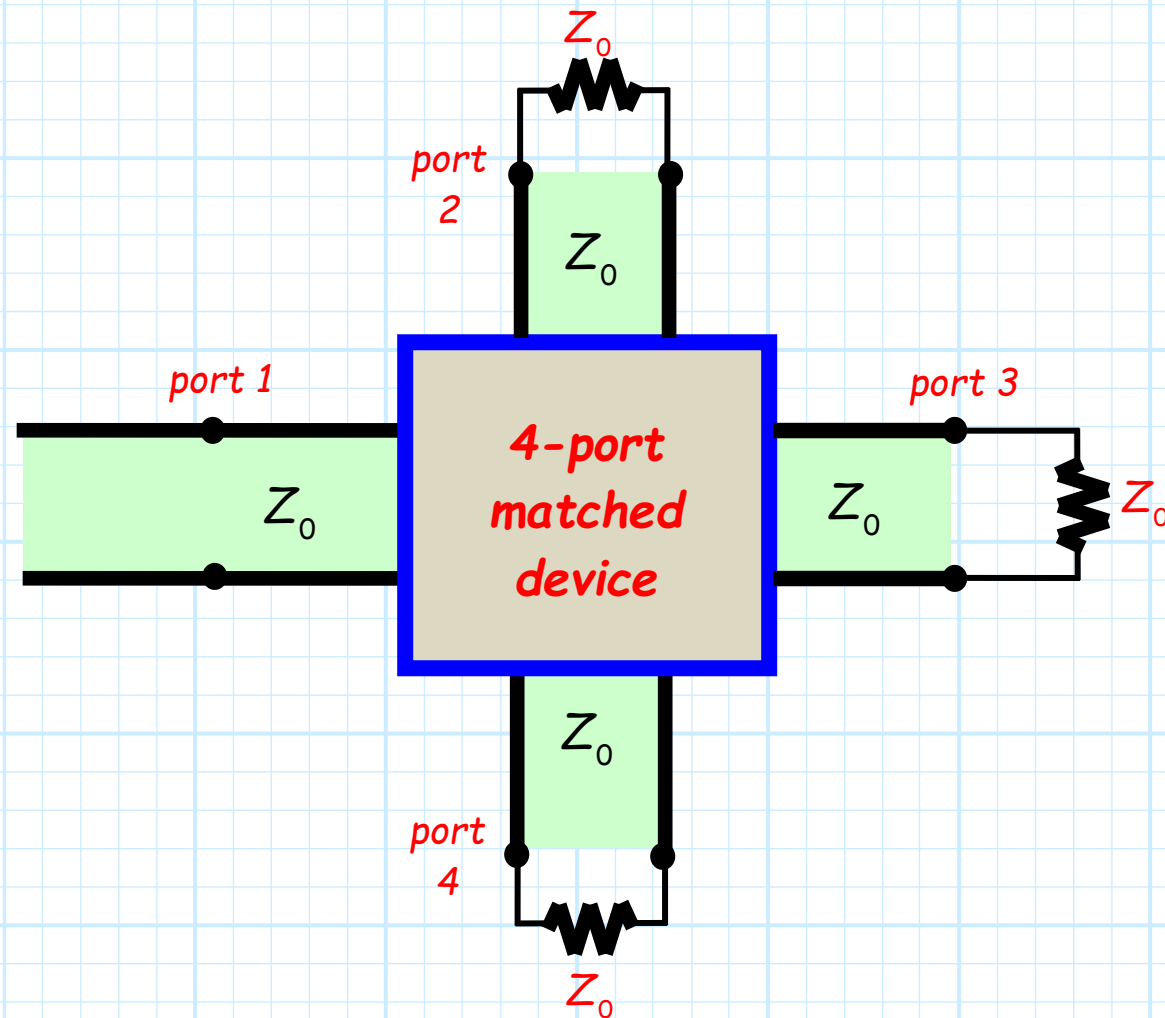Since this four-port  
component is "matched"...



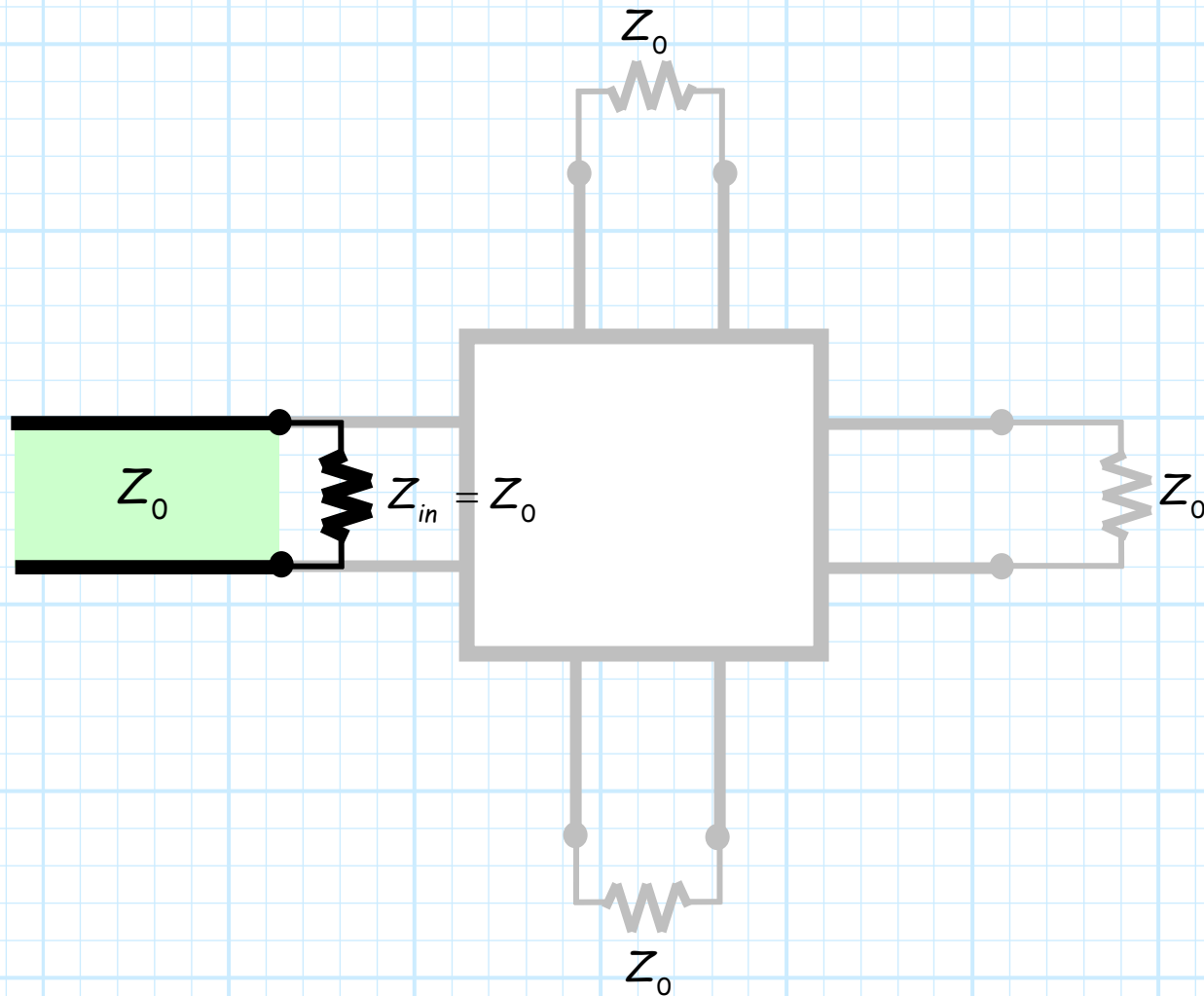The input impedance at every port is  $Z_0$



## Without exception, every device must be matched

In summary, a microwave **system** (e.g., a microwave receiver) must be **constructed entirely of “matched” components (no exceptions!)**.


In this way we find that:

- A.** A conjugate match is **preserved** (available power is delivered!) at **every** point in the system, and...
- B.** this is true **regardless of the lengths** of the transmission lines connecting the devices (the transmission lines are “matched” devices as well!).

## Without exception !!!!

If even **one component** in the system is not “matched”, then the matched system will be **corrupted**, meaning:

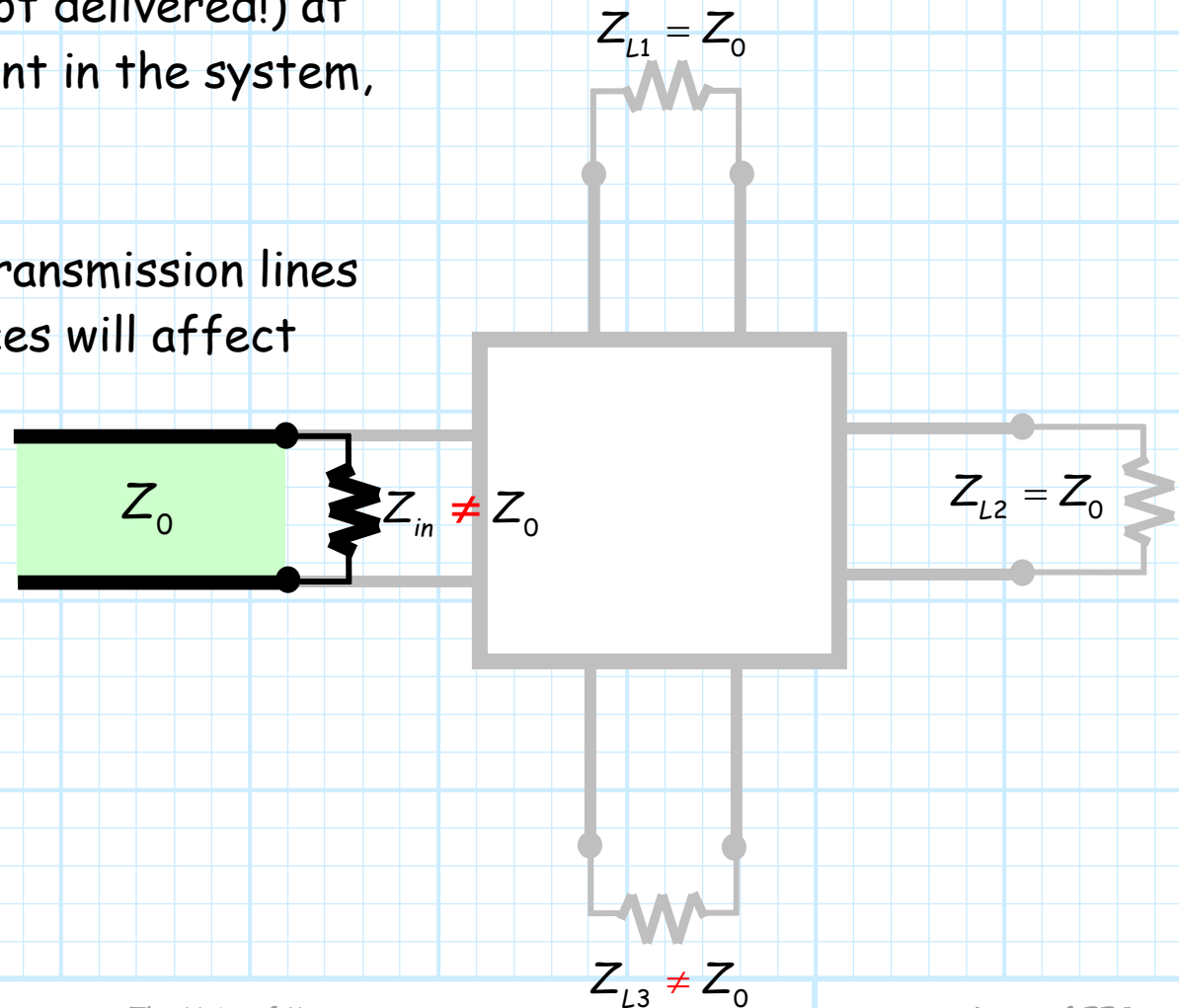- A. A conjugate match is not **preserved** (available power is not delivered!) at potentially **every** point in the system, and...
- B. the lengths of the transmission lines connecting the devices will affect this power transfer.






# It's not like they're lying (usually)

**Q:** So do vendors tell us what  $Z_{in}$  *really* is?

**A:** Not usually!

Remember, input impedance is a **complex** value.

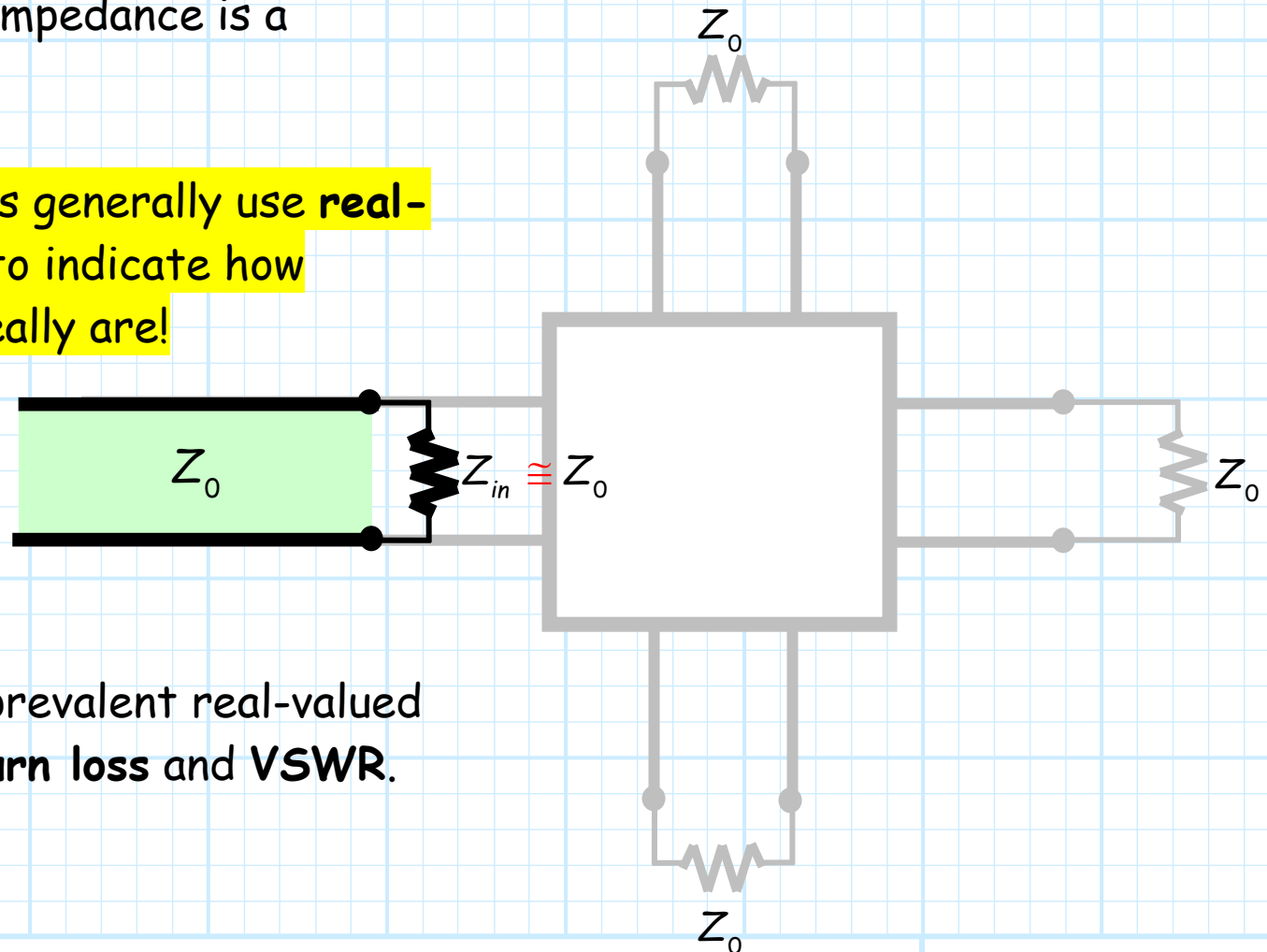Therefore vendors generally use **real-valued** measures to indicate how "matched" they really are!



Two of the most prevalent real-valued measures are **return loss** and **VSWR**.