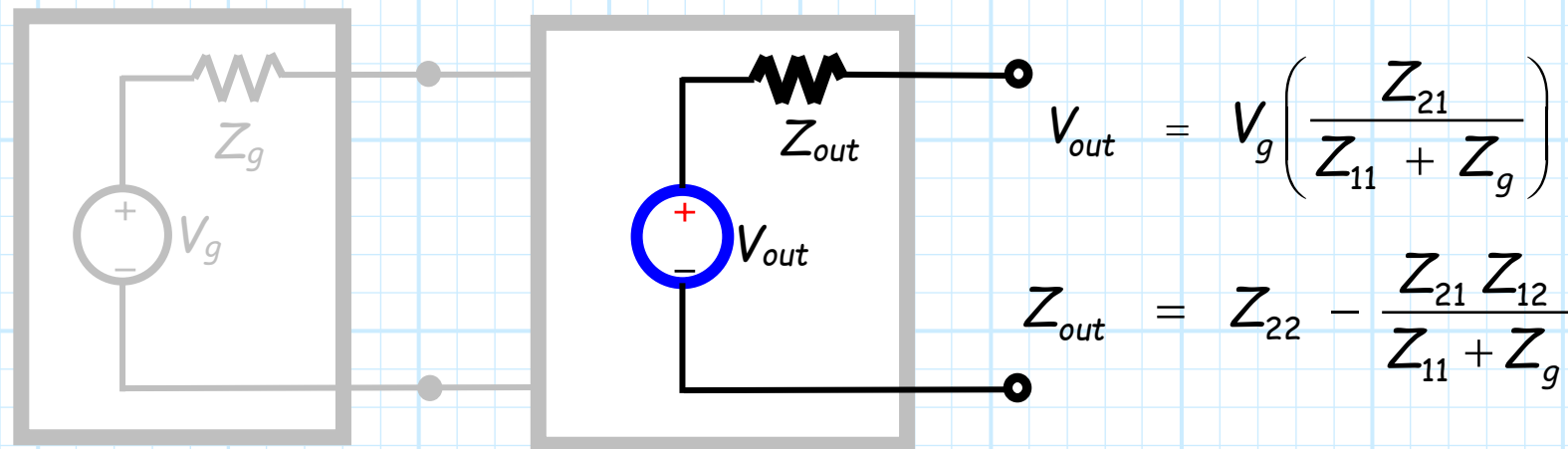


Available Power Transformation

Q: So, you said that a two-port device can be viewed as a **source transformer**, which provides a **new equivalent source**:




but, just what is the available power P_{out}^{pavl} of this **transformed** source??

Transformed available power


A: Recall available power P_{avl} is a parameter of the **source only**.

For the “**original**” source this value is:

$$p_g^{avl} = \frac{|V_g|^2}{8 \operatorname{Re}\{Z_g\}} = \frac{|V_g|^2}{8 R_g}$$

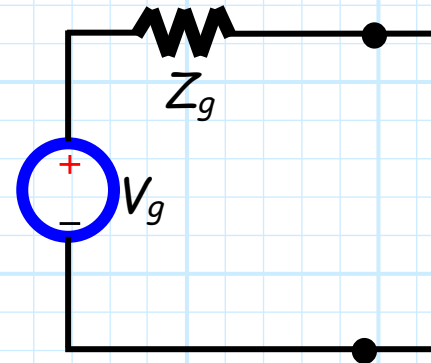

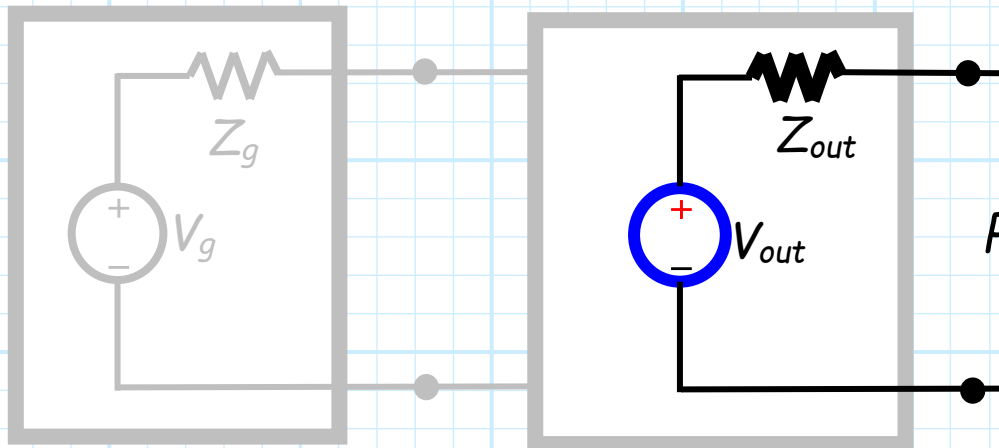Thus, for the **transformed** source (i.e., $V_g \rightarrow V_{out}$ and $Z_g \rightarrow Z_{out}$) the available power is likewise:



$$p_{out}^{avl} = \frac{|V_{out}|^2}{8 \operatorname{Re}\{Z_{out}\}} = \frac{|V_{out}|^2}{8 R_{out}}$$


A lossy network reduces available power

Q: But how are these values related?

Is one value *different* than the other?


A: It all depends on the **characteristics** of the **two-port** network!

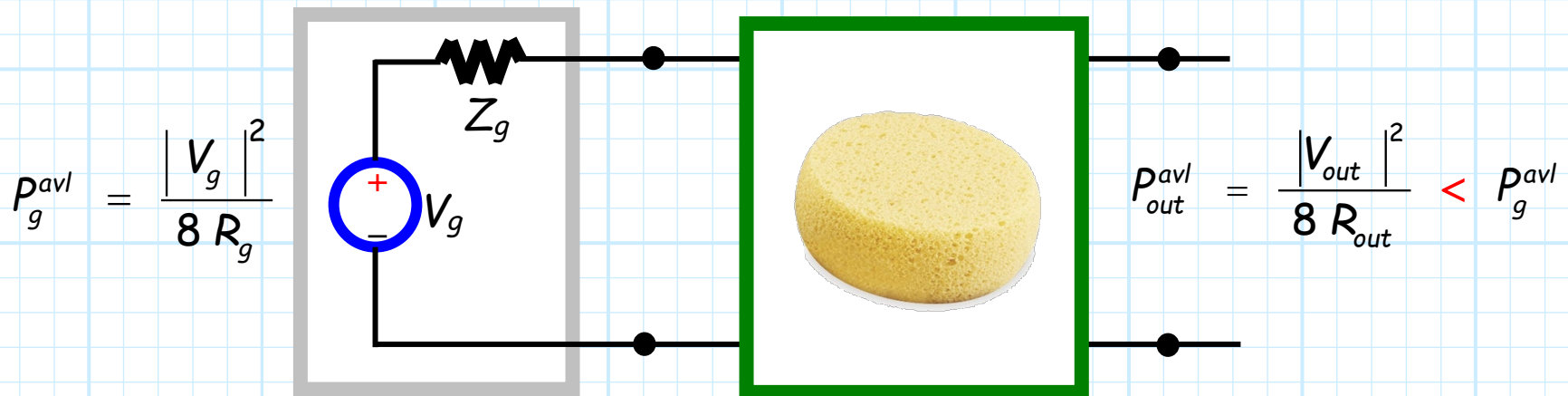If the two-port device is **lossy**, we find that available power of the transformed source is **less** than the original:



An active device can increase available power

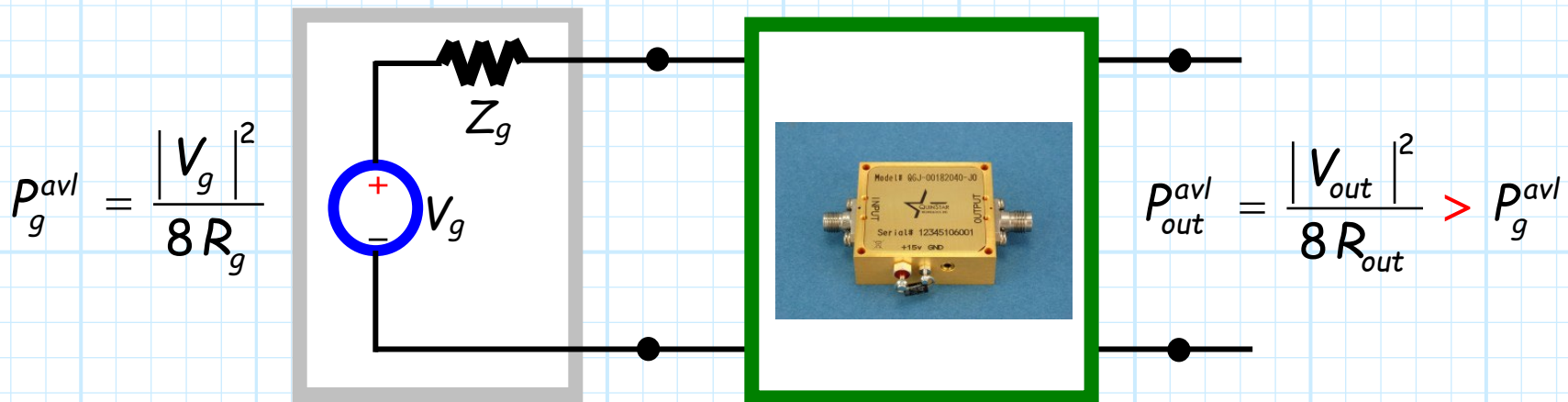Conversely, if the two-port device is an **active** device (e.g., an **amplifier**) then the available power of the **transformed** source can be **greater** than the original:



Q: *I think I see where this is going!*

*If the two-port device is **lossless**, is the available power of the transformed source **equal** to that of the original?*

A: Let's find out!


Lossless means purely reactive

Recall for a **lossless** device, the elements of its impedance matrix are **purely imaginary** (i.e., reactive).

$$\mathbf{Z}_{\text{lossless}} = \begin{bmatrix} jX_{11} & jX_{12} \\ jX_{12} & jX_{22} \end{bmatrix}$$

For this **lossless** case, the **transformed** source has the form:
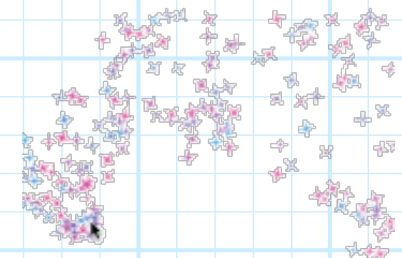
$$V_{\text{out}} = V_g \left(\frac{jX_{21}}{jX_{11} + Z_g} \right)$$



$$Z_{\text{out}} = jX_{22} + \frac{(X_{21})^2}{jX_{11} + Z_g} = \frac{(X_{21})^2 Z_g^*}{|R_g + j(X_g + X_{11})|^2} + j \frac{(X_{22} - (X_{21})^2 X_{11})}{|R_g + j(X_g + X_{11})|^2}$$

Preparing to determine P_{avl} ...

Using these results, we **further** determine:

$$|V_{out}|^2 = |V_g|^2 \left| \frac{jX_{21}}{jX_{11} + Z_g} \right|^2 = |V_g|^2 \frac{(X_{21})^2}{|R_g + j(X_g + X_{11})|^2}$$


and:

$$Re\{Z_{out}\} = \frac{(X_{21})^2 Re\{Z_g^*\}}{|R_g + j(X_g + X_{11})|^2} = R_g \frac{(X_{21})^2}{|R_g + j(X_g + X_{11})|^2}$$

...and we've seen this result before!

Thus, the available power of the **transformed** source is:

$$P_{out}^{avl} = \frac{|V_{out}|^2}{8R_{out}} = |V_g|^2 \frac{(X_{21})^2}{|R_g + j(X_g + X_{11})|^2} \frac{|R_g + j(X_g + X_{11})|^2}{8R_g(X_{21})^2} = \frac{|V_g|^2}{8R_g}$$

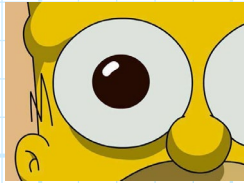

Look at this result!

It says that although a source transformed by a **lossless** two-port device exhibits a **different** voltage source ($V_{out} \neq V_g$), and a **different** source impedance ($Z_{out} \neq Z_g$)—it exhibits precisely the **same available power**:

$$P_{out}^{avl} = \frac{|V_g|^2}{8R_g} = P_g^{avl} \text{ !!!!! (for lossless transformer!)}$$

But won't a smaller R_{out} result in greater available power?

Q: Wait a second! According to *this* result:

$$R_{out} = R_g \frac{(X_{21})^2}{|R_g + j(X_g + X_{11})|^2}$$

the transformed output resistance could be much **greater** than the original (i.e., $R_{out} > R_g$).

You said earlier that a **larger** source resistance results in a **reduction** in available power (and **vice versa**).


→ How then could the available power remain the **same**?

Can't transform Z_g without transforming V_g also

A: For a **given** (i.e., **fixed**) voltage source, an increase (decrease) in source resistance **does** result in a decrease (increase) in available power—just **look** at the math→ $p_g^{avl} = \frac{|V_g|^2}{8R_g}$


The important thing to remember in this circumstance is that the **voltage** source is **not** fixed!

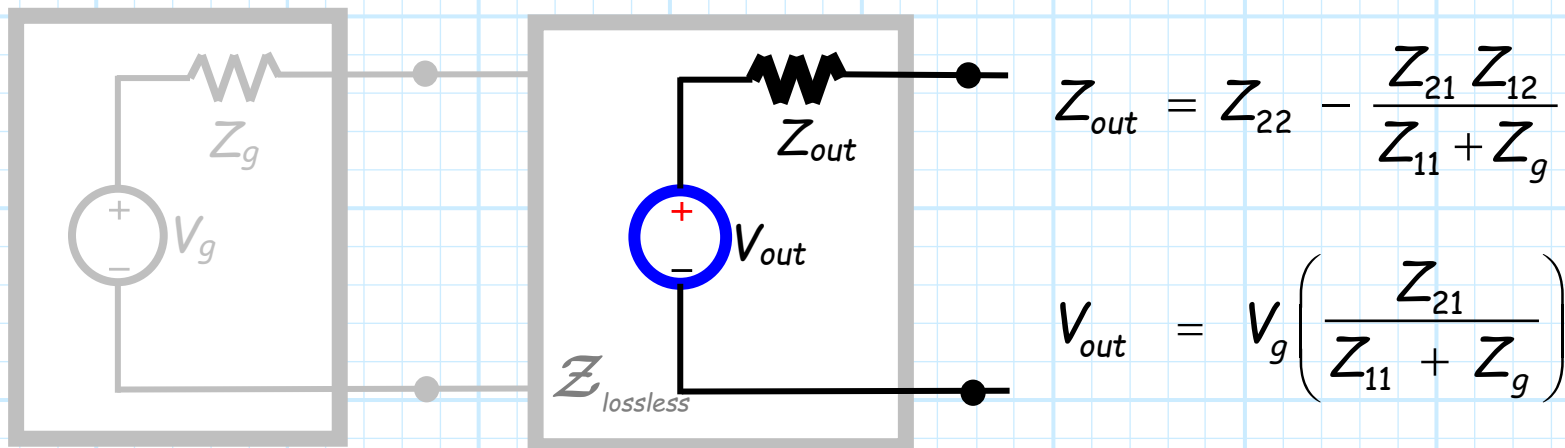A two-port device transforms **both** the voltage source V_g **and** the source impedance Z_g !



An example

For a **lossless** two-port device, we find that if the transformed source resistance is **four** times (say) that of the original (i.e., $R_{out} = 4R_g$), then the **voltage** source will likewise be transformed such that its magnitude is **doubled** (i.e., $|V_{out}|^2 = 4|V_g|^2$).

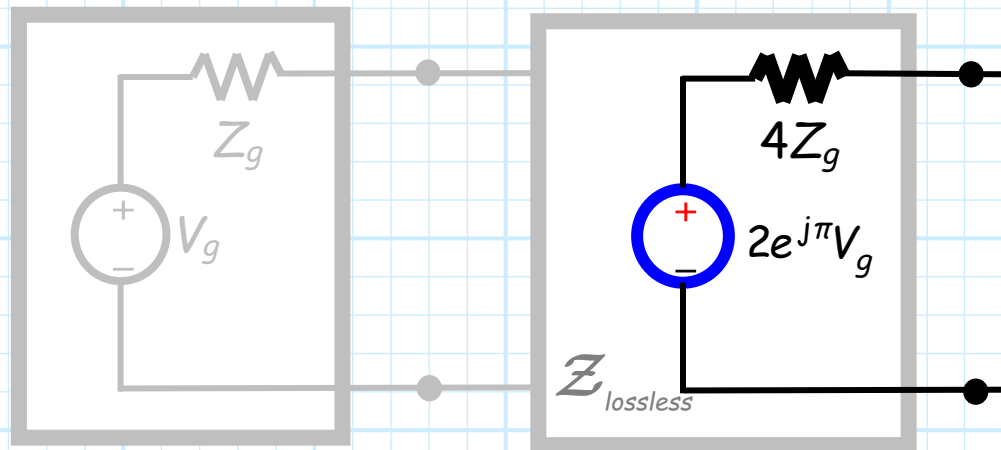

$$\begin{aligned}
 p_{out}^{avl} &= \frac{|2e^{j\pi} V_g|^2}{8(4R_g)} \\
 &= \frac{4|V_g|^2}{32R_g} \\
 &= \frac{|V_g|^2}{8R_g} \\
 &= p_g^{avl}
 \end{aligned}$$

The transformed **available** power is thus **unaltered** (i.e., $p_{out}^{avl} = p_g^{avl}$)!