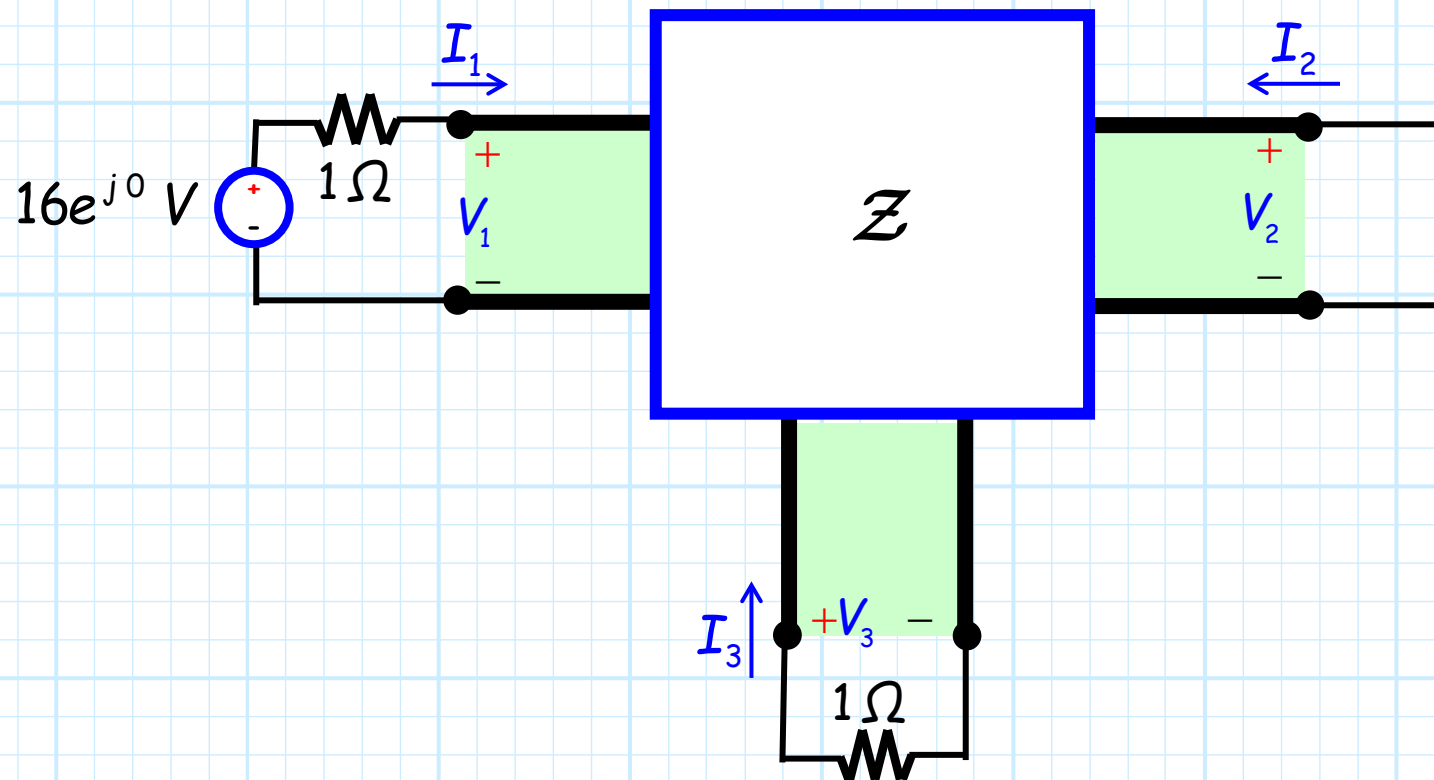


# Example: Using the Impedance Matrix

Consider this circuit:




Where the 3-port **device** is characterized by this **impedance matrix**:

$$\mathbf{Z}(\omega) = \begin{bmatrix} 2 & 1 & 2 \\ 1 & 1 & 4 \\ 2 & 4 & 1 \end{bmatrix} \Omega$$
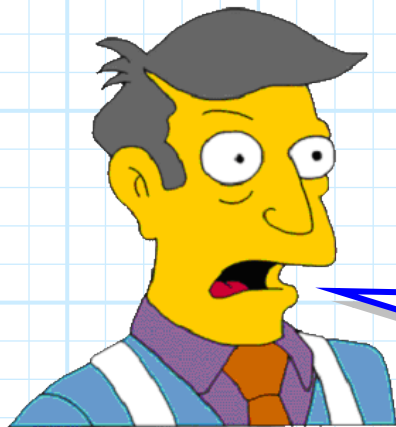
## The impedance matrix is a complete description!

Let's now determine all port **voltages**  $V_1, V_2, V_3$  and all **currents**  $I_1, I_2, I_3$ .



**Q:** *How can we do that—we **don't** know what the device is made of!*

*What's **inside** that box?*

**A:** We **don't** need to know what's inside that box!

We know its impedance matrix—and that **completely** characterizes the device (or, at least, characterizes it at **one** frequency).

Thus, we have **enough information** to solve this problem!

## The impedance matrix describes what's inside the box—but not what is outside!

From the impedance matrix we know:

$$V_1 = 2I_1 + I_2 + 2I_3$$

$$V_2 = I_1 + I_2 + 4I_3$$

$$V_3 = 2I_1 + 4I_2 + I_3$$

**Q:** Wait! There are 6 unknowns here.

Yet there are only 6 equations!?

**A:** True!



The impedance matrix describes the device in the box, but it does **not** describe the devices attached to it.

## One equation for each attached device

We require **three more equations** that describe the **three attached devices**!

1. Using KVL, the **source** at **port 1** is described by the equation:

$$V_1 = 16.0 - (1)I_1$$

2. The **short** circuit on **port 2** means that:

$$V_2 = 0$$

3. While the **load** on **port 3** leads to:

$$V_3 = -(1)I_3 \quad (\text{note the minus sign!})$$



**Now there are 6 equations and 6 unknowns!**

## The answers are complex numbers

**Combining** these 6 equations, we find:

$$V_1 = 16 - I_1 = 2I_1 + I_2 + 2I_3$$

$$\therefore 16 = 3I_1 + I_2 + 2I_3$$

$$V_2 = 0 = I_1 + I_2 + 4I_3$$

$$\therefore 0 = I_1 + I_2 + 4I_3$$

$$V_3 = -I_3 = 2I_1 + 4I_2 + I_3$$

$$\therefore 0 = 2I_1 + 4I_2 + 2I_3$$

**Solving**, we find (I'll let **you** do the algebraic details!):

$$I_1 = 7.0 e^{j0}$$

$$I_2 = 3.0 e^{j\pi}$$

$$I_3 = 1.0 e^{j\pi}$$

$$V_1 = 9.0 e^{j0}$$

$$V_2 = 0.0$$

$$V_3 = 1.0 e^{j0}$$