

# Maximum Power Transfer along a Transmission Line

**Q:** *I think I finally have this all figured out.*

*The power **delivered** by the source is equal to the **difference** of the **incident** and **reflected** power along the lossless transmission line:*

$$p_g^{del} = p^{inc} - p^{ref}$$

**A:** Yes, absolutely.

**Q:** *And by conservation of energy, this power is also that **absorbed** by the load:*


$$p_g^{del} = p^{inc} - p^{ref} = p_L^{abs}$$

**A:** I think I made that **quite clear**.

## All true!

**Q:** Further, the “matched” load  $Z_L = Z_0$  is precisely the load that reduces the **reflected** power to **zero**, so that:

$$p_g^{del} = p^{inc} = p_L^{abs}$$

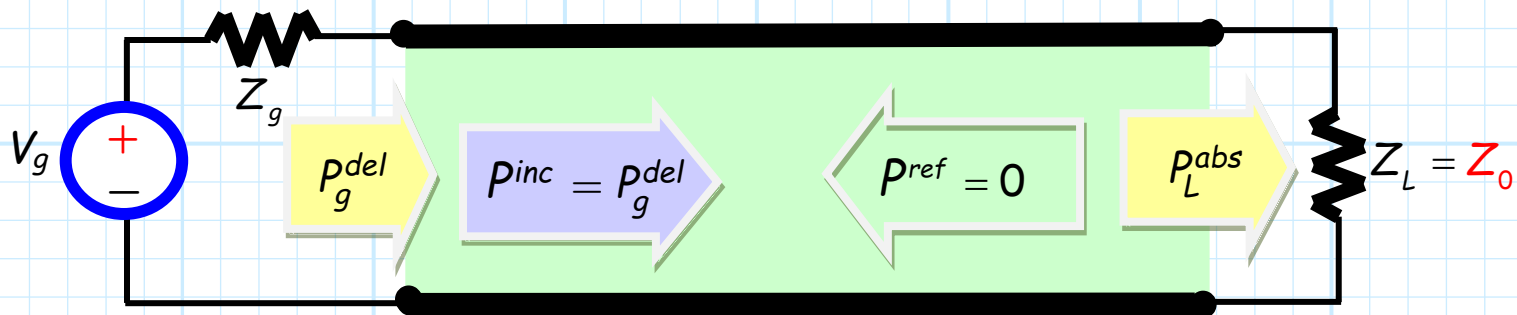

And thus for the case where  $Z_L = Z_0$ —but for **just** this case—the **incident** power is equal to the power **delivered** by the source.

**A:** And equal to the **power absorbed** by the load as well!!

## ACK! COMPLETELY FALSE!!!!

**Q:** And, since the reflected power is zero, the power absorbed by matched load  $Z_L = Z_0$  is maximized—it equals all the available power  $P_{avl}$  of the source, and so:

$$P_g^{del} = P^{inc} = P_L^{abs} = P_g^{avl}$$

Right?????

**A:** NO!!!!!!! This last statement is absolutely false!!!!!!



Yes, a matched load  $Z_L = Z_0$  will minimize (to zero) the reflected power  $P^{ref}$ .

➔ But, that will not (generally) maximize the absorbed/delivered power!

## The load affects both waves!

**Q:** Huh? Just *look* at the math (like you're *always* telling us to do!):

$$P_g^{del} = P^{inc} - P^{ref} = P_L^{abs}$$

**Why** would minimizing  $P^{ref}$  **not** maximize the values of  $P_g^{del}$  and  $P_L^{abs}$  ??

**A:** Remember, the value of load  $Z_L$  affects **both** the reflected ( $V_0^-$ ) and the **incident ( $V_0^+$ ) wave!!!**

$$P^{inc} = \frac{|V_0^+|^2}{2 Z_0} = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})|^2}$$


$$P^{ref} = P^{inc} |\Gamma_L|^2 = \frac{|V_g|^2}{2} \frac{Z_0 |\Gamma_L|^2}{|Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})|^2}$$

## A "matched" load minimizes both reflected and incident power

A "matched" load of  $Z_L = Z_0$  does minimize the reflected power ( $P_{ref} = 0$ ).


But, this same "matched" load does not maximize  $P_{inc}$ !

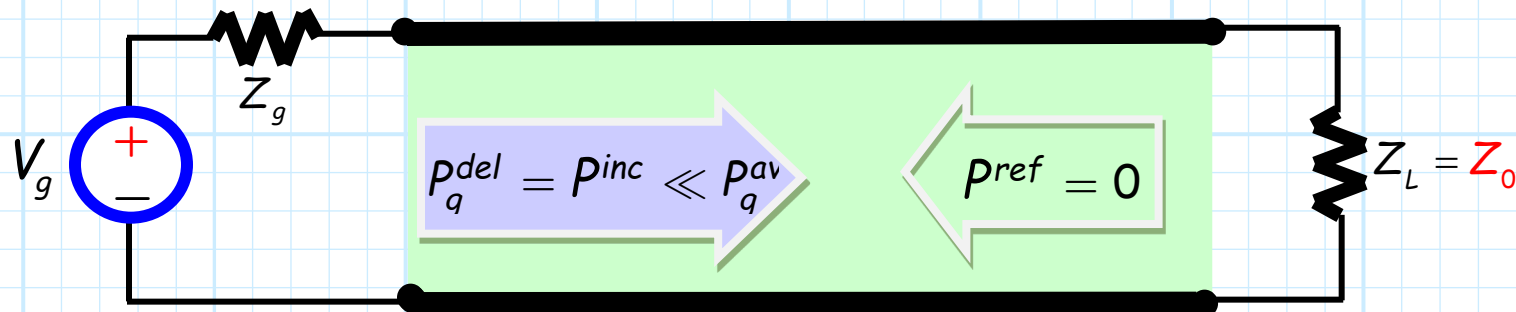In fact a "matched" load actually minimizes the incident power!


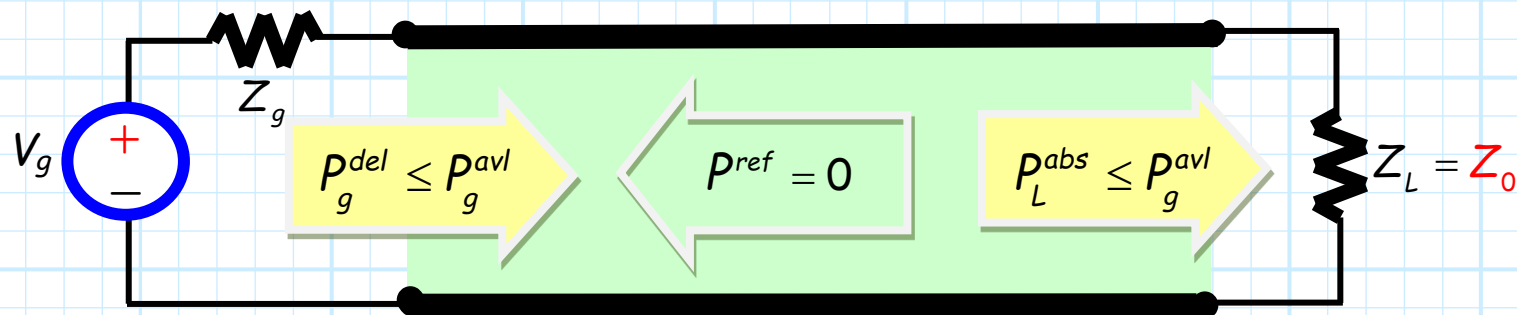
## Minimizing reflection does NOT maximize absorption!

This means that the power absorbed by a **matched load**—and thus the power **delivered** by the source—will generally be **less** than the **available power** of the source.



If  $Z_L = Z_0$ , then the reflected power is minimized ( $p^{ref} = 0$ ), but the absorbed power is (generally speaking) **not maximized** ( $p_L^{abs} < p_g^{avl}$ )!


## A reactive load maximizes both incident and reflected power

**Q:** So, the load  $Z_L$  that *maximizes its absorbed power* is instead the load that *maximizes its incident power*  $P^{inc}$  ????

**A:** Gosh no!

The load that maximizes the incident power is in fact a **reactive load**.

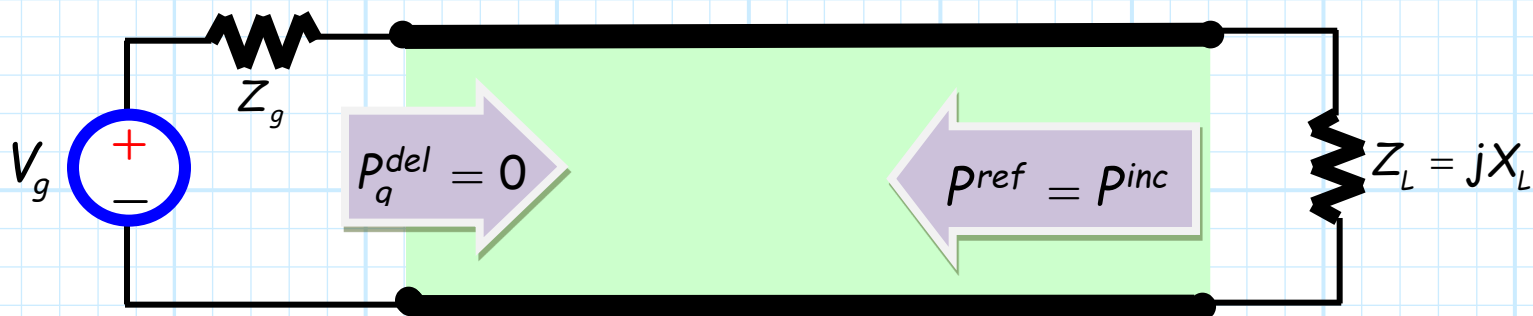➔ But a reactive load **cannot absorb** any energy at all!



The load that maximizes the **incident power** (i.e.  $Z_L = jX_L$ ) is (unfortunately) the same load that maximizes the **reflected power**!

## Not minimize reflected, nor maximize incident—maximize their difference!

**Q:** So, the load impedance  $Z_L$  that **maximizes** its absorbed power is **not** the value  $Z_L$  that **minimizes**  $P^{\text{ref}}$ .

**Nor** is it the value  $Z_L$  that **maximizes**  $P^{\text{inc}}$ .

So, just what load impedance  $Z_L$  **does** maximize its absorbed power?

**A:** The value of  $Z_L$  that **maximizes the difference** between  $P^{\text{inc}}$  and  $P^{\text{ref}}$ !

$$P_g^{\text{del}} = P^{\text{inc}} - P^{\text{ref}} = P_L^{\text{abs}}$$


**Q:** But what **specific value** of  $Z_L$  actually does that?


**A:** You know the answer!


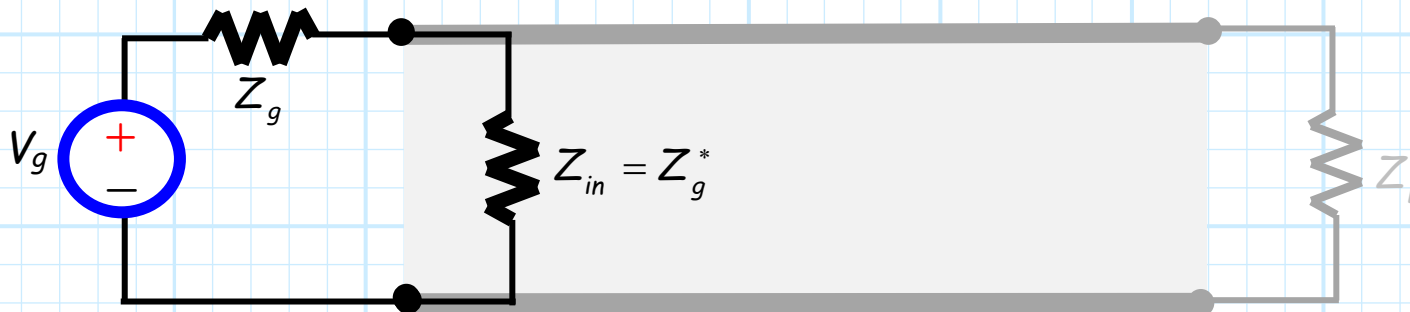
# Conjugate match maximizes absorbed power!


Recall that the **maximum** rate of energy absorption *i.e.*,  $P_L^{abs} = P_g^{avl}$  is achieved **only** if the **input impedance** of the terminated transmission line is equal to the **complex conjugate** of the source:

$$P_L^{abs} \quad (= P_g^{del}) = P_g^{avl} \quad \text{only if} \quad Z_{in} = Z_g^*$$


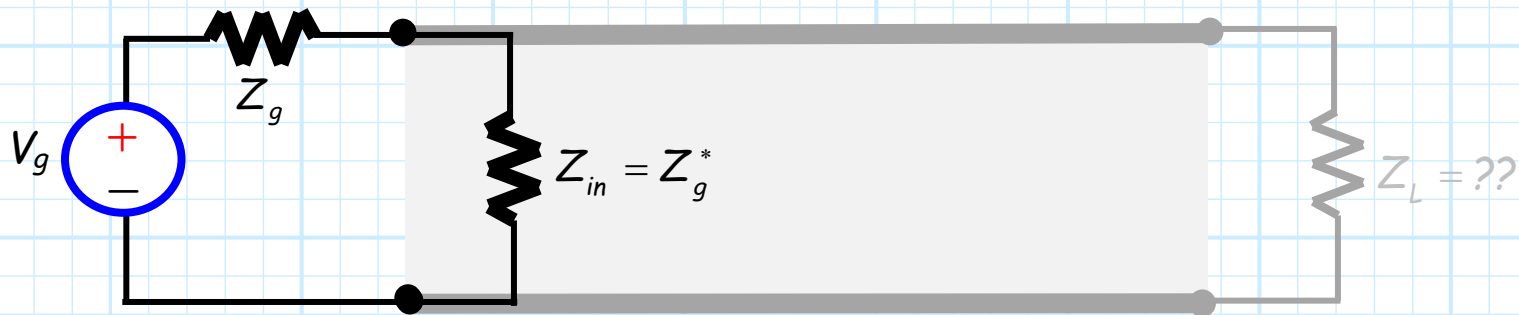
## Whatever this load is

Thus, the load that maximizes its absorbed power is **whatever** value of  $Z_L$  that results in  $Z_{in} = Z_g^*$ !!



Note this value of load impedance  $Z_L$  **depends on**:

1. the transmission line **characteristic** impedance  $Z_0$  .
2. the **source** impedance  $Z_g$  .
3. **and—most annoyingly—the line length  $\ell$  .**


# A "matched" load is **not** a conjugate match!

Note for a "matched" load  $Z_L = Z_0$ , the input impedance is likewise numerically equal to the characteristic impedance:

$$Z_{in} = Z_0 \quad \text{if} \quad Z_L = Z_0$$

But, this input impedance is **not typically the complex conjugate of the source impedance:**

$$Z_g^* \neq Z_0!!!!$$

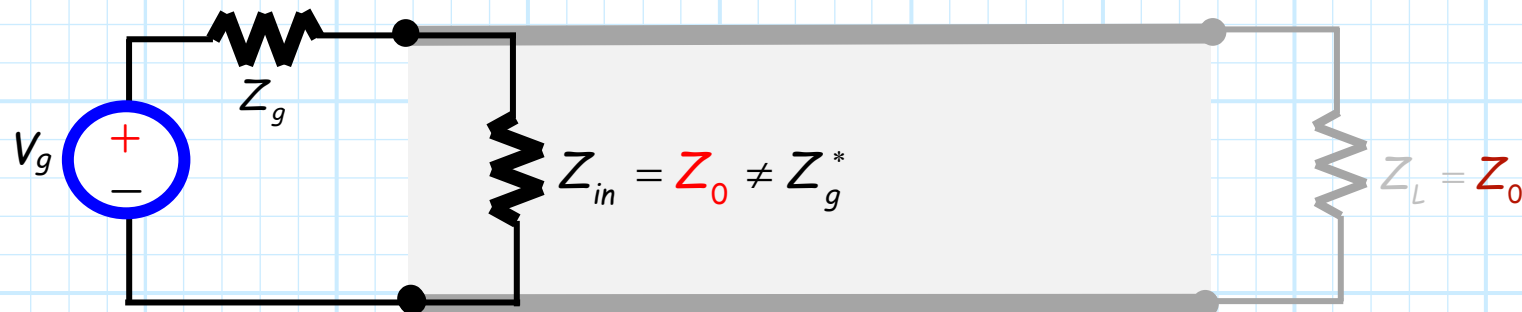


## A “matched” source is **not** a conjugate match either!

Likewise, for a “matched” source (where  $Z_g = Z_0$ )

But, this source impedance is **not** typically the **complex conjugate** of the input impedance:

$$Z_{in}^* \neq Z_0!!!!$$

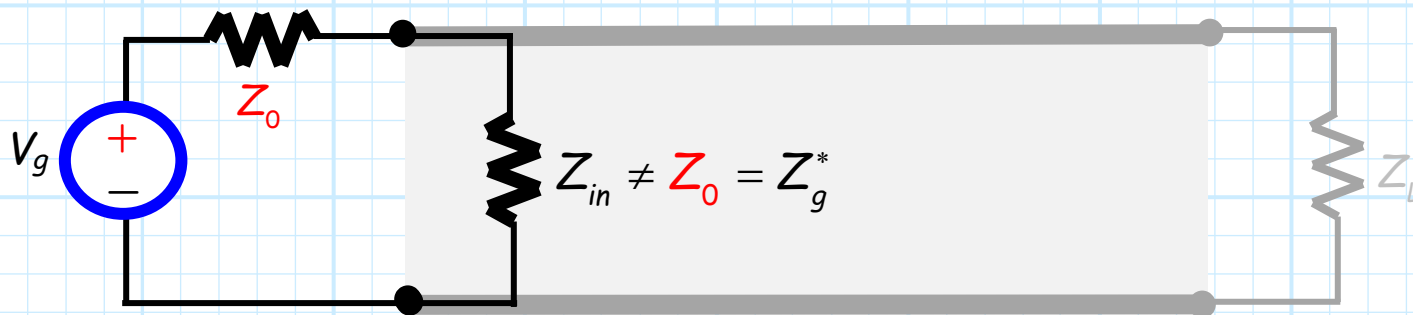

## ACK! AGAIN COMPLETELY FALSE!!!!

**Q:** It *seems* logical that for the *conjugate matched* case, the *incident* power should be equal to its *maximum* possible value—equal to the *available* power of the source:

$$P_{inc} = P_g^{avl} \quad \text{if} \quad Z_{in} = Z_g^* \quad \text{right ???}$$

**A:** Nope; this statement is completely **false** as well !!!!!!!!!!!!!!!



## Incident is greater than delivered!

Remember, when a **conjugate match** occurs, the **delivered** (and thus absorbed) power is **equal** to all the available power of the source:

$$P_g^{avl} = P_g^{del} = P_L^{abs} \quad \text{if} \quad Z_{in} = Z_g^*$$

But, remember also that (in general), the **incident** power is **greater** than the power **delivered/ absorbed**:

$$P^{inc} \geq P_g^{del} = P_L^{abs}$$


Recall that the **equality** ( $P^{inc} = P_g^{del} = P_L^{abs}$ ) occurs **only** when  $P^{ref} = 0$  (i.e., when  $Z_L = Z_0$ ).

And recall also that the **matched load** case  $Z_L = Z_0$  generally **does not** **create a conjugate match** ( $Z_{in} = Z_0 \neq Z_g^*$ )!
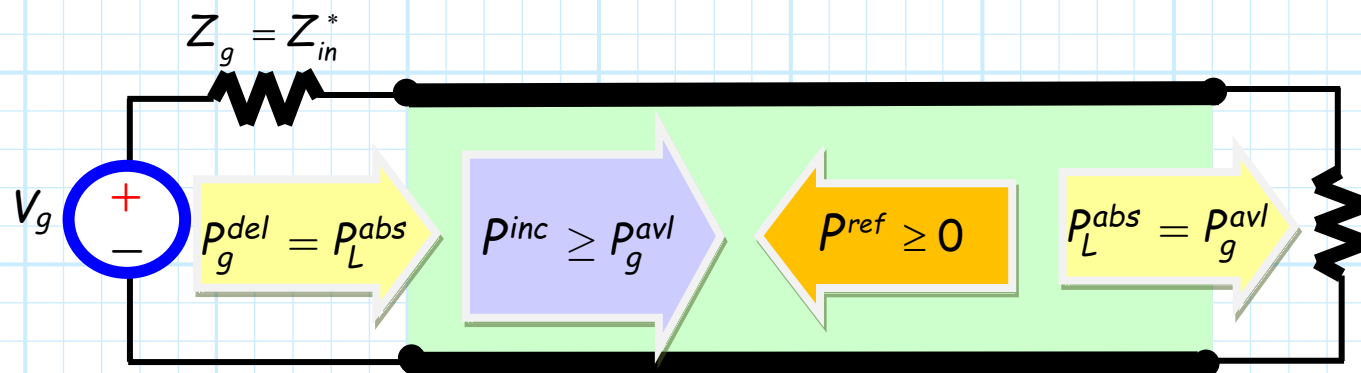
# So incident is greater than the available!!

We come to the conclusion that when a **conjugate match** occurs, the **incident** power is generally **greater** than the available power of the source:

$$P_{inc} \geq P_g^{avl} = P_g^{del} = P_L^{abs} \quad \text{if} \quad Z_{in} = Z_g^* \text{!!!!!!}$$



**Q:** Yikes! Doesn't this **violate** some sort of **conservation of energy** thing?

**A:** Nope.

## Relax, the net power does not violate conservation of energy

Although the **incident power** is **greater** than that **available** ( $P^{inc} \geq P_g^{avl}$ ), the **net power** ( $P^{net} = P^{inc} - P^{ref}$ ) will be **equal to**  $P_g^{avl}$  when a conjugate match is established.

Conservation of energy is **not violated!**

Moreover, we **frequently** find that the **incident power will exceed the power available** from the source—even when no conjugate match exists!

$$P^{inc} = \frac{|V_0^+|^2}{2 Z_0} = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})|^2}$$



## Weasel words: they're my specialty


**Q:** You peppered this discussion with *weasel words* like "generally".

*Might there be a situation where a "matched" load  $Z_L = Z_0$  indeed does absorb all available power?*

**A:** Sure!

Remember, if the load is a "matched" load, then the absorbed power is equal to the incident power (the reflected power being zero and all):
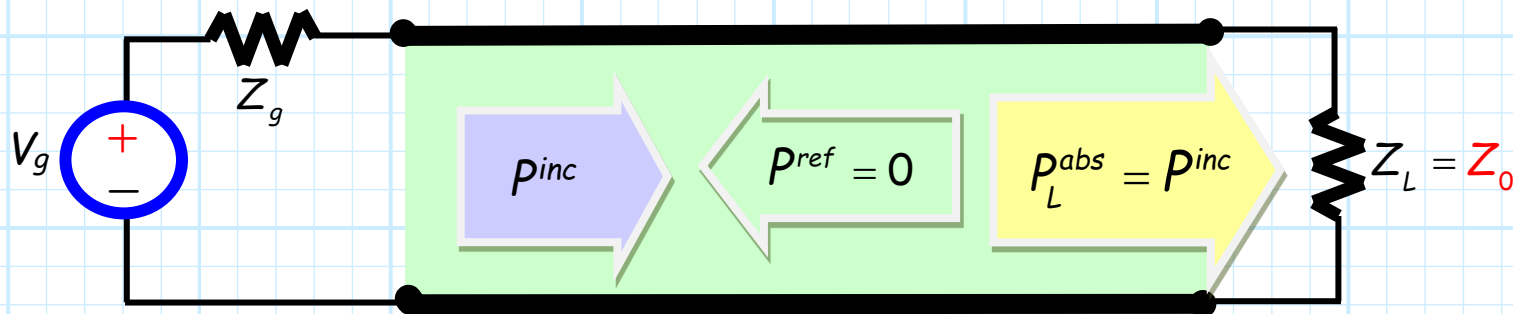
$$p_L^{abs} = p^{inc} \quad \text{if} \quad Z_L = Z_0$$



## Deja Vu

Thus, the power **absorbed** by the “**matched**” load can be equal to the **available** power of the source **only** if the **incident** power is **equal** to the **available** power of the source!

$$\text{If } Z_L = Z_0, \text{ then } P_L^{abs} = P_g^{avl} \text{ only if } P^{inc} = P_g^{avl}$$

**Q:** Hey, didn't we discuss this case **earlier**?

*Isn't the incident power equal to the available power when the source impedance is “matched” to the transmission line (i.e.,  $Z_g = Z_0$ )?*

**A:** Precisely!

## Matched source and matched load

For a “**matched**” source, the **incident** power of the transmission line will be equal to the **available** power of the source:

$$P^{inc} = P_g^{avl} \quad \text{if} \quad Z_g = Z_0$$

And so if the **load** is likewise “**matched**”, **all this incident power** will be **absorbed** by the source:

$$P_g^{avl} = P^{inc} = P_L^{abs} \quad \text{if} \quad Z_g = Z_0 \quad \text{and} \quad Z_L = Z_0$$

Perhaps most importantly, this is true **regardless of transmission line length  $\ell$ !**

## It's THE ideal situation!

Thus, the case of the “matched” load **AND** “matched” source is effectively the **ideal** case for transmission line interconnection.

Note that a **conjugate match is established**—such that **all** available source power is connected to the load.

→ And, it's all independent of line length  $\ell$ !

