

EECS 622: Homework #12

October 9, 2025


Grant Saggars

Problem 1

The two lossless matching networks in the circuit below were designed such that **maximum power transfer** is achieved—**regardless of length ℓ** of the transmission line!

In other words, line length ℓ can be changed **without affecting** this maximum power transfer.

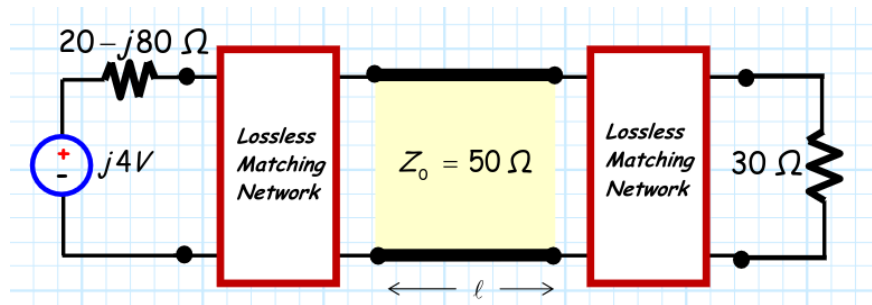Hint: The answers to the following questions are **not** particularly difficult to determine. However, you must provide **detailed, explicit, and complete justification** for all your answers!



A. Determine the **power absorbed** by the 30Ω load.

Solution:


The fact that this is lossless ensure that power delivered equals power absorbed. The fact that this is matched ensures that all available power is absorbed. The existence of the load-side matching network also guarantees there are no reflections. Therefore;

$$P_g^{avl} = P_L^{del} = P_L^{abs}$$

Where,

$$P_g^{avl} = \frac{|V_g|^2}{8 \cdot R_g} = \frac{|j4|^2}{8 \cdot 20} = 10 \text{ mW}$$

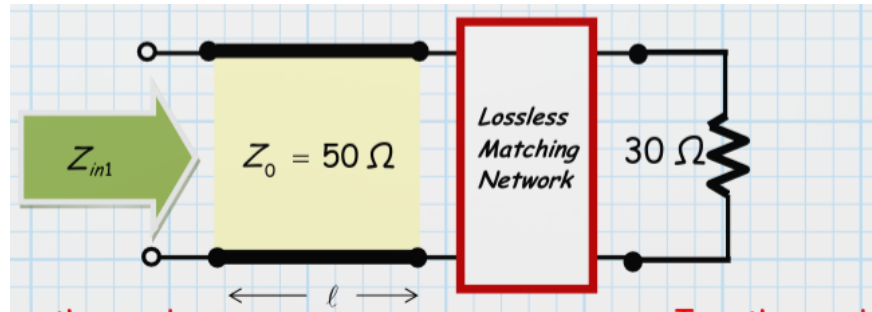B. Determine the **input impedance** Z_{in1} of this part of the circuit:




Solution:

If Z_{in1} is the equivalent resistance seen by the source side lossless matching network, we know that it must be matched to the line characteristic impedance, so

$$Z_{in1} = Z_0 = 50 \, \Omega$$

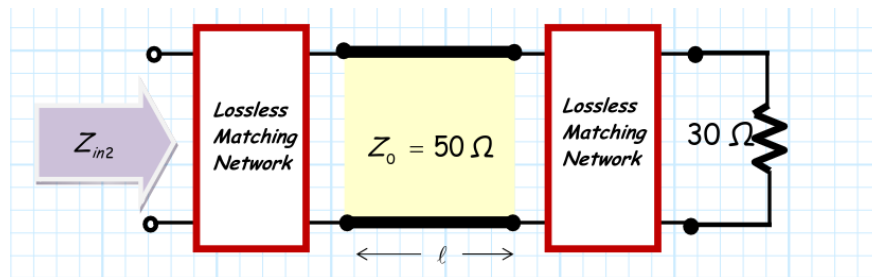C. Determine the **input impedance** Z_{in2} of this part of the circuit.




Solution:

If we look at the input impedance seen by the source, including the lossless matching network, we know that this must equal

$$Z_{in2} = Z_g^* = 20 + j80 \, \Omega$$

Because there must be a conjugate match everywhere to guarantee maximum power transfer.

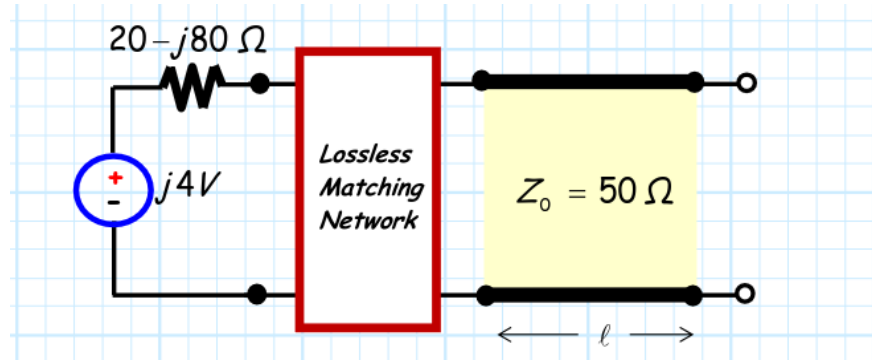D. Determine the **output impedance** Z_{out1} of the Thevenin's equivalent for this part of the circuit.




Solution:

The load side matching network will match to the transmission line characteristic impedance Z_0 , so this will have

$$Z_{out1} = Z_0 = 50 \Omega$$

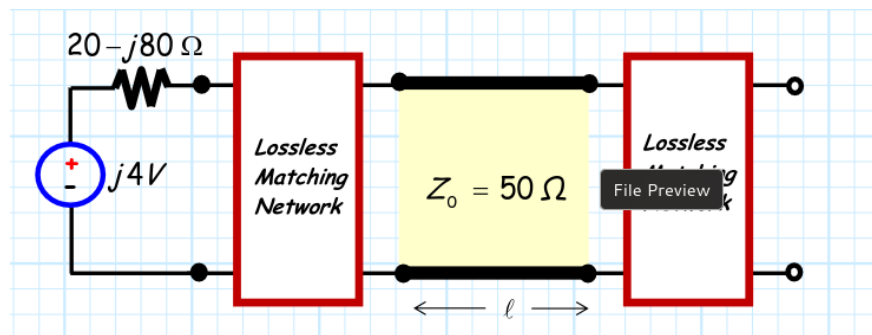E. Determine the **output impedance** Z_{out2} of the Thevenin's equivalent for this part of the circuit.



Solution:

Similarly to C., there must be a conjugate match between all of the components in the figure and the load impedance in order to guarantee maximum power delivery. Therefore,


$$Z_{out2} = Z_L^* = 30 \Omega$$

Problem 2

In the circuit below, the **source delivers** energy at a rate equal to its **available power**.

The **squared-magnitude of the load reflection coefficient** is

$$|\Gamma_L|^2 = 0.375.$$

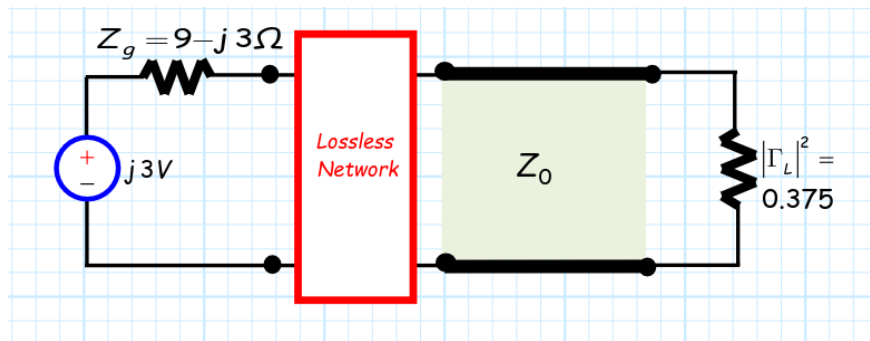

Determine the power incident on the load Γ_L

Provide **explicit and detailed justification** for your answer.

Your grade will **primarily** depend on this justification.

Solution:

Because the source is lossless, all available power is delivered. We clearly do not have a matched load, since $\Gamma_L \neq 0$. We can however express this as:

$$P^{del} = P^{inc} - P^{ref}$$

$$P^{del} = P^{inc} (1 - |\Gamma_L|^2)$$

$$P^{inc} = \frac{P^{del}}{1 - |\Gamma_L|^2}$$

Now, we know that $P_g^{avl} = P_g^{del}$, so we can complete this:

$$P^{inc} = \frac{1}{1 - |\Gamma_L|^2} \frac{|V_g|^2}{8 \cdot R_g} \quad (\text{since } P_g^{avl} = \frac{|V_g|^2}{8R_g})$$

$$P^{inc} = \frac{1}{1 - |0.375|^2} \frac{|j3|^2}{8 \cdot 9}$$

$$P^{inc} \approx 14.5 \text{ mW}$$