

¹ Lab 2: Thevenin Equivalent Circuits

² **Grant Saggars**
PHSX 536

³ February 8, 2025

⁴ **Abstract**

⁵ In this experiment, I investigate the Thevenin resistance [1] of a
⁶ "complex circuit" by experimental means. By modifying the circuit
⁷ using a potentiometer, I am able to fit values for Thevenin equivalent
⁸ components with high precision. I then compare results with mea-
⁹ surements, simulation, and theoretical predictions for such behavior.
¹⁰ My results demonstrate how fitting parameters to a data often results
¹¹ in lower uncertainty than direct measurement, although not necessar-
¹² ily higher accuracy. Furthermore, it is shown that results found using
¹³ the different techniques provide statistically similar results.

¹⁴ **1 Introduction**

¹⁵ The Thevenin equivalent circuit is an essential introductory concept in
¹⁶ circuit design, and in this experiment, I aim to explore it using the circuit
¹⁷ shown in figure 1, by determining the Thevenin equivalent resistance (R_{th})
¹⁸ and Thevenin equivalent voltage (V_{th}) for R_4 . This was done in four key ways.
¹⁹ First, I perform theoretical predictions using the measured properties of my
²⁰ circuit components and propagating error. Second, I measured only V_{th} with
²¹ a multimeter (Fluke 179). R_{th} could not be measured in this way. Finally,
²² I use a variable resistor in parallel with R_4 , as shown in figure 2, to use the
²³ linear relation between current and voltage to fit a line with parameters R_{th}
²⁴ and V_{th} . I also perform simulation using the software package "LTSpice," for
²⁵ which I can fit in the same way as I did on measured data to compare.

²⁶ **1.1 Calculations of Thevenin Equivalent Values**

Calculating theoretical Thevenin equivalent resistance is rather straightforward. For R_{th} , we simply find the equivalent resistance of the circuit, replacing batteries with short circuits. In the case of the circuit shown in figure 1, this is as follows:

$$R_{th} = \left(\left(\left(\frac{1}{R_1} + \frac{1}{R_3} \right)^{-1} + R_2 \right)^{-1} + \frac{1}{R_4} \right)^{-1}.$$

²⁷ Meanwhile, Thevenin equivalent voltage is said to be the voltage across
²⁸ the device in question. In the case of this experiment, this is R_4 , so by mesh
²⁹ analysis I arrive at the following equations for this voltage drop:

$$\begin{aligned} -R_1I_1 - R_3I_1 + R_3I_2 &= V \\ -R_2I_2 - R_4I_2 - R_3I_2 + R_3I_1 &= 0 \\ V_{th} &= R_4I_2 \end{aligned}$$

Solving this system (see appendix A) gives

$$V_{th} = R_4 \cdot \left(\frac{VR_3}{R_1R_2 + R_1R_3 + R_1R_4 + R_2R_3 + R_3R_4} \right)$$

³⁰ **1.2 Fitting of Thevenin Equivalent Values**

³¹ The primary objective of this experiment is to determine precise values
³² for V_{th} and R_{th} by fitting a linear model to the measured data. This is
³³ achieved by introducing a potentiometer in parallel with R_4 , allowing data
³⁴ collection that follows Ohm's Law. The circuit's behavior can be described
³⁵ by the linear equation:

³⁶
$$V = -R_{th}I + V_{th}$$

³⁷ Wherein the slope corresponds to $-R_{th}$ and the y-intercept represents
³⁸ V_{th} .

³⁹ Additionally, it is of note that the power dissipation of the potentiometer
⁴⁰ is of high concern. The potentiometer available is rated to handle a maximum
⁴¹ 0.5 mW power dissipation, so prior to applying a voltage to it, I calculated
⁴² the power dissipation and concluded that it is impossible to damage a ca-
⁴³ pacitor with this circuit configuration. My calculations for this are included
⁴⁴ in appendix C.

⁴⁵ 2 Experimental Technique

⁴⁶ Prior to constructing my circuit, I take measurements of all quantities of
⁴⁷ resistance and voltage and their uncertainties using a Fluke 179 multimeter;
⁴⁸ the results of which can be found in table D. Then, on my breadboard, I
⁴⁹ construct the circuit shown in figure 1. I am able to directly measure voltage
⁵⁰ across R_4 , the Thevenin equivalent voltage.

⁵¹ Fundamental to this experiment is the fitting of data collected by use of
⁵² a potentiometer, as discussed in section 1. This was done by inserting a po-
⁵³ tentiometer in parallel, and connecting a voltmeter across R_4 and a ammeter
⁵⁴ in series between R_2 and R_4 (these are not true voltmeters or ammeters, but
⁵⁵ rather multimeters in these respective modes). The resulting circuit is shown
⁵⁶ in figure 2. Following, I carefully collect data from the two multimeters for
⁵⁷ linearly spaced values in my potentiometer. I observe a weighting of data
⁵⁸ points in the low current, high voltage region of the plot, so I collect a greater
⁵⁹ number of data points in the low resistance range.

⁶⁰ Additionally, prior to measurement, the terminals of my potentiometer
⁶¹ broke. I found that my new potentiometer varied slightly in resistivity when
⁶² compared to my previous one. To ensure consistent results in my experiment,
⁶³ I carefully measured resistance using the Fluke 179 multimeter as a function
⁶⁴ of potentiometer index, and I have included my results in fitting parameters
⁶⁵ for it in appendix B.

Schematic of the Base Circuit with Potentiometer Measurements

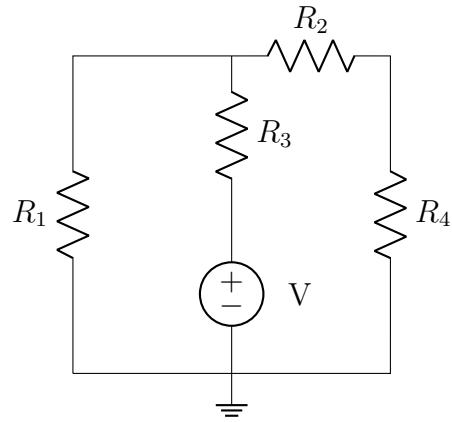


Figure 1: The simple circuit used for calculation and measurement of Thevenin equivalent values, including the voltmeter across R_4 and ammeter between R_2 and R_4 .

**Circuit Modified with
a Potentiometer**

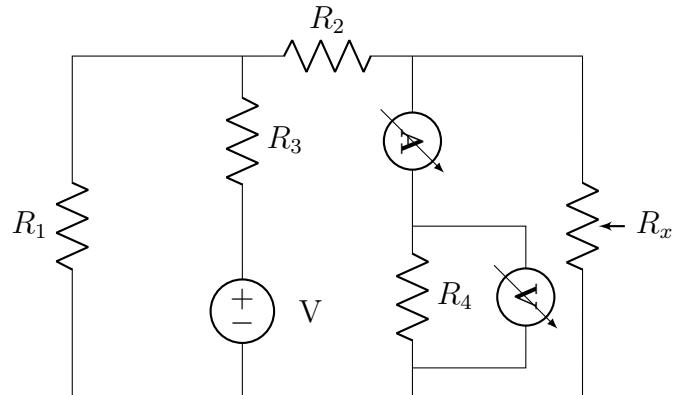


Figure 2: Circuit diagram illustrating the circuit used to fit current and voltage to determine Thevenin resistance and voltage. It is in parallel with the part of the circuit we intend to find Thevenin equivalent values for. The locations of the ammeter and voltmeter (features on the Fluke 179 multimeter) are inserted as well.

Photograph of my Circuit Modified with a Potentiometer

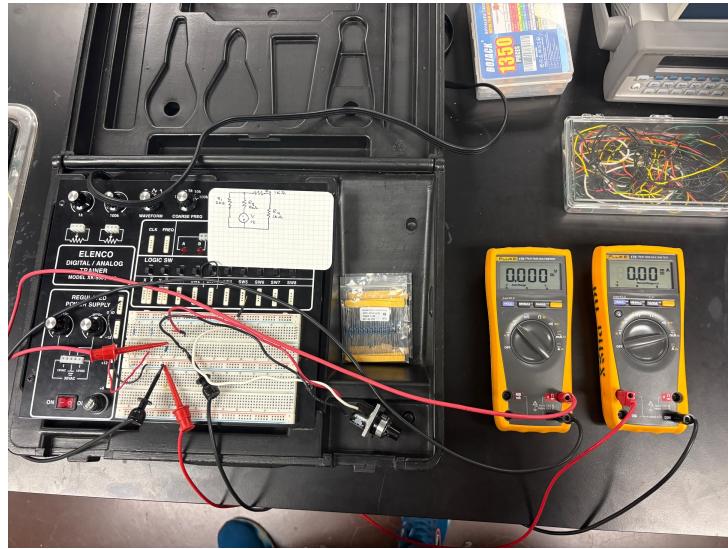


Figure 3: A photograph of figure 2 on my breadboard. Fluke 179 multimeters are shown connected to measure voltage and current as discussed in section 2.

66 3 Systematic Uncertainty Analysis

67 In the measurements disclosed in table D, the multimeter has an asso-
68 ciated systematic uncertainty of $0.09\% + 1$ least significant digit for DC
69 voltages in these ranges, and an uncertainty of $1.0\% + 3$ least significant
70 digits for DC current. This results in rather accurate measurements of data
71 to be used for fitting, calculation, and direct measurement of V_{th} , and I argue
72 that systematic uncertainty is extremely low due to the multimeter. For the
73 purposes of my calculations, I propagate my error numerically using Julia's
74 excellent physical measurements library (see the code provided in the same
75 directory as this writeup).

76 To eliminate the effects of weighting towards high resistances, I resample
77 my data to be equally spaced the current axis. The resulting data is unreli-
78 able in uncertainty, due to it not being systematically gathered. Regardless,
79 it serves to reliably demonstrate that my original fitted data describes the

80 underlying parameters well because the error between the two is very small.

81 I propose that the most significant source of error in this writeup is statistical in nature, and arises as a consequence of tolerance in my potentiometer.
82 Our potentiometer is rated for $\pm 5\%$ tolerance, resulting in very significant
83 fluctuations in measured values, particularly for the low resistance, high cur-
84 rent and voltage range. I believe that this deviation at low resistance is the
85 primary reason my results have significant statistical deviation from predic-
86 tion, measurement, and simulation. It could be eliminated by taking many
87 more samples at low resistance, or by accounting for this uncertainty statis-
88 tically.
89

90 4 Results

91 I present data in table 1 which, with low uncertainty, accurately estimates
92 values for R_{th} and V_{th} for several methods of measurement. More detail in
93 the fitting of my Thevenin parameters is also shown in fig 4. For most
94 purposes, I find that any of the presented methods for estimating R_{th} and
95 V_{th} produce measurements with very high precision, and it is observed that
96 the fitted results produce the lowest uncertainty. This is not to say that it is
97 the most characteristic of the actual values, as the estimated value is highly
98 dependent on tolerance. Propagation of this to the uncertainty, and the
99 collection of many more data points at low resistances in the potentiometer
100 would certainly reduce the error in this.

To compare my results, I compute z-scores for my fitted data as follows, using measurement error to normalize.

$$\frac{|R_{th, \text{ fit}} - R_{th, \text{ theory}}|}{\text{error}} = \frac{|66.67 - 68.58|}{6.237} = 0.3062$$

$$\frac{|V_{th, \text{ fit}} - V_{th, \text{ theory}}|}{\text{error}} = \frac{|1.979 - 1.964|}{0.010} = 1.5$$

And I do the same for the fitted V_{th} and measured V_{th} .

$$\frac{|V_{th, \text{ fit}} - V_{th, \text{ meas}}|}{\text{error}} = \frac{|1.979 - 1.969|}{0.010} = 1.0$$

It is also useful to compare my measured value to the theoretical value, where it is observed that there is extremely low standard deviation between

the two.

$$\frac{|V_{\text{th, meas}} - V_{\text{th, theory}}|}{\text{error}} = \frac{|1.969 - 1.964|}{0.018} = 0.28$$

Again, I repeat this for my simulated data, using propagated uncertainty in my calculations as the error.

$$\frac{|R_{\text{th, simulated}} - R_{\text{th, theory}}|}{\text{error}} = \frac{|68.58 - 68.5|}{0.47} = 0.38$$

$$\frac{|V_{\text{th, simulated}} - V_{\text{th, theory}}|}{\text{error}} = \frac{|1.983 - 1.964|}{0.020} = 882.85$$

Summary of Data

Parameter	Theoretical Value	Measured Value	Fitted Value	Simulated Value
Thevenin Resistance R_{th}	$68.58 \pm 0.47 \Omega$	N/A	$66.67 \pm 6.23 \Omega$	68.58Ω
Thevenin Voltage V_{th}	$1.964 \pm 0.02 \text{ V}$	$1.969 \pm 0.018 \text{ V}$	$1.979 \pm 0.010 \text{ V}$	1.983 V

Table 1: The results, which demonstrate very similar values in the estimation of R_{th} and V_{th} .

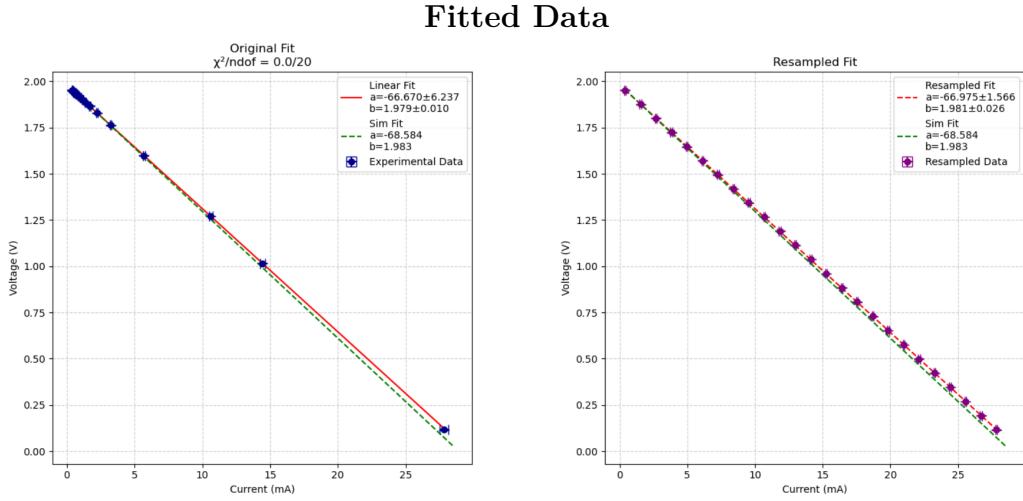


Figure 4: A comparison between fitted data, a resampled copy of the data on the right, and simulated data in both. Slope is given by $-R_{th}$, and intercept is given by V_{th} . The resampled data is shown to demonstrate that the data on the left is independent of the weighting of samples. The fitted results represent the true value of both resistance and voltage with very high accuracy; more so than simulated and directly measured results, and are presumably limited primarily by the tolerances of the film-metal resistors. Such an issue could be alleviated with a greater number of samples to average out the error caused by variance in the readings, or by directly accounting for it in uncertainty.

101 5 Summary

102 I present my work on the determination of Thevenin equivalent param-
 103 eters, R_{th} and V_{th} , which are essential to a basic understanding of circuit
 104 behavior. I do so by employing several methods, including theory, simula-
 105 tion, direct measurement by multimeter, and by fitting. All methods result
 106 in estimations of the parameters which are very precise, with low statistical
 107 uncertainty when applicable. I expected the fitted value to have the smallest
 108 uncertainty, which is what is observed; however, this does not necessarily
 109 imply that it is the most characteristic of the actual parameter. This is due
 110 largely to unaccounted for effects of potentiometer tolerance, which result in
 111 variation in measurements at low resistances. It can be alleviated in future

₁₁₂ work by taking more measurements at low resistances, where the effects of
₁₁₃ resistive tolerance are greatest, or by directly accounting for it in calculation
₁₁₄ of uncertainty.

₁₁₅ References

- ₁₁₆ [1] Wikipedia contributors. Thévenin's theorem — Wikipedia, the free en-
₁₁₇ cyclopedia. https://en.wikipedia.org/w/index.php?title=Th%C3%A9venin%27s_theorem&oldid=1260319611, 2024. [Online; accessed 6-
₁₁₉ February-2025].

₁₂₀ Appendices

₁₂₁ A Mathematical Work

₁₂₂ I have the system of equations, which are solved as follows:

$$\begin{aligned} -R_1I_1 - R_3I_1 + R_3I_2 &= V \\ -R_2I_2 - R_4I_2 - R_3I_2 + R_3I_1 &= 0 \\ V_{th} &= R_4I_2 \end{aligned}$$

$$-R_3I_1 + (R_2 + R_4 + R_3)I_2 = 0$$

$$I_2 = \frac{R_3I_1}{R_2 + R_4 + R_3}$$

$$(R_1 + R_3)I_1 - R_3 \left(\frac{R_3I_1}{R_2 + R_4 + R_3} \right) = V$$

$$I_1 \left[(R_1 + R_3) - \frac{R_3^2}{R_2 + R_4 + R_3} \right] = V$$

$$I_1 = \frac{V}{(R_1 + R_3) - \frac{R_3^2}{R_2 + R_4 + R_3}}$$

$$I_2 = \frac{R_3V}{(R_2 + R_4 + R_3)(R_1 + R_3) - R_3^2}$$


$$I_2 = \frac{R_3V}{R_1R_2 + R_1R_4 + R_1R_3 + R_2R_3 + R_3R_4}$$

$$V_{th} = \frac{R_3R_4V}{R_1R_2 + R_1R_3 + R_1R_4 + R_2R_3 + R_3R_4}$$

$$V_{th} = R_4 \cdot \left(\frac{VR_3}{R_1R_2 + R_1R_3 + R_1R_4 + R_2R_3 + R_3R_4} \right)$$

¹²³ B Potentiometer Fitting

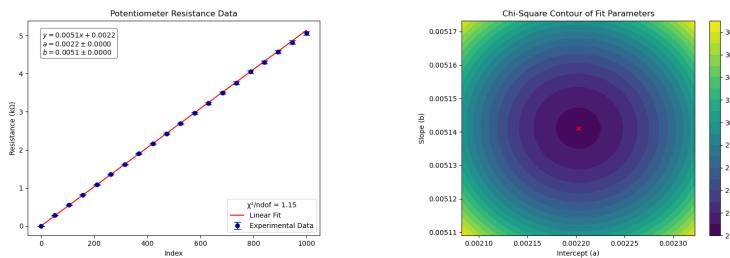¹²⁴ It was necessary to fit new values to my potentiometer in this experiment.



¹²⁵ **C Verification of Power Dissipation in Potentiometer**

¹²⁶

To ensure the safety of the potentiometer, we cannot dissipate more than 0.5mW of power across it. To avoid this, I will calculate what resistance I can go up to before damaging it. We have power dissipated given as:

$$P = I^2 R$$

for DC circuits. Since I varies as a function of resistance, we express it as:

$$I = \frac{V_{th}}{R_{th} + R}$$

Substituting this into the power equation:

$$P = \left(\frac{V_{th}}{R_{th} + R} \right)^2 R$$

Given that we can only dissipate 0.5 mW, we set up the equation:

$$0.5 \times 10^{-3} = \frac{V_{th}^2}{(R_{th} + R)^2} R$$

Multiplying both sides by $(R_{th} + R)^2$ to clear the fraction:

$$0.5 \times 10^{-3} (R_{th} + R)^2 = V_{th}^2 R$$

Expanding and rearranging:

$$\begin{aligned} R^2 + 2R_{th}R + R_{th}^2 &= \frac{V_{th}^2}{0.5 \times 10^{-3}} R \\ R^2 + (2R_{th} - \frac{V_{th}^2}{0.5 \times 10^{-3}})R + R_{th}^2 &= 0 \end{aligned}$$

Solving for R using the quadratic formula:

$$\begin{aligned} R &= \frac{-(2R_{th}) \pm \sqrt{(2R_{th})^2 - 4R_{th}^2}}{2} \\ R &= R_{th} \pm \sqrt{\frac{V_{th}^2}{0.5 \times 10^{-3}} - R_{th}^2} \end{aligned}$$

¹²⁷ This gives the maximum resistance R before the power dissipation exceeds 0.5mW. In our configuration, this gives an imaginary value, which implies we ¹²⁸ could not possibly dissipate this much power.

¹³⁰ **D Raw Data**

Measurements of Component Values

Component	Measured Value
PSU Voltage	12.12 ± 0.03 V
R_1	219.9 ± 2.0 Ω
R_2	101.2 ± 1.0 Ω
R_3	217.8 ± 2.0 Ω
R_4	101.7 ± 1.0 Ω
V_{th}	1.969 ± 0.019 V

Table 2: Measurements taken from the Fluke 179 multimeter. This is the source data used for all calculations and simulations.

Measurements of Voltage and Current for Varying Resistance on Potentiometer

Index	Current (mA)	Voltage (V)
999	-0.47 ± 0.03	1.948 ± 0.002
946	-0.40 ± 0.03	1.952 ± 0.002
893	-0.42 ± 0.03	1.950 ± 0.002
841	-0.45 ± 0.03	1.949 ± 0.002
788	-0.48 ± 0.03	1.947 ± 0.002
736	-0.52 ± 0.04	1.944 ± 0.002
683	-0.55 ± 0.04	1.941 ± 0.002
630	-0.60 ± 0.04	1.939 ± 0.002
578	-0.65 ± 0.04	1.935 ± 0.002
525	-0.71 ± 0.04	1.931 ± 0.002
473	-0.79 ± 0.04	1.926 ± 0.002
420	-0.88 ± 0.04	1.920 ± 0.002
368	-1.01 ± 0.04	1.912 ± 0.002
315	-1.17 ± 0.04	1.900 ± 0.002
262	-1.39 ± 0.04	1.886 ± 0.002
210	-1.69 ± 0.05	1.867 ± 0.002
157	-2.24 ± 0.05	1.830 ± 0.002
105	-3.25 ± 0.06	1.763 ± 0.002
52	-5.70 ± 0.09	1.599 ± 0.002
20	-10.62 ± 0.14	1.272 ± 0.001
10	-14.44 ± 0.17	1.016 ± 0.001
0	-27.84 ± 0.31	0.115 ± 0.001

Table 3: Measured current and voltage values with their respective errors. Data was taken across a range of resistances, designated by the index on the potentiometer. From this, I obtain my fitting results.