


EECS 622: Homework #4

September 14, 2025


Grant Saggars

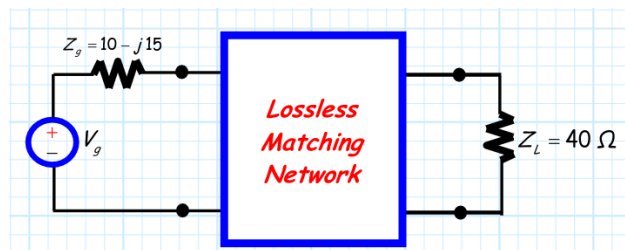Problem 1


A lossless matching network was properly constructed to match a source with parameters V_g and $Z_g = 10 - j15\Omega$ to a load $Z_L = 40\Omega$:



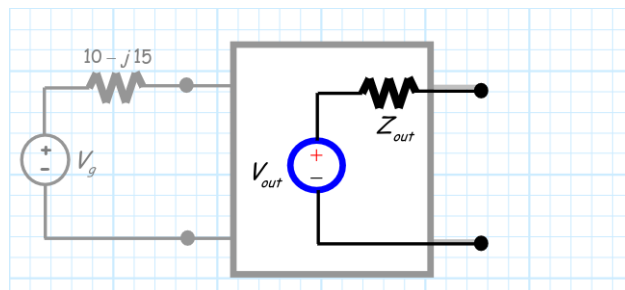If we disconnect the load from the matching network, we find that we have a new equivalent source (the original source followed by the matching network), with parameters V_{out} and Z_{out} :



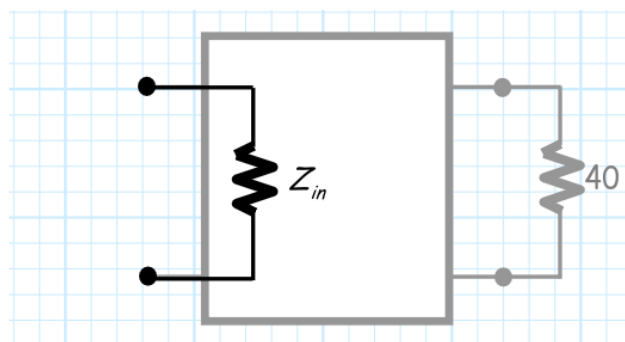Likewise, if we disconnect the source from the matching network, we find an input impedance (the matching network followed by the load) of Z_{in} (turn the page!!):



1. Determine the impedance values Z_{in} and Z_{out} .

Solution:

We design a matching network for the express purpose of setting the following relationship,

$$\begin{cases} Z_g = Z_{\text{in}}^* = 10 + j15 \, \Omega \\ Z_L = Z_{\text{out}}^* = 40 \, \Omega \end{cases}$$

2. Say the load Z_L absorbs energy at a rate of 800 mW. Determine then the value $|V_g|$.

Solution:

Because this is a *lossless* matching network, we may exploit the following invariance to determine the magnitude $|V_g|$.

$$P_g^{\text{avl}} = P_L^{\text{abs}} \quad (\text{Lossless})$$

$$\frac{|V_g|^2}{8R_g} = P_L^{\text{abs}} \quad (\text{Known expression for } P^{\text{avl}})$$

$$|V_g| = \sqrt{(8R_g)P_L^{\text{abs}}} \quad (\text{Algebra})$$


$$|V_g| = 8 \, \text{V}$$

Note: $1 \, \Omega = 1 \frac{\text{V}^2}{\text{W}}$.

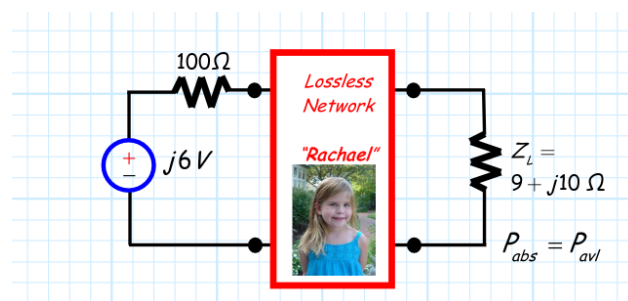Problem 2

A promising young engineer has designed a lossless matching network.

The design matches a specific source (with $Z_g = 100\Omega$) to a specific load impedance $Z_L = 9 + j10\Omega$.




The engineer tests the design in the lab, by measuring the power absorbed by the load Z_L .

The engineer is very happy, because the design worked perfectly-the power absorbed by the load is equal to the power available from the source.

The engineer is so happy with the design that the engineer gives the matching network a name-Rachael.

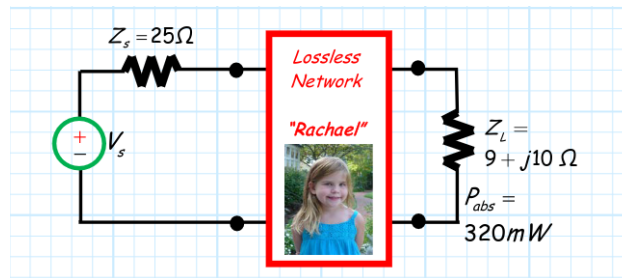Now, the engineer removes the source, and replaces it with a completely new one (i.e., $V_s \neq j6$ and $Z_s = 25\Omega$) :



Note however, that both the load $Z_L = 9 + j10\Omega$, and the lossless network "Rachael", remain completely unchanged.

The engineer now measures the power absorbed by the load $Z_L = 9 + j10\Omega$, and finds that it is 320 mW .

Determine the magnitude $|V_s|$ of this new source.

Provide explicit justification for your answer.

Solution:

Because power on the load side was not changed, we are fortunate to have the same Z_{in} which is notably not a conjugate match.

$$I = \frac{V_s}{Z_g + Z_{in}} = \frac{V_s}{125}$$

Power is simply:

$$P_{in, rms} = \frac{1}{2} |I|^2 Z_{in} = \frac{|V_s|^2 \cdot 100}{2(125)^2}$$

Since it is lossless, this is also the power absorbed, and I can therefore express $|V_s|$:

$$P_{abs} = 0.320 = \frac{2|V_s|^2}{625} \implies |V_s| = 10$$