

EECS 622: Homework #6

September 25, 2025

Grant Saggars

Problem 1

The **reflection coefficient function** along a transmission line is:

$$\Gamma(z) = j 0.5 e^{+j(\pi)z}$$

At $z = 1$ on this same line, the minus-wave voltage is:

$$V^-(z = 1) = 2.0 \text{ V}$$

Determine the value of the **plus-wave voltage**, at transmission line location $z = 1$.
In other words, determine the value $V^+(z = 1)$.

Solution:

We have some relations between the decomposed wave components and reflection function:

$$\Gamma(z, \omega) = \frac{V^-(z, \omega)}{V^+(z, \omega)} \quad V(z, \omega) = V(z, \omega)^+ + V(z, \omega)^-$$

The reflection coefficient makes this straightforward,

$$V^+(z, \omega) = \frac{2.0 e^{j0}}{j 0.5 e^{+j\pi}} = \frac{2}{0.5j} = 4j \text{ V}$$

Problem 2

For a certain transmission line, $\beta = \pi/2$ (radians/m) and $Z_0 = 50 \Omega$.

We know that the total voltage at location $z = -1$ m on this transmission line is:

$$V(z = -1) = j 6 \text{ V}$$

The reflection coefficient function at location $z = 1$ m is likewise:

$$\Gamma(z = 1) = -0.25$$

Determine the total current at location $z = 0$ (i.e., $I(z = 0)$) on this transmission line.

Solution:

Starting with the same relations:

$$\Gamma(z, \omega) = \frac{V^-(z, \omega)}{V^+(z, \omega)} \quad (1)$$

$$V(z, \omega) = V(z, \omega)^+ + V(z, \omega)^- \quad (2)$$

$$Z_0 = \frac{V^+(z, \omega)}{I^+(z, \omega)} \quad (3)$$

$$-Z_0 = \frac{V^-(z, \omega)}{I^-(z, \omega)} \quad (4)$$

And β is sufficient to make the additional relations:

$$V^+(z, \omega) = V_0^+(\omega)e^{-j\beta z} \quad V^-(z, \omega) = V_0^-(\omega)e^{+j\beta z} \quad (5)$$

$$I^+(z, \omega) = I_0^+(\omega)e^{-j\beta z} \quad I^-(z, \omega) = I_0^-(\omega)e^{+j\beta z} \quad (6)$$

It is most convenient to start with some relations since we know β

$$V_0^+ = \frac{V^+}{e^{+j\pi/2}} = jV^+ \quad V_0^- = \frac{V^-}{e^{-j\pi/2}} = -jV^-$$

Use (1-2) extract components for a fixed $z = 1$:

$$\begin{aligned} & \begin{cases} -j0.25V_0^+(z=1, \omega) = -jV_0^-(z=1, \omega) \\ j6 \text{ V} = j(V_0^+(z=1, \omega) - V_0^-(z=1, \omega)) \end{cases} \quad (\text{At } z=-1) \\ \Rightarrow & \begin{cases} V_0^+(z=1, \omega) = 8\text{V} \\ V_0^-(z=1, \omega) = 2\text{V} \end{cases} \end{aligned}$$

Current falls out of (3):

$$I_0^+ = \frac{V^+}{Z_0} = -\frac{8}{50} = 0.16 \text{ A} \quad I_0^- = -\frac{V^-}{Z_0} = \frac{2}{50} = 0.04 \text{ A}$$

Total current I is given as the sum:

$$I(z=0, \omega) = I_0^+ + I_0^- = 0.20 \text{ A}$$