


EECS 622: Homework #8

September 30, 2025

Grant Saggars

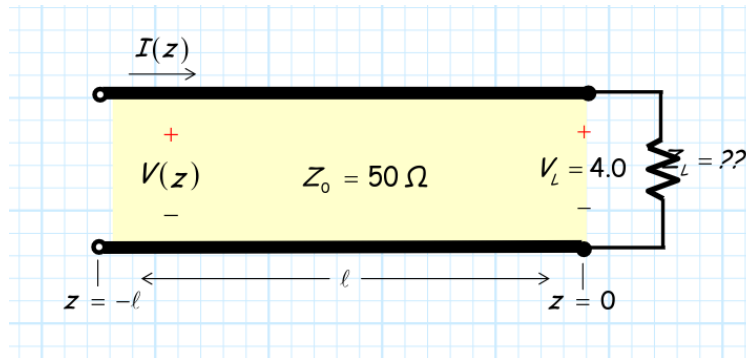Problem 1

Consider a terminated, lossless **transmission line**:



The wave **reflected from load** Z_L has the form:

$$V^-(z) = -2e^{+j\beta z}$$

And the load voltage is:

$$V_L = 4.0$$

Determine the value of load Z_L .

Solution:

The load establishes the boundary conditions on the right, such that

$$V_L \equiv V_0, \quad I_L = I_0$$

And we could claim

$$Z_L = \frac{V_0}{I_0}$$


By our definition of characteristic impedance we can express I_0 :

$$\begin{aligned} I(z, \omega) &= \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{+j\beta z} \\ I(z = 0, \omega) \equiv I_0 &= \frac{V^+}{Z_0} - \frac{V^-}{Z_0} \\ I_0 &= \frac{V_L - V_0^-}{Z_0} - \frac{V_0^-}{Z_0} \quad (\text{because } V(z) \equiv V^+(z) + V^-(z)) \end{aligned}$$

Therefore,

$$\begin{aligned}
 Z_L &= \frac{V_L}{\frac{V_L - V_0^-}{Z_0} - \frac{V_0^-}{Z_0}} \\
 &= \frac{V_L}{\frac{V_L - 2V_0^-}{Z_0}} \\
 &= \frac{4 \text{ V } Z_0 \Omega}{4 + 2 + 2 \text{ V}} \\
 &= 25 \Omega
 \end{aligned}$$

Problem 2

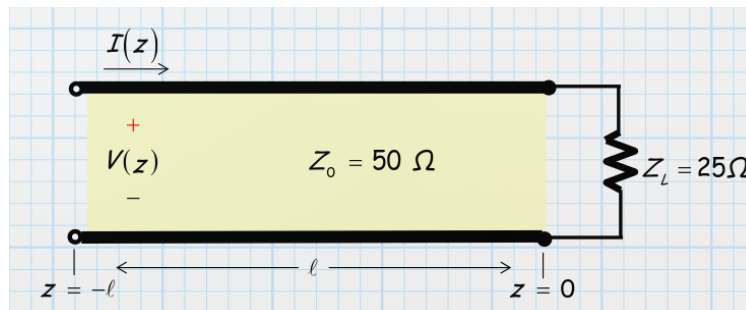

The total voltage at location $z = 0$ is:

$$V(z = 0) = j 2.0 \text{ V}$$

Determine the value of the **reflected voltage wave** at location $z = 0$ (i.e., $V^-(z = 0)$).

Solution:

We have a convenient expression for:

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (1)$$

Where,

$$\Gamma_0 = \frac{V_0^-}{V_0^+} \quad (2)$$

Substituting this into the complete wave solution I can solve for V^+

$$\begin{aligned}
 V(z, \omega) &\equiv V^+(z, \omega) + V^-(z, \omega) \\
 V_0 &= V_0^+ + \Gamma_0 V_0^+ & (V_0^- = \Gamma V_0^+) \\
 V_0 &= V_0^+ (1 + \Gamma_0) & \text{(Algebra)} \\
 V_0^+ &= \frac{V_0}{1 + \Gamma_0} & (3)
 \end{aligned}$$

Using (3) I can eliminate V_0^+ from (2):

$$V_0^- = \frac{\Gamma_0 V_0}{1 + \Gamma_0}$$

$$V_0^- = \frac{\frac{Z_L - Z_0}{Z_L + Z_0} V_0}{1 + \frac{Z_L - Z_0}{Z_L + Z_0}}$$

$$V_0^- = \frac{(-1/3)(j2)}{1 + (-1/3)}$$

$$V_0^- = -\frac{j}{2} V$$