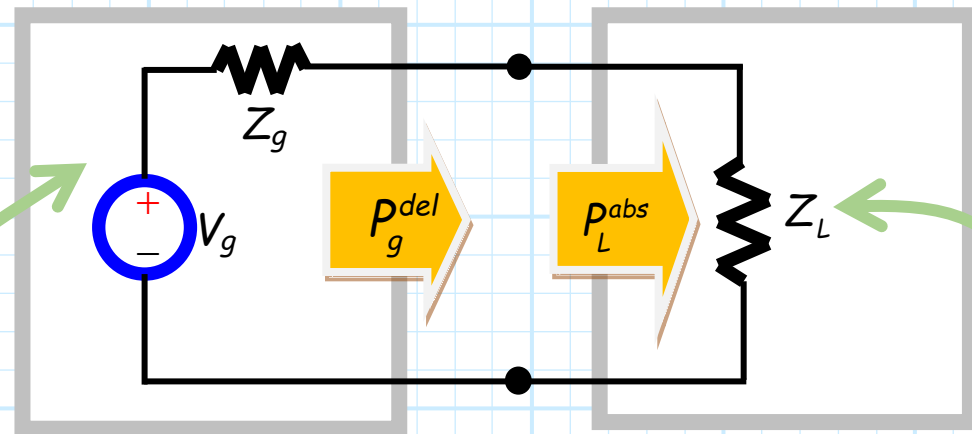


# Special Cases of Source and Load Impedance

Consider again the power **absorbed** by the load (delivered by the source):

$$p_g^{del} = p_L^{abs} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_g + Z_L|^2}$$



It is evident that this power transfer is dependent on **each and every element** of the equivalent circuit:

1. the source parameters  $V_g$  and  $Z_g$ ,
2. as well as the load impedance  $Z_L$ .

## You would think that maximum power transfer would not be so controversial

**Q:** *I assume that we want to **maximize** this power transfer.*

*How can we maximize  $P_L^{abs}$  ??*


**A:** The answer to that question is among the **best known** in electrical engineering.

→ Unfortunately, it is also frequently **misunderstood** and misapplied—**so pay attention!**

## Carefully consider this question

First, let's ask **this** question:

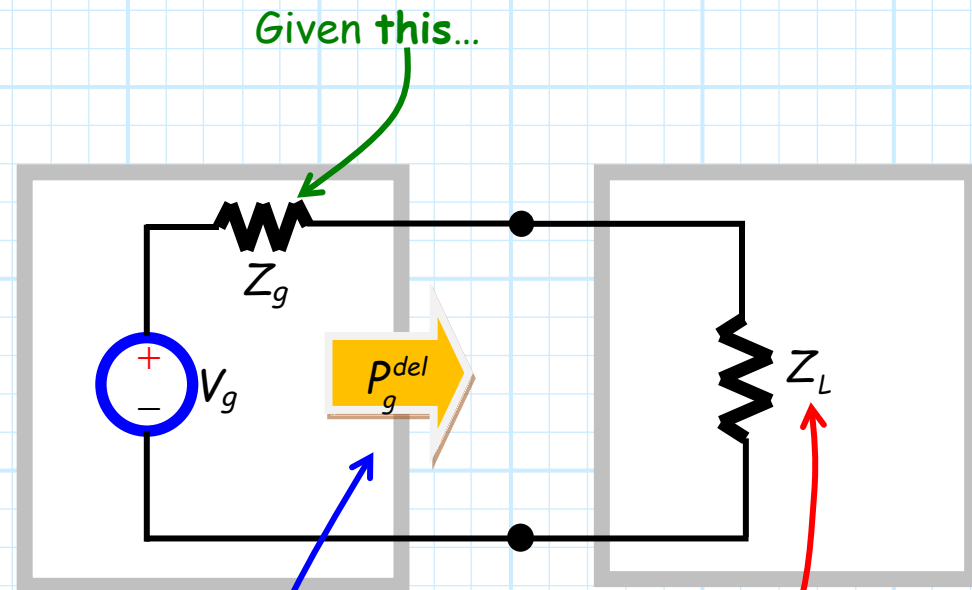**Q1:** What **load** impedance  $Z_L$  will maximize the power delivered by a **given source** (i.e., maximize  $P_g^{del}$ )?



**A1:** A **load** impedance with value:

$$Z_L = Z_g^*$$

will maximize the power **delivered by the source.**


## The available power of the source

We can likewise determine the **value** of this maximum power!

For  $Z_L = Z_g^*$ , we find:

$$P_g^{del} \Big|_{Z_L=Z_g^*} = \frac{|V_g|^2}{2} \frac{R_g}{|Z_g + Z_g^*|^2} = \frac{|V_g|^2}{2} \frac{R_g}{|2R_g|^2} = \frac{|V_g|^2}{8R_g}$$

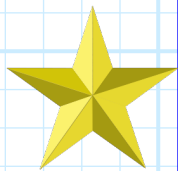This maximum delivered power is **very important**; it is dubbed the **available power**  $P_g^{avl}$  of the source:



$$P_g^{avl} = \frac{|V_g|^2}{8R_g}$$

Note the available power is **dependent just on source parameters** (i.e.,  $V_g$  and  $R_g$ ).

And so  $P_g^{avl}$  is a parameter of the **source only**!


## Available power is an upper limit

Available power is the **maximum**—the upper limit on—power that can be **delivered** by a source, i.e.:

$$P_g^{del} \leq P_g^{avl}$$

This **available** source power—the **maximum** possible—is delivered **only if** the **load impedance** is numerically equal to the complex conjugate of the source impedance (i.e.,  $Z_L = Z_g^*$ ):



$$P_g^{del} = P_g^{avl} = \frac{|V_g|^2}{8R_g} \quad \text{iff} \quad Z_L = Z_g^*$$

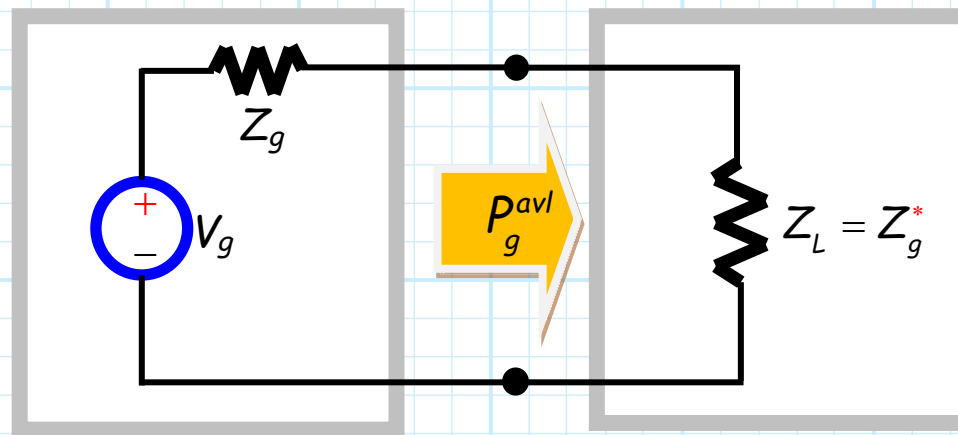

# Consider this completely different question!

Now, let's ask a **completely different question**:

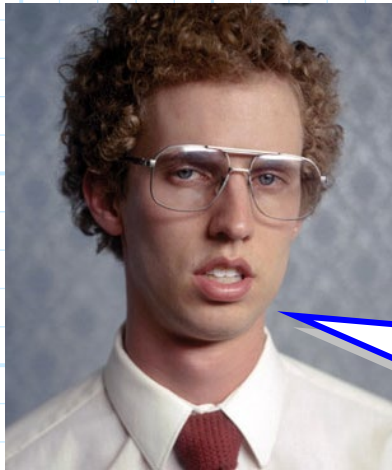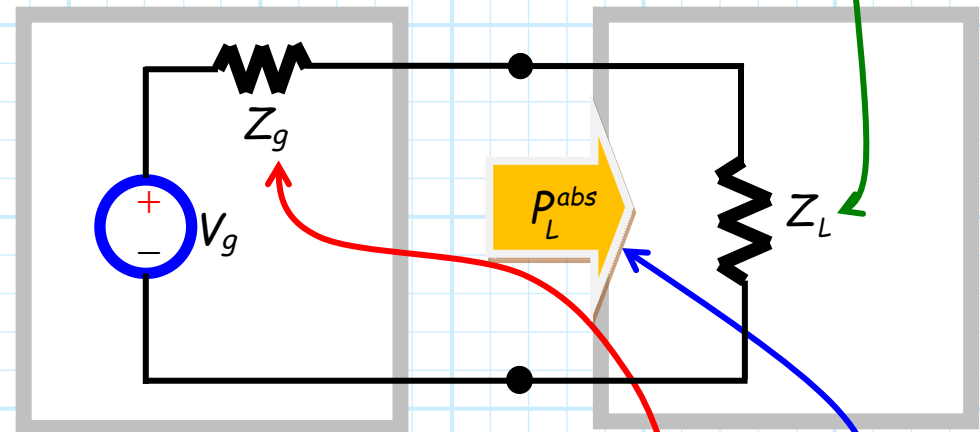**Q2:** What **source** impedance  $Z_g$  will maximize the power absorbed by a **given load** (i.e., maximize  $P_L^{abs}$ )?



Like, don't we already know the answer?  
Absorbed power is maximized by a  
**conjugate match**:

$$Z_g = Z_L^*. \quad \text{Gosh!}$$

NOT!

**A2:** Not. So. Fast.

It can be shown that the value of **source** impedance  $Z_g$  that maximizes the power **absorbed by the load**  $Z_L$  is—in fact—**purely reactive**, with value:

$$Z_g = -jX_L$$

where  $X_L$  is the imaginary (i.e., **reactive** portion of the load ( $X_L = \text{Im}\{Z_L\}$ ))!

## The importance of asking the right question

Thus, we conclude a **correct** question—and answer—is:

**Q2:** What **source** impedance  $Z_g$  will maximize the power absorbed by a **given load** (i.e., maximize  $P_{abs}$ )?

**A2:** The **source** impedance  $Z_g = -jX_L$  will maximize the power absorbed by a **given load** (i.e., maximize  $P_{abs}$ ).

Although it is **very common** for electrical engineers to assume the answer to question **Q2** is **instead** answer **A1** (i.e.,  $Z_g = Z_L^*$ ), this is **far** from the correct answer!

Question **Q1** and question **Q2** are **completely different**—it should be **no** surprise that **answers A1** and **A2** are completely different as well.



## Here; I'll prove it to you

Using the **correct** solution for **Q2** ( $Z_g = -jX_L$ ), we find the power absorbed by the load is then:

$$p_L^{abs} \Big|_{Z_g = -jX_L} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_g + Z_L|^2} = \frac{|V_g|^2}{2 R_L}$$

Whereas, if we enforce a “**conjugate match**”, by setting the source impedance to be  $Z_g = Z_L^*$ , the load **instead** absorbs energy at a rate:

$$p_L^{abs} \Big|_{Z_g = Z_L^*} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_L^* + Z_L|^2} = \frac{1}{4} \frac{|V_g|^2}{2 R_L}$$


The power absorbed by the load when  $Z_g = Z_L^*$  is just **25%** of the power absorbed when  $Z_g = -jX_L$ !

## It's maximum—but far less than the available

**Q:** But if  $Z_L \neq Z_g^*$ , isn't the absorbed power *less* than the *available* power ??

**A:** Darn right it's **not**!

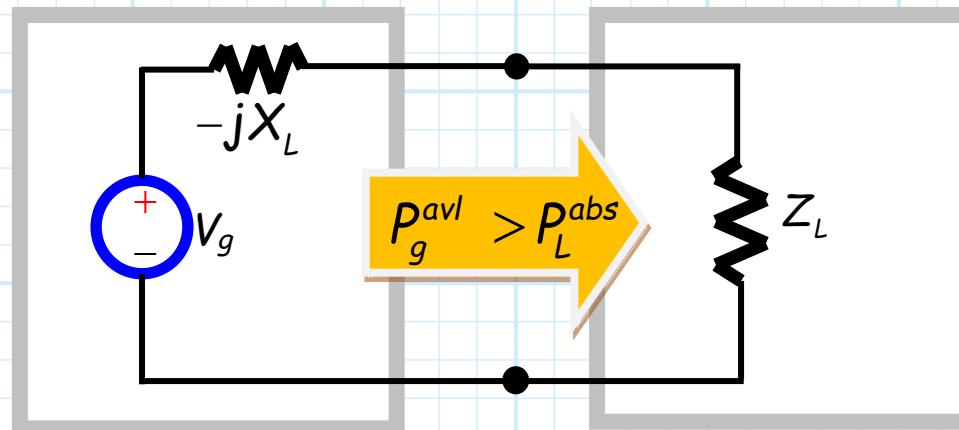If  $Z_g = -jX_L$ , the absorbed power is **far less** than the **available** power.



## Dazed and Confused

**Q:** *I'm so confused!*

*I thought you said that setting  $Z_g = -jX_L$  actually **maximizes** the absorbed power.*

*How can the power be maximized if it is less than the **available** power??*

**A:** Here's the deal; setting the source impedance to  $Z_g = -jX_L$  (i.e.,  $R_g = 0$ ) **does** in fact maximize the power absorbed by the load.

But, it **also** increases the available power of the source—increases it all the way to **infinity** (but not beyond)!



$$\lim_{R_g \rightarrow 0} P_g^{avl} = \lim_{R_g \rightarrow 0} \frac{|V_g|^2}{8R_g} = \infty$$

## A finite value is always less than infinity!

The maximized absorbed power (when  $Z_g$  is set to  $Z_g = -jX_L$ ) is **finite**—therefore it is much less than the **infinite** available power!

$$P_L^{abs} \Big|_{Z_g = -jX_L} = \frac{|V_g|^2}{2R_L} \ll P_g^{del} \Big|_{Z_g = -jX_L} = P_g^{avl} = \infty$$

**Contrast** this with altering the value of **load** impedance  $Z_L$  (i.e., **Q1**).

Altering the **load** changes the **delivered** power  $P_g^{del}$  but does **not** alter the **available** power  $P_g^{avl}$  of the source.

Thus, the best we can do is set  $Z_L$  such that **all available power(100%)** is delivered to the load (i.e., set  $Z_L = Z_g^*$ ).

## First find the biggest plate of cookies, then eat as many of them as you can

Of course, achieving **infinite** available power is **not practical**—the available power  $P_g^{avl}$  of any **realizable** source is **finite**.

Still, engineers attempting to **maximize** the power **absorbed** by a load should:

1. Attempt to select/design/alter the **source** such that its **available power**  $P_g^{avl}$  is **maximized**.
2. Then, attach a **load** that is conjugate matched ( $Z_L = Z_g^*$ ) to this source, such that **all available power is delivered** to the load.

## 1% of Bill Gate's \$\$\$, or 100% of mine?

A problem that often arises is that a source with a **large available power** usually has likewise a very **low source impedance**,

→ This makes it is **difficult/impractical** to provide a load where  $Z_L = Z_g^*$ .

Engineers sometimes **erroneously** alter/design/select **another source** that it **easier** to “match”, but usually this results in a dramatic **decrease in available power!**

For **example**, consider two cases:

Source	Available Power	Delivered Power
1	500 mW	200 mW
2	100 mW	100 mW

→ For **which** source is “power transfer maximized”?

## Most of a lot is better than all of very little

For source 2, **100%** of the **available power** is delivered to the load—clearly the **load is a conjugate match** to the source impedance.

For source 1, **only 40%** of the available power is delivered to the load—the load is most definitely **not conjugate matched** to source impedance.

Yet, the **mismatched load** absorbs **twice** the power of the “mismatched” case!

It does so because the available power of source 1 is **five times** larger than that of source 2.

→ It's better to have **most of a lot**, rather than **all of very little!!**

## Be careful!

Hence, we need to be **careful** when considering a conjugate match.

Ask yourself, what does "maximum power transfer" **really** mean?

Is **your** design problem described by **Q1** or by **Q2**?

→ Matching a load to a source is a good idea, but altering the source to match the load is typically **not**.

These questions have—and continue to—spark many **unpleasant disagreements** among electrical engineers!!

