


LO Drive Power

Q: I don't understand.

The "control voltage" for the switching mixer is the *LO* signal.

$$v_{ctrl}(t) = v_{LO}(t)$$

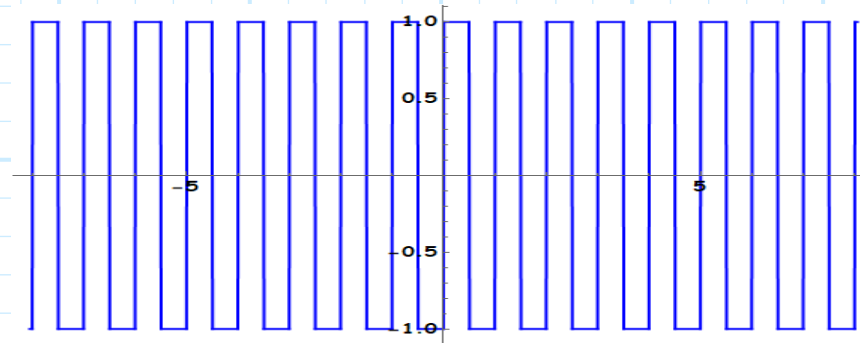But, the "control voltage" for the switching mixer analysis was a **square wave**.



And yet, the *LO* oscillator produces a **sinewave**.

A: This is all true.


MOSFET as a switch

Consider this **active** mixer design:

Note the **LO** port is attached to the **gate terminals** of the NMOS devices.

These (non-linear) NMOS devices are acting as **switches**—they ideally toggle between **cutoff** mode (i.e., switch is **open**), and **triode** mode (i.e., switch is **closed**).

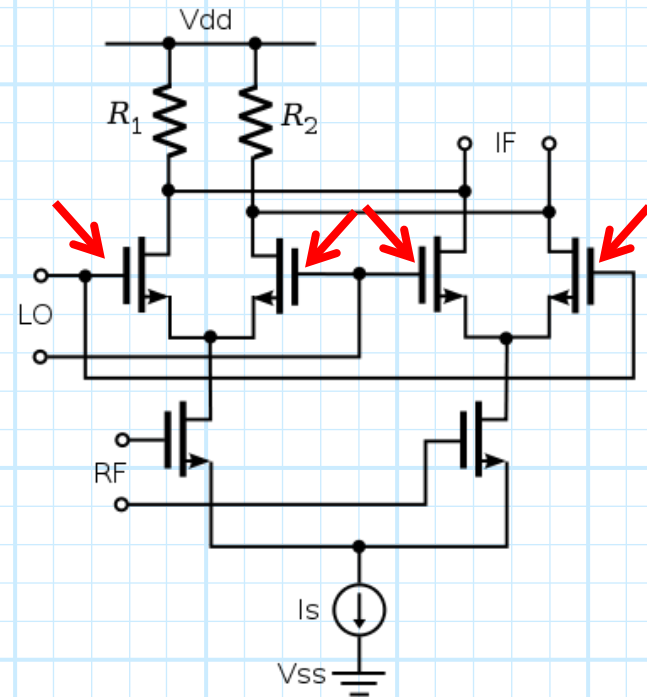https://commons.wikimedia.org/wiki/File:Double_Balanced_Mixer_in_Integrated_Circuit.svg



cutoff mode



triode mode



The mode of these NMOS devices are of course determined by the **gate voltage**—which is clearly the **LO voltage**!

Cutoff and Triode

Thus, if the LO sinusoidal voltage is **large enough**, it will **toggle** the MOSFET switch between **open** and **closed** (just like a square-wave would).

When the LO voltage is **sufficiently positive**:

$$v_{LO}(t) > V_G^{closed}$$

the "switch" will **close** (triode!).




And when the LO voltage is **sufficiently negative**:

$$v_{LO}(t) < V_G^{open}$$

the "switch" will **open** (cutoff).



Just be large enough to switch

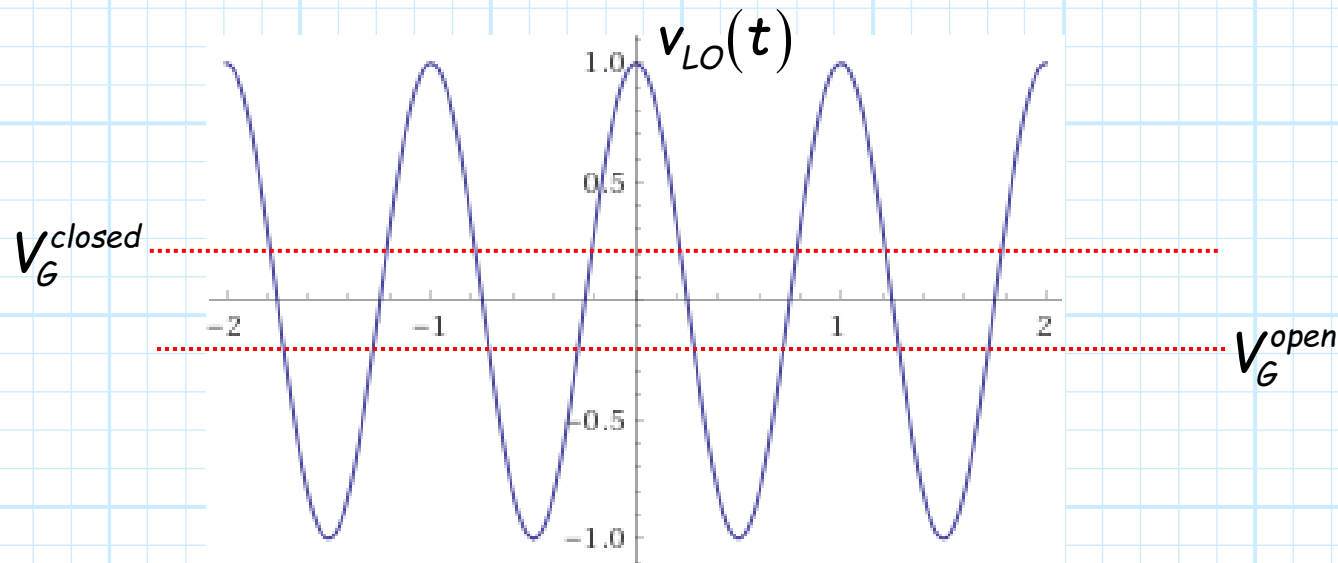


Thus—for this switch control—it **doesn't much matter** whether the LO signal is a **square-wave** or a **sine-wave**, just as long as it:

- a)** is oscillating at the **proper frequency** ω_{LO} , and
- b)** is **sufficiently large**!

A balanced diode mixer

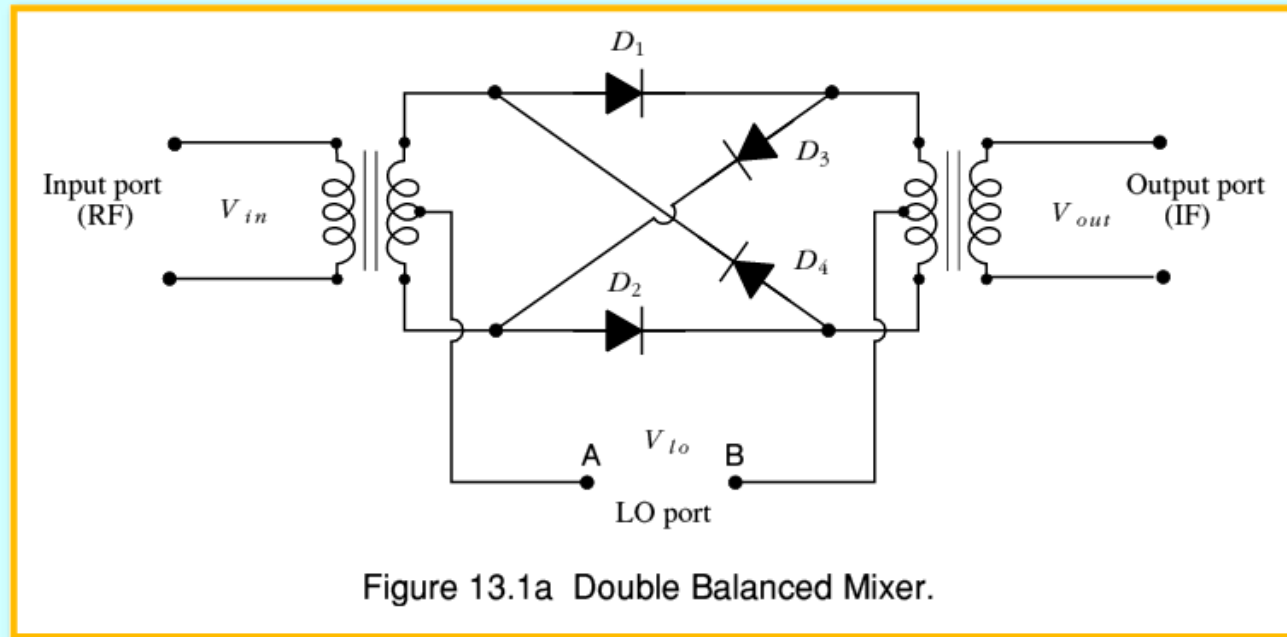Passive mixers generally implement **diodes**; for example:



https://www.st-andrews.ac.uk/~www_pa/Scots_Guide/RadCom/part13/page1.html

The job of the LO signal is to “switch” the non-linear diodes between emphatically **reverse-biased** (switch is **open**) and emphatically **forward-biased** (switch is **closed**).

Make sure you do this...

Again, the LO signal needs to **be sufficiently large** to (emphatically) change these diode **bias states**.

Q: So *how large* is "sufficiently large"?

A: For passive (i.e., **diode**) balanced mixers, we find that this drive power is **typically** in a range from **+8.0 to +16.0 dBm**.

This value is a very important device parameter, called the mixer **LO drive power** P_{drive}^{LO} .

To achieve the specified mixer conversion loss (e.g., 4.0 dB), the LO signal power **MUST** exceed this LO drive power:

$$P_{avl}^{LO} > P_{drive}^{LO}$$

It is up to **you** (i.e., the engineer) to **ensure** this is achieved!

...because bad things happen if you don't!

Q: So, what happens if my LO signal power P_{avl}^{LO} is less than my mixer LO drive power P_{drive}^{LO} ?


A: Besides getting fired, you will find that the **apparent conversion loss** of the mixer will **increase** (which is **why** you got fired)!



When the LO signal is **too small**, it **cannot** adequately “switch” the semiconductor devices in the mixer.

For example, the switching NMOS devices may be **neither** in cutoff or triode—it instead might be in **saturation mode**!

Saturation mode

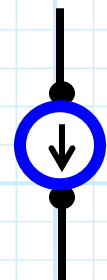
$$i = K(v_{GS} - V_t)^2$$

We call it multiplier mode

As a result, the (too small) LO voltage becomes like a “**small-signal**”, and we say the mixer is **no longer** in “**switch**” mode!


Instead, we say the mixer is in “**multiplier mode**”, where the IF signal power (and thus conversion loss) is **proportional** to the LO power.

$$P_{IF} \propto A_{RF}^2 A_{LO}^2$$

This is **bad news**, since your LO power is now **not** particularly large!


Conversion Loss increases proportionally

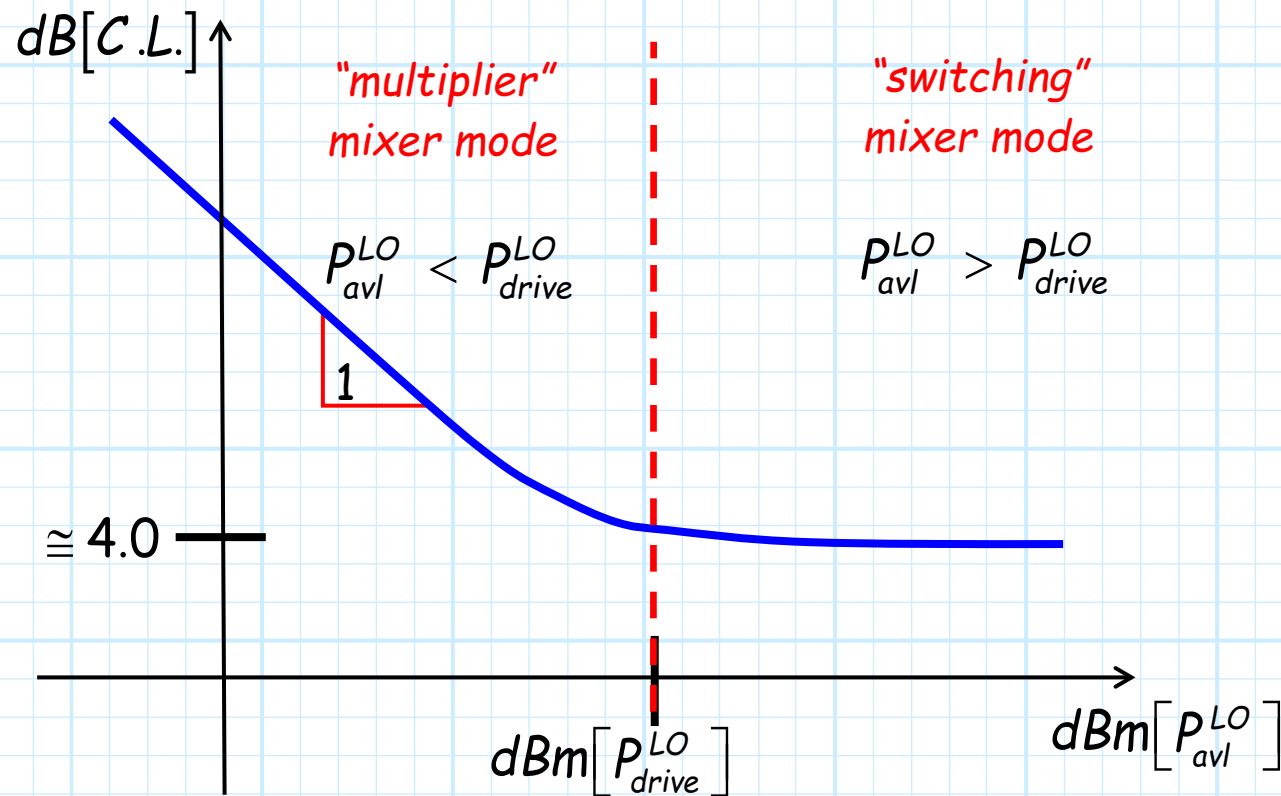Thus, if the LO power drops **below** the required mixer drive power, the conversion loss will increase **proportionately**—1 dB per dB!



For example

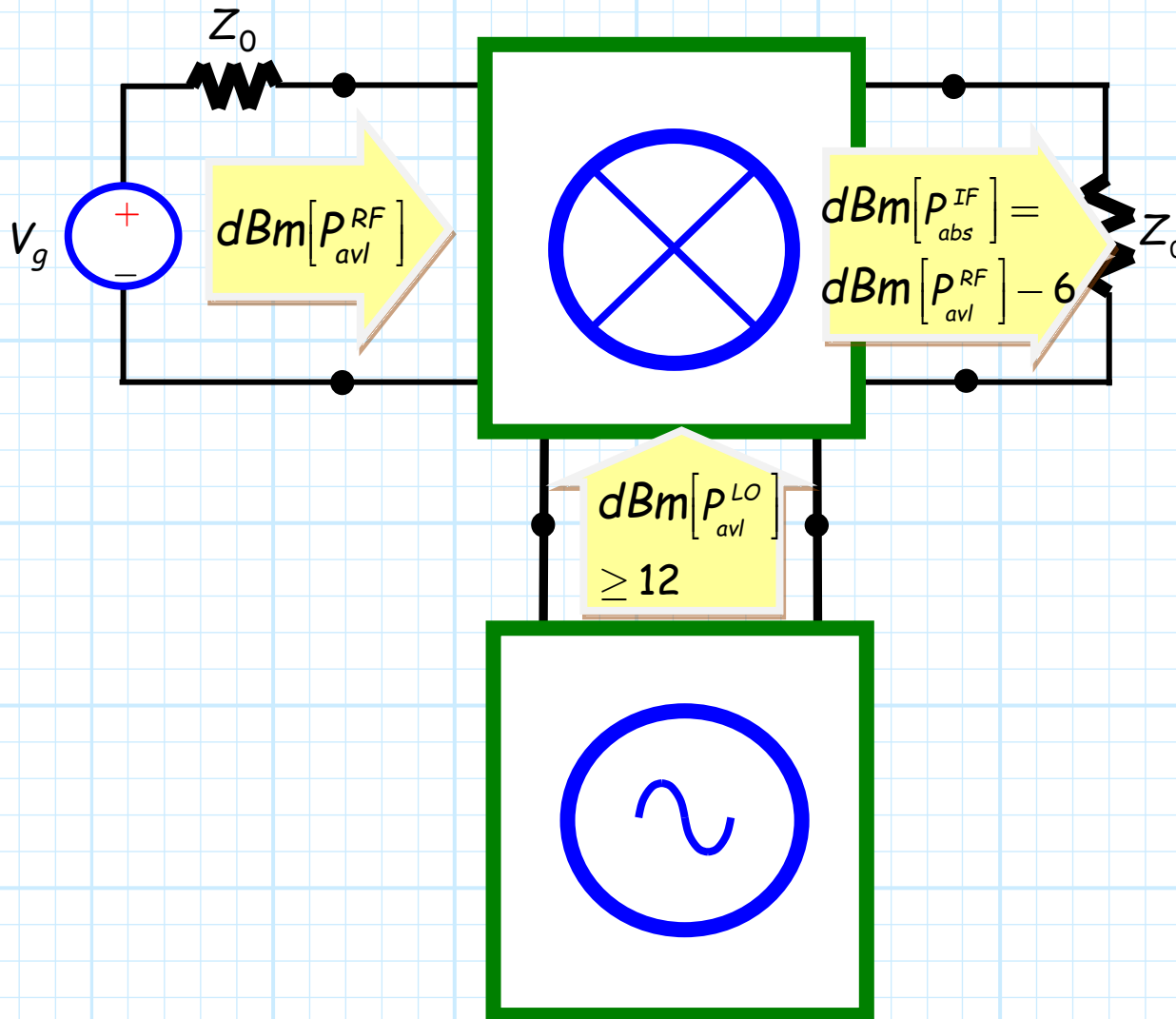For **example**, say a mixer requires an LO drive power of 12.0 dBm, and exhibits a conversion loss of 6.0 dB...



Don't starve your mixer!!!

...now say we mistakenly drive the mixer with an LO signal of **only +5 dBm** (7dB less than the drive power!).

We find that the mixer conversion loss will **increase** to 13.0 dB (**7 dB**) more than before!

In other words, if we “**starve**” our mixer LO by **7.0 dB**, then we will increase the **conversion loss** by **7.0 dB**.

Lesson learned →
Don't starve your mixer!

