


EECS 622: Homework #1

September 5, 2025

Grant Saggars

Problem 1

Consider the circuit:

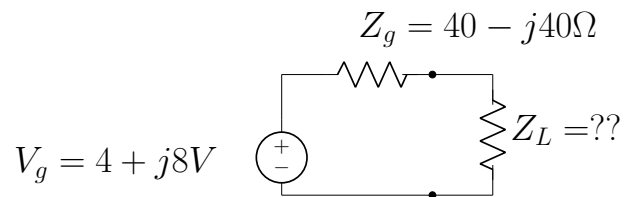

Given the values of V_g and Z_g , determine:

- (a) The value of load impedance Z_L that will maximize the power source delivered by this source.

Solution:

A load impedance with value:

$$Z_L = Z_g^*$$

will maximize the power delivered by the source. Therefore, we should choose Z_L equal:

$$\boxed{Z_L = 40 + j40 \Omega}$$

(b) The value of this maximum power.

Solution:

Numerically, we will have


$$\begin{aligned}
 P_g^{del} \Big|_{Z_L=Z_g^*} &= \frac{1}{2} I_{RMS} I_{RMS}^* R && \text{(Definition of Power for a Sinusoidal Source)} \\
 &= \frac{R_g}{2} \left(\frac{V_g}{Z_L + Z_g} \right) \left(\frac{V_g^*}{Z_L^* + Z_g^*} \right) \Big|_{Z_L=Z_g^*} && \text{(Substitute } I \text{ and } R) \\
 &= \frac{R_g}{2} \left(\frac{VV^*}{Z_L Z_L^* + Z_L Z_g^* + Z_L^* Z_g + Z_g Z_g^*} \right) \Big|_{Z_L=Z_g^*} && \text{(Expand)} \\
 &= \frac{R_g}{2} \left(\frac{VV^*}{Z_g Z_g^* + Z_g Z_g^* + Z_g^* Z_g + Z_g Z_g^*} \right) && \text{(Apply Boundary)} \\
 &= \frac{VV^*}{8} \left(\frac{R_g}{Z_g Z_g^*} \right) && \text{(Algebra)} \\
 &= \frac{VV^*}{8R_g} && (Z_g Z_g^* = |R_g|^2)
 \end{aligned}$$

This just shows that we have the same circuit as in the lecture. R_g is simply $\text{Re}\{Z_g\} = 40 \Omega$. Maximum power is then:

$$P_g^{del} = \frac{(4 + j8)(4 - j8)}{8 \cdot 40} = 0.25 \frac{\text{J}}{\text{s}}$$

Problem 2

Now consider the circuit:

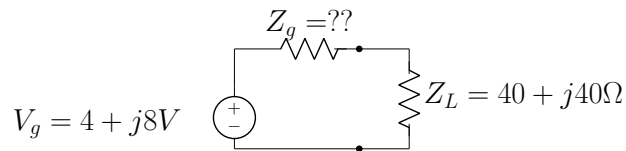

Given the values of V_g and Z_g , determine:

(a) The value of source impedance Z_g that will maximize the power absorbed by load Z_L .

Solution:

It can be shown that the value of source impedance Z_g that maximizes the power absorbed by the load Z_L is-in fact-purely reactive, with value:

$$Z_g = -jX_L$$

Therefore, $Z_g = -j40 \Omega$ to maximize the power absorbed by the load.

(b) The value of this maximum power.

Solution:

With a purely reactive Z_g , we should expect total resistance to just be R_L :

$$\begin{aligned} Z_{total} &= Z_g + Z_L = (-jX_L) + (R_L + jX_L) \\ &= R_L + (jX_L - jX_L) \\ &= R_L \end{aligned}$$

Great, I can derive the power for this in the same way:

$$\begin{aligned} P_L^{abs} &= \frac{1}{2} I_{RMS} I_{RMS}^* R && \text{(Definition of Power for a Sinusoidal Source)} \\ &= \frac{V_g V_g^*}{2} \left(\frac{R_L}{R_{total}^2} \right) && \text{(Substitute I and R)} \\ &= \frac{V_g V_g^*}{2} \left(\frac{R_L}{|R_L|^2} \right) && (Z_{total} = R_L) \\ &= \frac{V_g V_g^*}{2R_L} \end{aligned}$$


Again, what we got in class. Power delivered is then just:

$$P_L^{abs} = \frac{(4 + 8i)(4 - 8i)}{2 \cdot 40} = 1 \frac{\text{J}}{\text{s}}$$

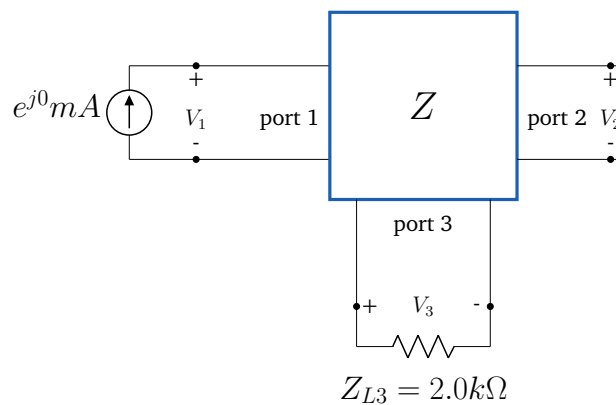Problem 3

$$\mathbf{Z} = \begin{bmatrix} 1 & j & 1 \\ j & 2 & 2 \\ 1 & 2 & 3 \end{bmatrix} \text{ k}\Omega$$

I will define I pointed into Z . Determine both the complex current vector I , and the complex voltage vector V .



Solution:

We will have a system of 6 equations:

$$V_1 = I_1 + jI_2 + I_3 \quad (1)$$

$$V_2 = jI_1 + 2I_2 + 2I_3 \quad (2)$$

$$V_3 = I_1 + 2I_2 + 3I_3 \quad (3)$$

$$I_1 = -e^{j0} \quad (4)$$

$$V_2 = 0 \quad (5)$$

$$V_3 = -2I_3 \quad (6)$$

Equations 1-3 are given by the impedance matrix. Equations 4-6 are boundary conditions describing the circuit attached to the terminals. The algebra is as follows:

$$\begin{cases} V_1 = -e^{j0} + jI_2 + I_3 \\ 0 = -je^{j0} + 2I_2 + 2I_3 \\ -2I_3 = -e^{j0} + 2I_2 + 3I_3 \end{cases} \quad (\text{Substitute 4-6 into 1-3})$$

$$\begin{cases} V_1 = -1 + jI_2 + I_3 \\ j = 2I_2 + 2I_3 \\ 1 - 5I_3 = 2I_2 \end{cases} \quad (\text{Simplify})$$

$$\begin{cases} V_1 = -1 + jI_2 + I_3 \\ \frac{1}{3} - \frac{j}{3} = I_3 \\ 1 - 5I_3 = 2I_2 \end{cases} \quad (\text{Simplify eqn. 2})$$

$$\begin{cases} V_1 = -1 + jI_2 + I_3 \\ \frac{1}{3} - \frac{j}{3} = I_3 \\ -\frac{1}{3} + \frac{5}{6}j = I_2 \end{cases} \quad (\text{Substitute eqn. 2 into 3})$$

$$\begin{cases} -\frac{3}{2} - \frac{2}{3}j = V_1 \\ \frac{1}{3} - \frac{j}{3} = I_3 \\ -\frac{1}{3} + \frac{5}{6}j = I_2 \end{cases} \quad (\text{Substitute all into eqn. 1})$$

To summarize:

$$\begin{aligned} V_1 &= -\frac{3}{2} - \frac{2}{3}j & V_2 &= 0 & V_3 &= -\frac{2}{3} + \frac{2}{3}j \\ I_1 &= -1 & I_2 &= -\frac{1}{3} + \frac{5}{6}j & I_3 &= \frac{1}{3} - \frac{j}{3} \end{aligned}$$