

EECS 622: Homework #7

September 25, 2025

Grant Saggars

Problem 1

The total voltage along a transmission line is:

$$V(z) = 14e^{-j(\pi/2)z} + 2e^{j(\pi/2)z}$$

The line impedance at location $z = 1$ on this same line is:

$$Z(z = 1) = 7.5\Omega$$

Determine the value of total current at transmission line location $z = 1$.
In other words, determine the value $I(z = 1)$.

Solution:

$$Z(z, \omega) \equiv \frac{V(z, \omega)}{I(z, \omega)} \quad (1)$$

Using (1),

$$\begin{aligned} I(z = 1, \omega) &= \frac{V(z = 1, \omega)}{Z(z = 1, \omega)} \\ &= \frac{-14j + 2j}{7.5} \\ &= -1.6j \text{ A} \end{aligned}$$

Problem 2

A certain transmission line has $\beta = \pi/2$ (radians/m).

We know that the reflection coefficient function at location $z = 1$ is:

$$\Gamma(z = 1) = -0.5$$

and the line impedance at location $z = 0$ is:

$$Z(z = 0) = 120\Omega$$

and the total voltage at location $z = -1$ is:

$$V(z = -1) = j4 \text{ V}$$

Determine the function $I(z)$ that describes the time-harmonic current along this transmission line.

Solution:

I just need to fit boundary conditions to the wave equations.

$$Z(z, \omega) \equiv \frac{V(z, \omega)}{I(z, \omega)} = Z_0 \left(\frac{e^{-j\beta z} + \Gamma_0 e^{+j\beta z}}{e^{-j\beta z} - \Gamma_0 e^{+j\beta z}} \right) \quad (1)$$

$$\Gamma \equiv \Gamma_0 e^{+j2\beta z} \quad (2)$$

$$\Gamma_0 \equiv \frac{V_0^-}{V_0^+} \quad (3)$$

$$I(z, \omega) = \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{+j\beta z} \quad (4)$$

It's possible to find Γ_0 using (2):

$$\Gamma_0 = 0.5 e^{j\pi(0-1)} = 0.5$$

Then, with (3) the components can be related by a scalar:

$$0.5 = \frac{V_0^-}{V_0^+} \implies 0.5 V_0^+ = V_0^-$$

This lets me derive V^+ , V^- components by substituting for one in the definition of V :

$$\begin{aligned} V(z = -1) &= V^+ e^{-j(\pi/2)(-1)} + V^- e^{j(\pi/2)(-1)} \\ j4 &= V^+ e^{-j(\pi/2)(-1)} + 0.5 V^+ e^{j(\pi/2)(-1)} \\ j4 &= jV^+ - 0.5jV^+ \\ j4 &= 0.5jV^+ \\ V^+ &= 8 \text{ V} \end{aligned}$$

Consequently, $V^- = 4 \text{ V}$. $Z(z = 0) \neq Z_0$, and it is instead given by (1):

$$120 = \frac{1 + \Gamma_0}{1 - \Gamma_0} = 3Z_0$$

Finally, (4) gives the solution we wanted:

$$I(z, \omega) = \frac{8}{40} e^{-j\pi z/2} - \frac{4}{40} e^{j\pi z/2} \text{ A}$$